

# Impedance, Resonance, and Filters



**Al Penney**

**VO1NO**

# A Quick Review...

- Before discussing Impedance, we must first understand capacitive and inductive reactance.

# Reactance

- **Reactance** is the **opposition** to the **flow of Alternating Current (AC)**.
- **Reactance** has **no effect** on the flow of **Direct Current (DC)**.

# Capacitive Reactance

- **Capacitive Reactance** is the **opposition** to the **flow of AC** by capacitance.
- As the **frequency of the AC** increases, **Capacitive Reactance** decreases.
- The **Symbol for Capacitive Reactance** is  $X_C$ .
- $X_C$  is expressed in **ohms**.
- Even though it is expressed in ohms, **power is not dissipated by Reactance!** Energy stored in a **capacitor** during **one part of the AC cycle** is simply **returned to the circuit** during the **next part of the cycle!**

# Capacitive Reactance

$$X_C = \frac{1}{2 \pi f C}$$

- Where:  
**F** = frequency in Hertz  
**C** = capacitance in Farads  
 **$\pi$**  = 3.14

# Inductive Reactance

- **Inductive Reactance** is the **opposition** to the **flow of current** in an **AC circuit** caused by an **inductor**.
- As the **frequency increases**, Inductive Reactance **also increases**.
- The **symbol for Inductive Reactance** is  $X_L$ .
- Even though it is expressed in ohms, **power is not dissipated by Reactance!** Energy stored in an **inductor's magnetic field** during **one part of the AC cycle** is simply **returned to the circuit** during the **next part of the cycle!**

# Inductive Reactance

$$X_L = 2 \pi f L$$

- Where:

**f = frequency in Hertz**

**L = inductance in henrys**

**$\pi = 3.14$**


# Current versus Voltage

- In a simple **resistive** circuit, the **current and voltage are always in phase.**
- For reasons beyond the scope of the Basic Course, the current and voltage are **not in phase in AC circuits** that contain **capacitance and/or inductance.**
- The **current** across a **capacitor** leads the voltage by **90 degrees.**
- The **current** across an **inductor** lags the voltage by **90 degrees.**



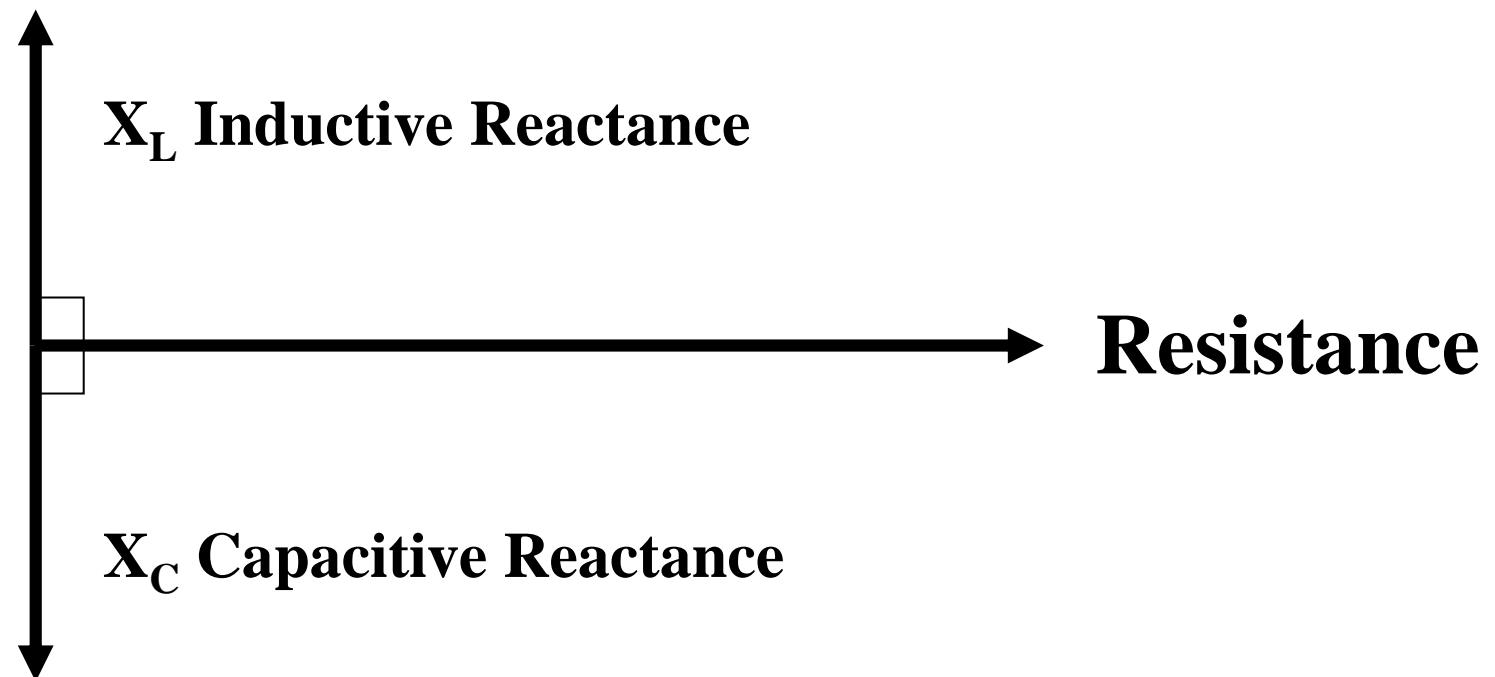
# Vector Representation

- When plotted as **vectors**, **series circuits** containing Inductance, Capacitance and Resistance (**LCR**) can be represented as such:


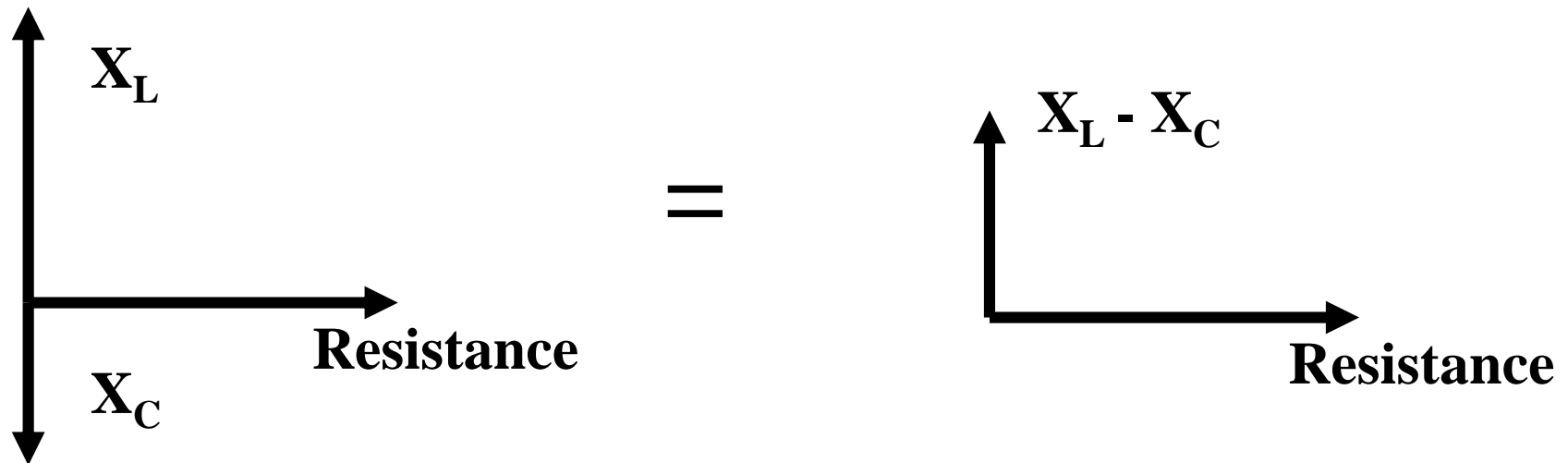
# Inductive vs Capacitive Reactance

- Inductive and Capacitive Reactance **cannot** be **added together** to give an overall reactance.
- In fact, they tend to **cancel each other out**.




# Impedance

- When a circuit contains both **resistance** and **reactance**, the **opposition to the flow of AC** is called **Impedance**, abbreviated **Z**.
- Because **Resistance** and **Reactance** are **not in phase** however, we must use **vectors** to determine the **Impedance**, even if Inductive and Capacitive Reactance have partly **cancelled each other out**.
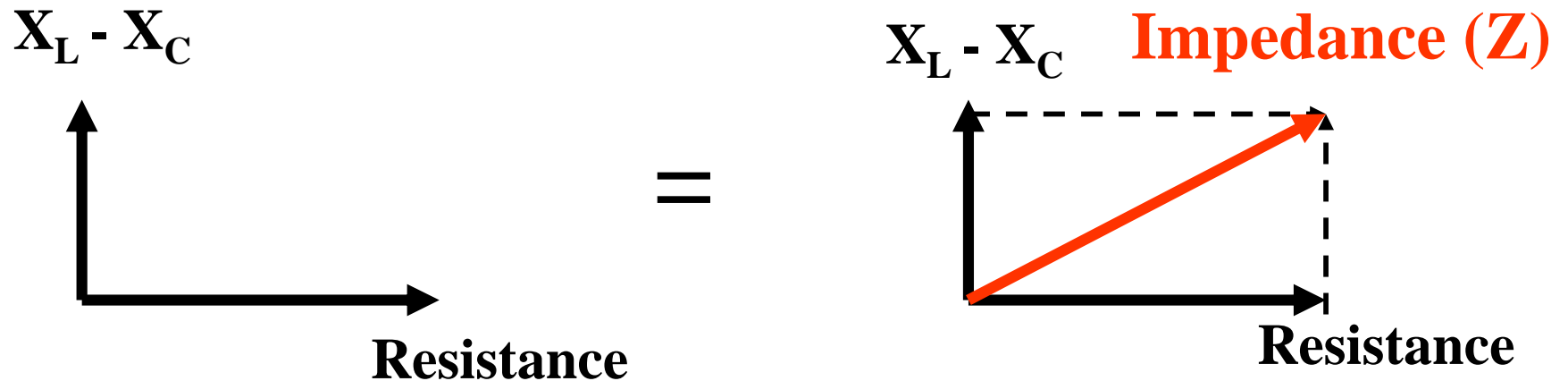
# Vector Addition

Through the use of **vector addition**, the Impedance can be determined...



# LCR Circuit Impedance Formula

- Rather than plot vectors every time we need to determine impedance however, we can use a **formula**:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

- Note that because the difference between  $X_L$  and  $X_C$  is squared, **it doesn't matter** what term is subtracted from what – you can use  $X_C - X_L$  if that is more convenient.

# LCR Circuit Impedance Example

- Resistance = 120 Ohms
- $X_L = 40$  Ohms
- $X_C = 130$  Ohms
  
- $Z = \text{Sqr Root} [ R^2 + (X_C - X_L)^2 ]$

# LCR Circuit Impedance Example

- Resistance = 120 Ohms
- $X_L = 40$  Ohms
- $X_C = 130$  Ohms
  
- $Z = \text{Sqr Root} [ R^2 + (X_C - X_L)^2 ]$   
= Sqr Root [  $(120)^2 + (130 - 40)^2$  ]

# LCR Circuit Impedance Example

- Resistance = 120 Ohms
- $X_L = 40$  Ohms
- $X_C = 130$  Ohms
  
- $Z = \text{Sqr Root} [ R^2 + (X_C - X_L)^2 ]$   
= Sqr Root [  $(120)^2 + (130 - 40)^2$  ]  
= Sqr Root [ 14400 + 8100 ]




# LCR Circuit Impedance Example

- Resistance = 120 Ohms
- $X_L = 40$  Ohms
- $X_C = 130$  Ohms
  
- $Z = \text{Sqr Root} [ R^2 + (X_C - X_L)^2 ]$   
= Sqr Root [  $(120)^2 + (130 - 40)^2$  ]  
= Sqr Root [ 14400 + 8100 ]  
= Sqr Root [ 22500 ]


# LCR Circuit Impedance Example

- Resistance = 120 Ohms
- $X_L = 40$  Ohms
- $X_C = 130$  Ohms
  
- $Z = \text{Sqr Root} [ R^2 + (X_C - X_L)^2 ]$   
= Sqr Root [  $(120)^2 + (130 - 40)^2$  ]  
= Sqr Root [ 14400 + 8100 ]  
= Sqr Root [ 22500 ]  
= 150 Ohms


# LCR Circuit Impedance Example

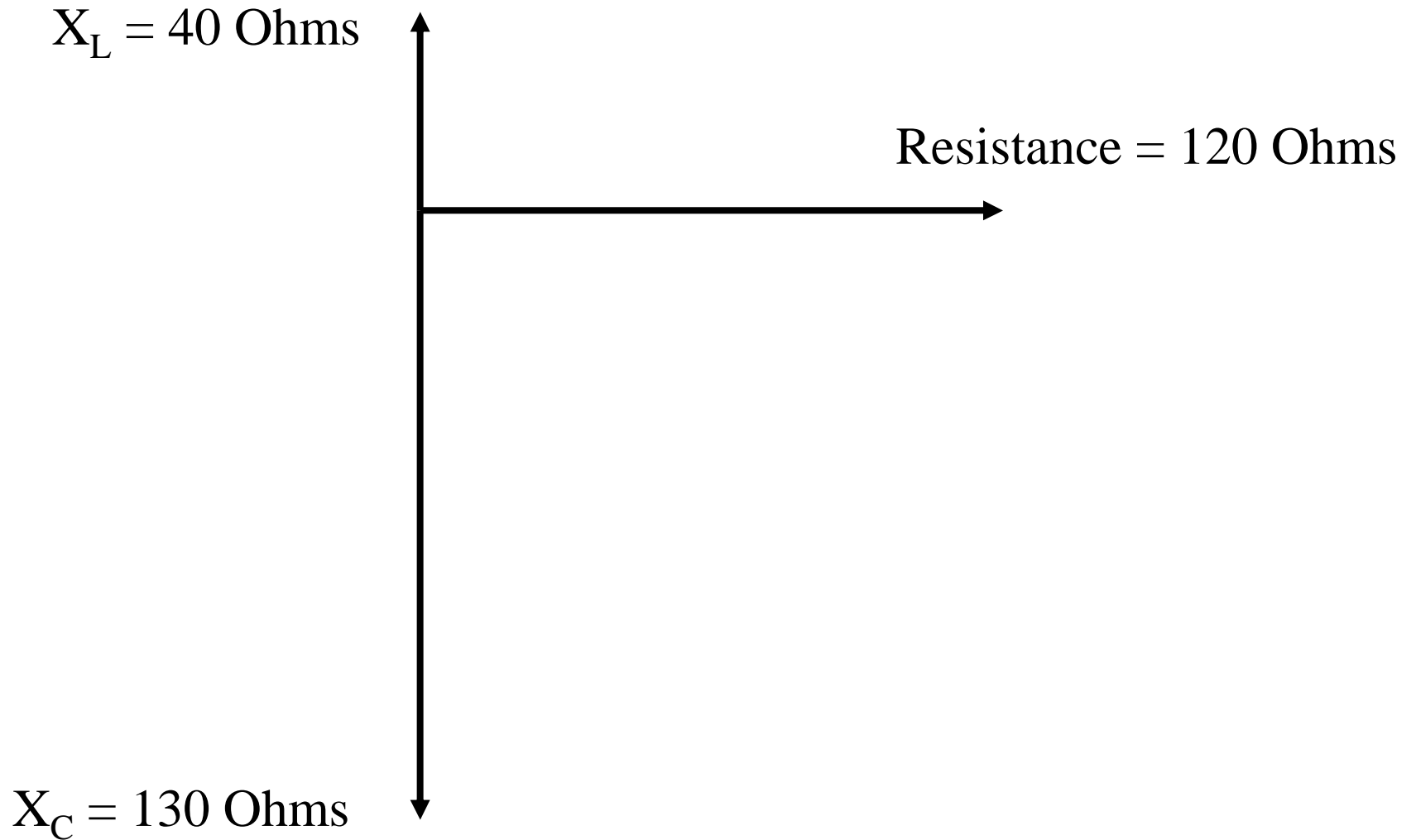


# LCR Circuit Impedance Example

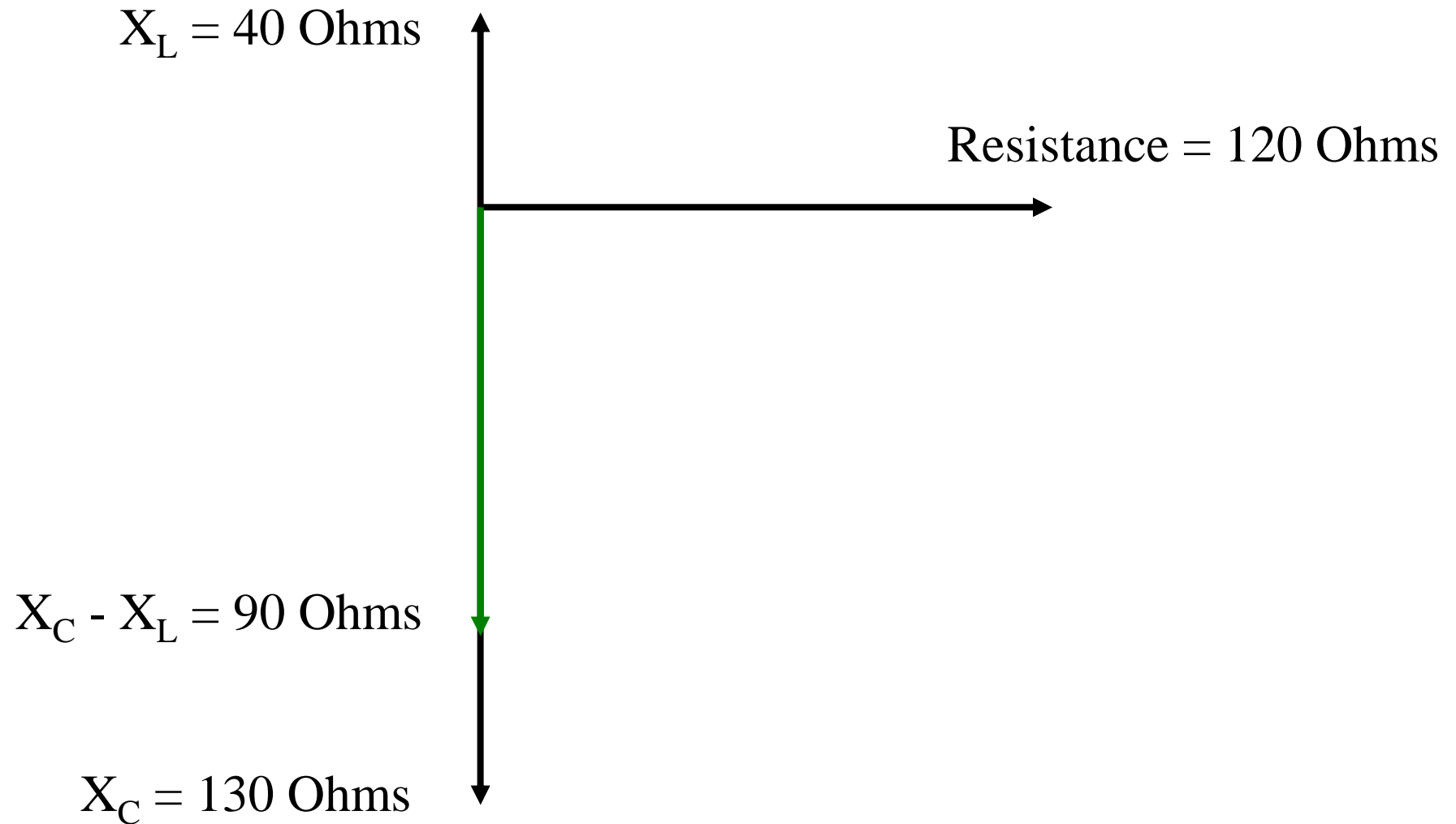

# LCR Circuit Impedance Example

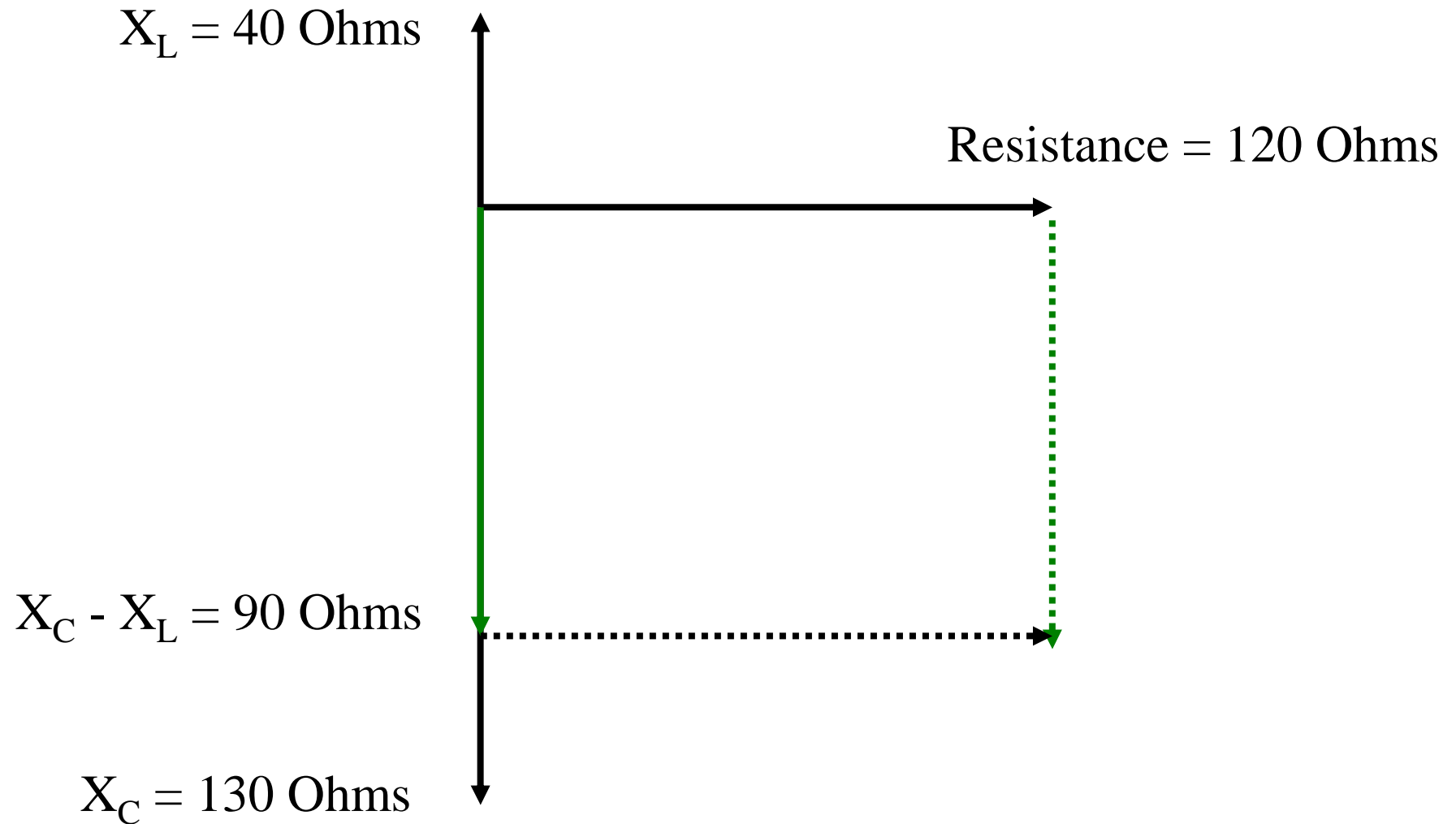

# LCR Circuit Impedance Example

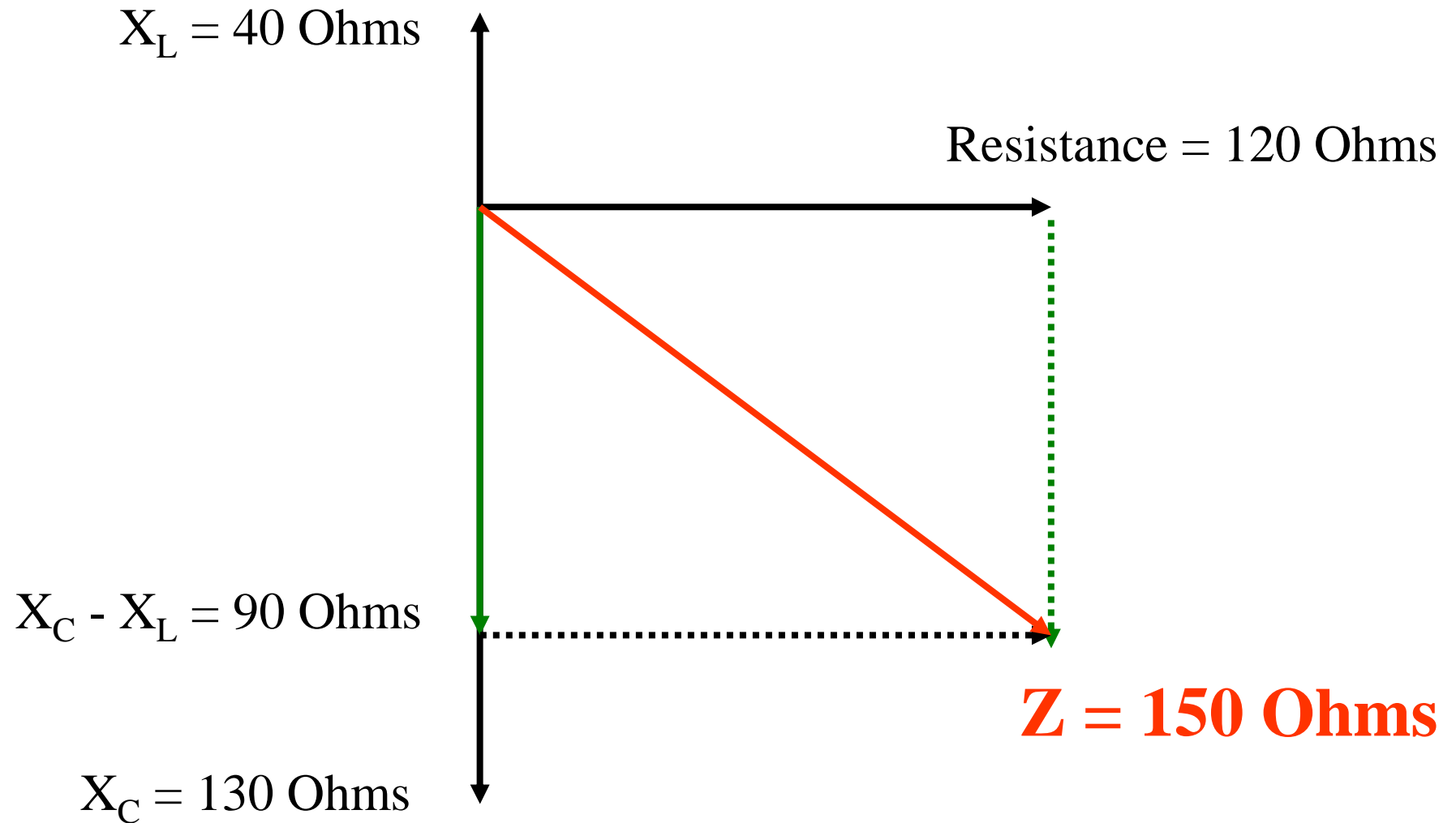

# Impedance Matching

- Many electronic devices and circuits (speakers, microphones, antennas, transmission lines, amplifiers etc.) have their own **characteristic impedance**.
- When interconnecting these devices and circuits, **maximum power transfer** will take place if the various **impedances are matched**.

# Matching with Transformers

- **Transformers** are often used to **match impedances** which are primarily **resistive**.
- This is especially true for **antenna and transmission line systems**.
- Take the matching transformer (**Balun – BALanced to UNbalanced**) used to match 300 Ohms to 75 Ohms in TV systems.



# 300 – 75 Ohm Balun

- These **matching transformers** are widely used for TV systems, and consist of a **small ferrite core with two windings**.
- In addition to the **impedance transformation**, it also converts between a **balanced** system and an **unbalanced** system.



# Number of Turns

- Different impedances can be matched quite easily by adjusting the number of turns using the following formula:

$$\mathbf{Z_S / Z_P = N_S^2 / N_P^2}$$

Or...

$$\mathbf{N_S / N_P = \sqrt{Z_S / Z_P}}$$

# Number of Turns - Example

- $Z_S = 300$  Ohms,  $Z_P = 75$  Ohms

$$N_S / N_P = \sqrt{Z_S / Z_P}$$


$$N_S / N_P = \sqrt{300 / 75} = \sqrt{4} = 2$$

- The **turns ratio** is 2:1 ie: for **every turn** on the **primary** winding, there are **two** on the **secondary** winding.
- The actual number of turns depends on the core material.

# Resonance

- In electronic circuits, a special condition exists when **Inductive** and **Capacitive Reactance** are **equal** to each other ( $X_L = X_C$ ).
- When that happens in Series LCR circuits,  $X_L$  and  $X_C$  **cancel** each other out, leaving only Resistance to oppose the flow of AC current.
- This condition is known as **Resonance**, and occurs at **only one frequency**, known as the **Resonant Frequency** ( $F_R$ ).

# Resonant Frequency

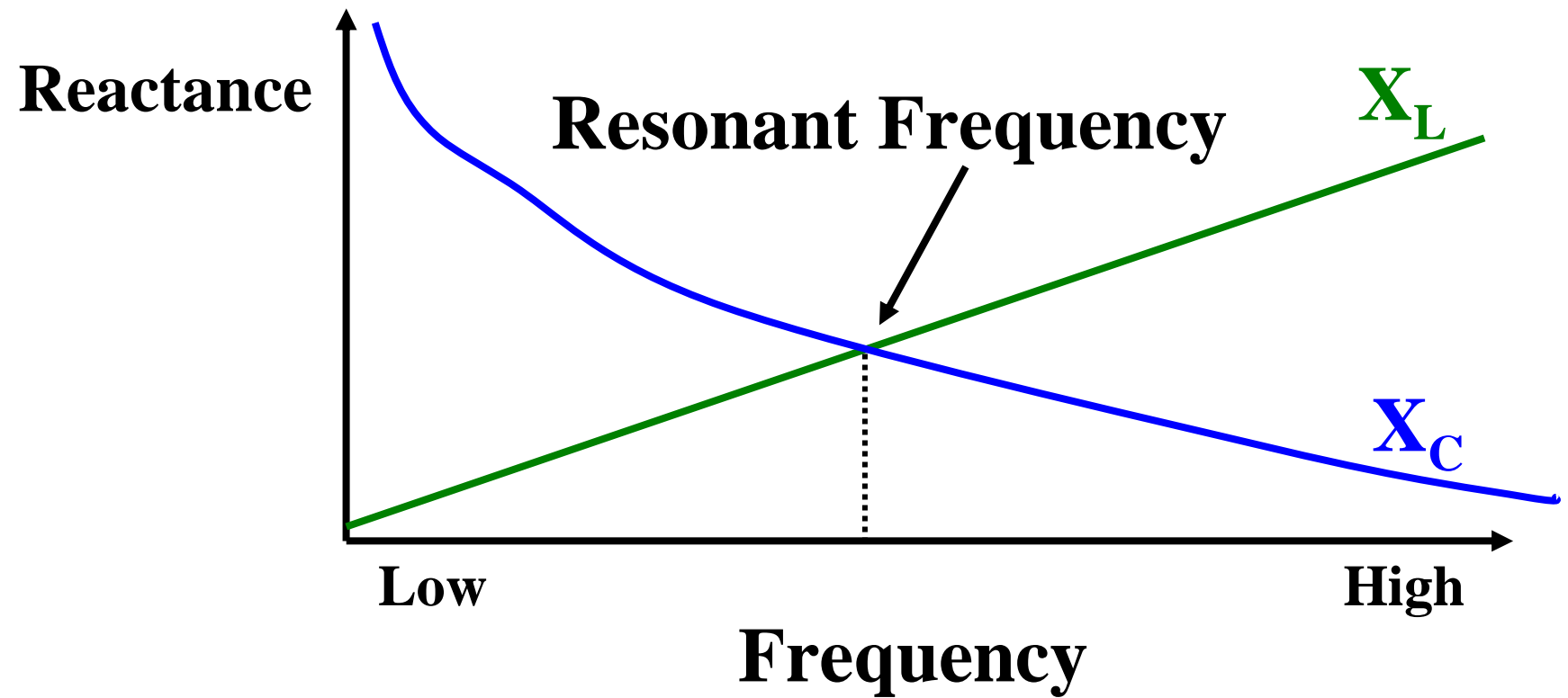

# Resonant Frequency

- At Resonance,  $X_C = X_L$  so

$$X_C = \frac{1}{2\pi f C} = X_L = 2\pi f L$$

- With a little mathematical wizardry, we can rearrange that equation to determine the **Resonant Frequency  $F_R$**  as follows...

# Resonant Frequency

$$F_R = \frac{1}{2\pi\sqrt{LC}}$$

- Where:


$F_R$  = Resonant Frequency in Hertz

$L$  = Inductance in henrys

$C$  = Capacitance in Farads

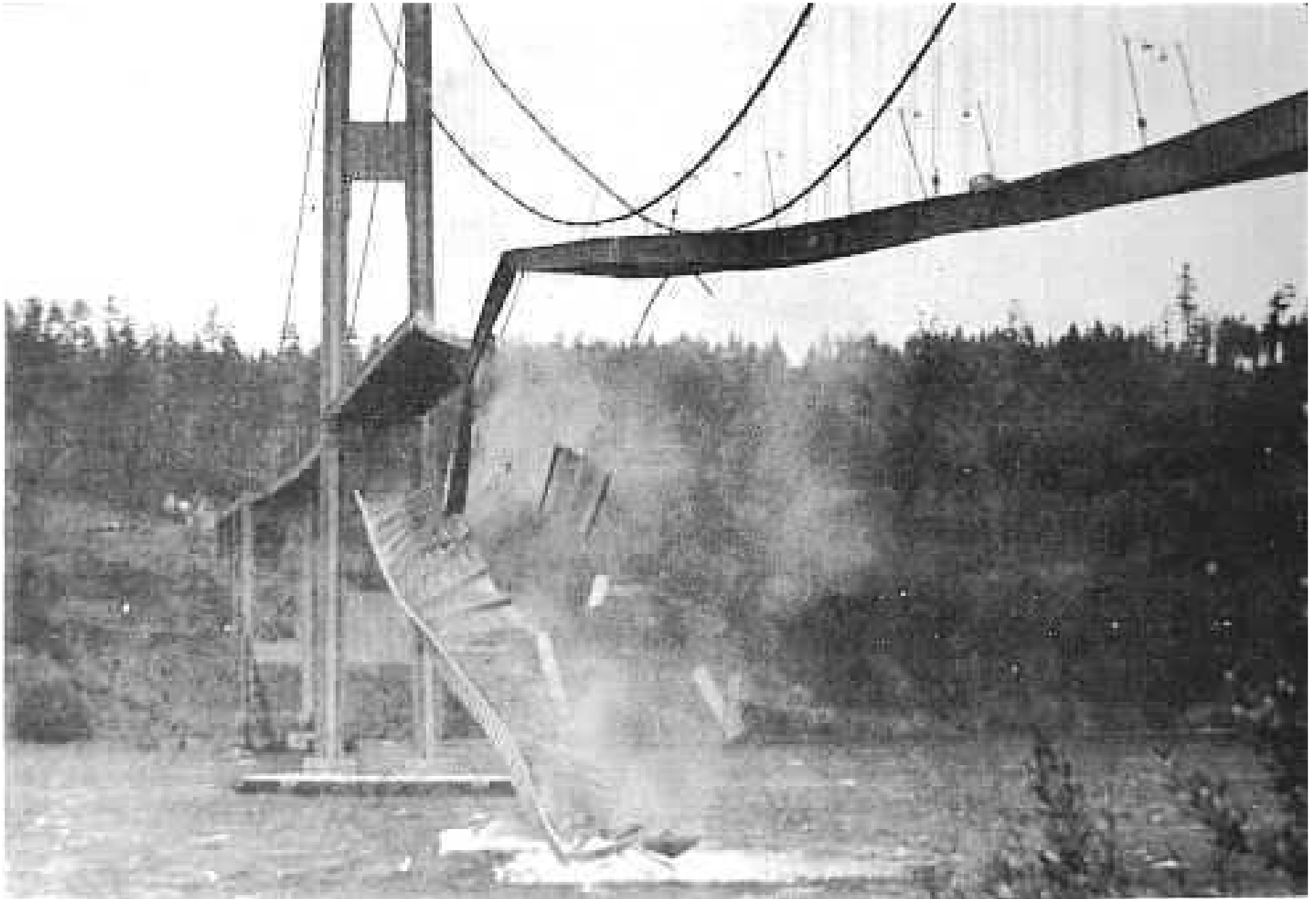**Resonance is not always a good  
thing however...**





Tacoma Narrows suspension bridge


# Tuned Circuits

- Circuits containing **Capacitors and Inductors** are often referred to as **Tuned Circuits**.
- They have **many uses** in electronics – every time you tune a radio, you are varying the **resonant frequency** of a **tuned circuit**.

# Series LCR Circuit


- When a **Series LCR** circuit is in **Resonance**, **current** in that circuit is at its **greatest** (the **Impedance** is at its **lowest**).
- There are **two ways** to achieve **Resonance** in **Series LCR** circuits:
  - **Vary the applied frequency** until we find the point where  $X_C = X_L$ .
  - Keep the frequency constant and **vary the value of the capacitance or inductance**, or both, until  $X_C = X_L$ .

# Series LCR Circuit

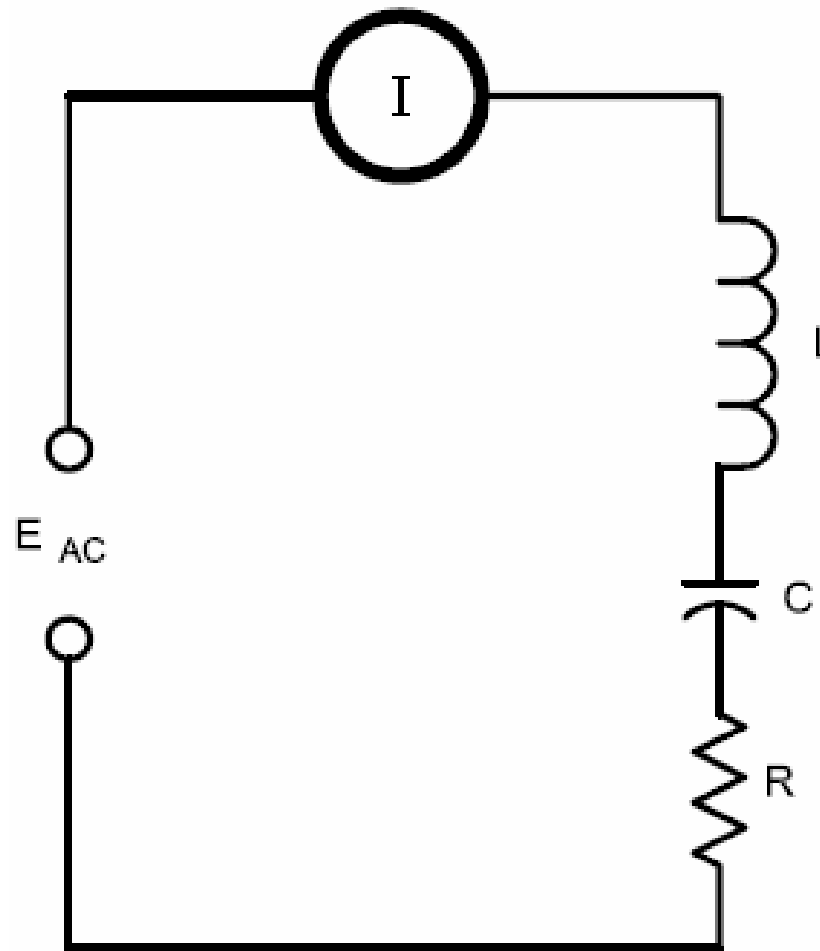



# Series LCR Circuit Impedance

L/C in Series .1H/.1uF

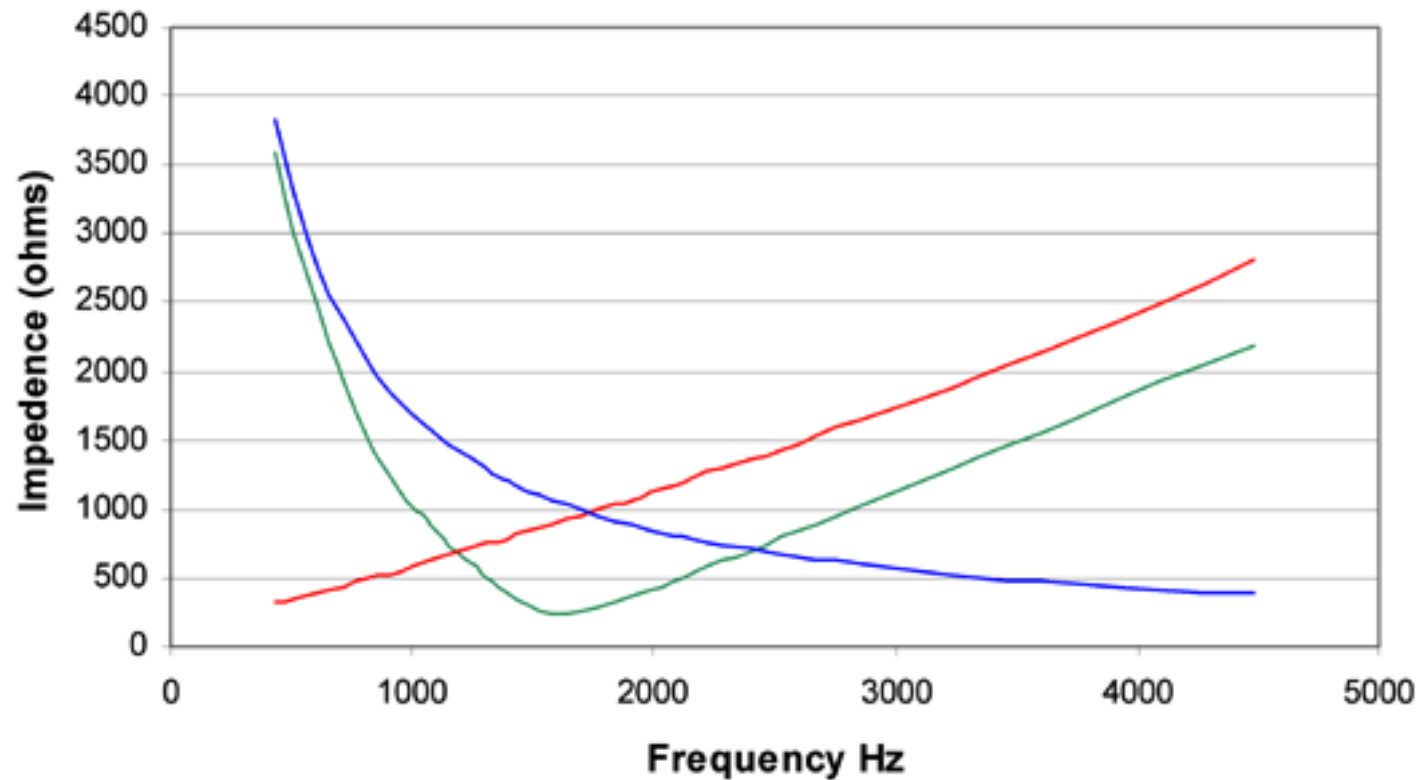


Series .1H Inductor .1uF Cap


# Varying the Frequency

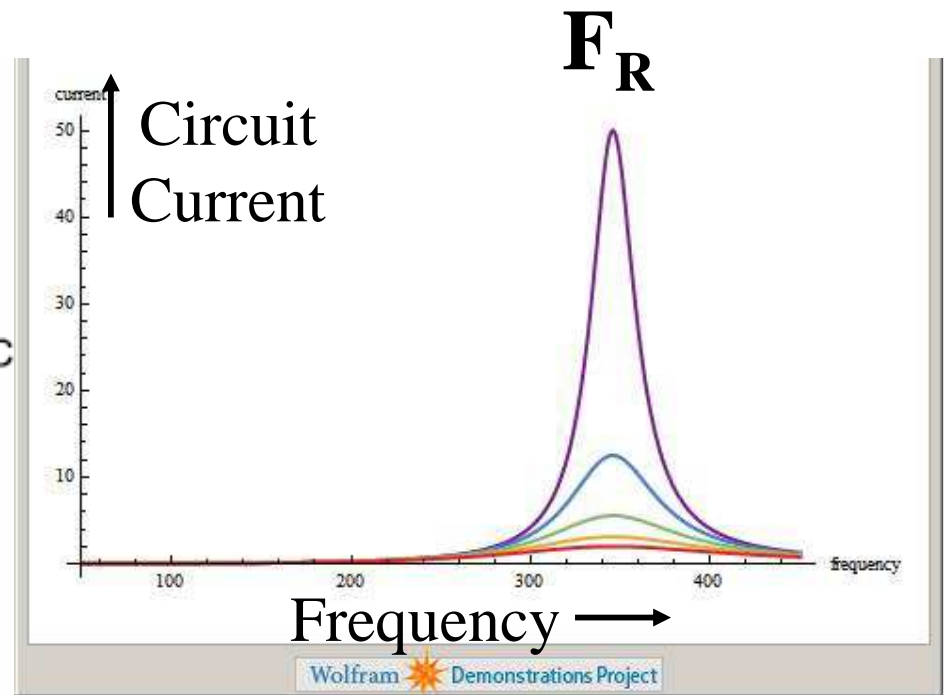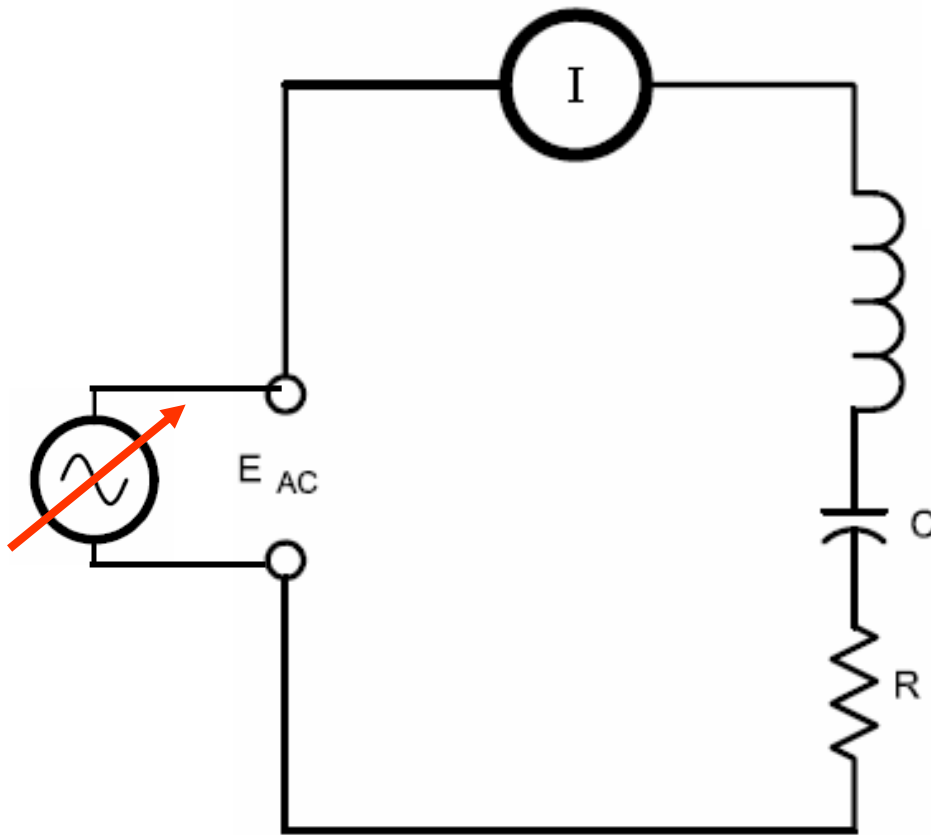

# Varying Capacitance or Inductance

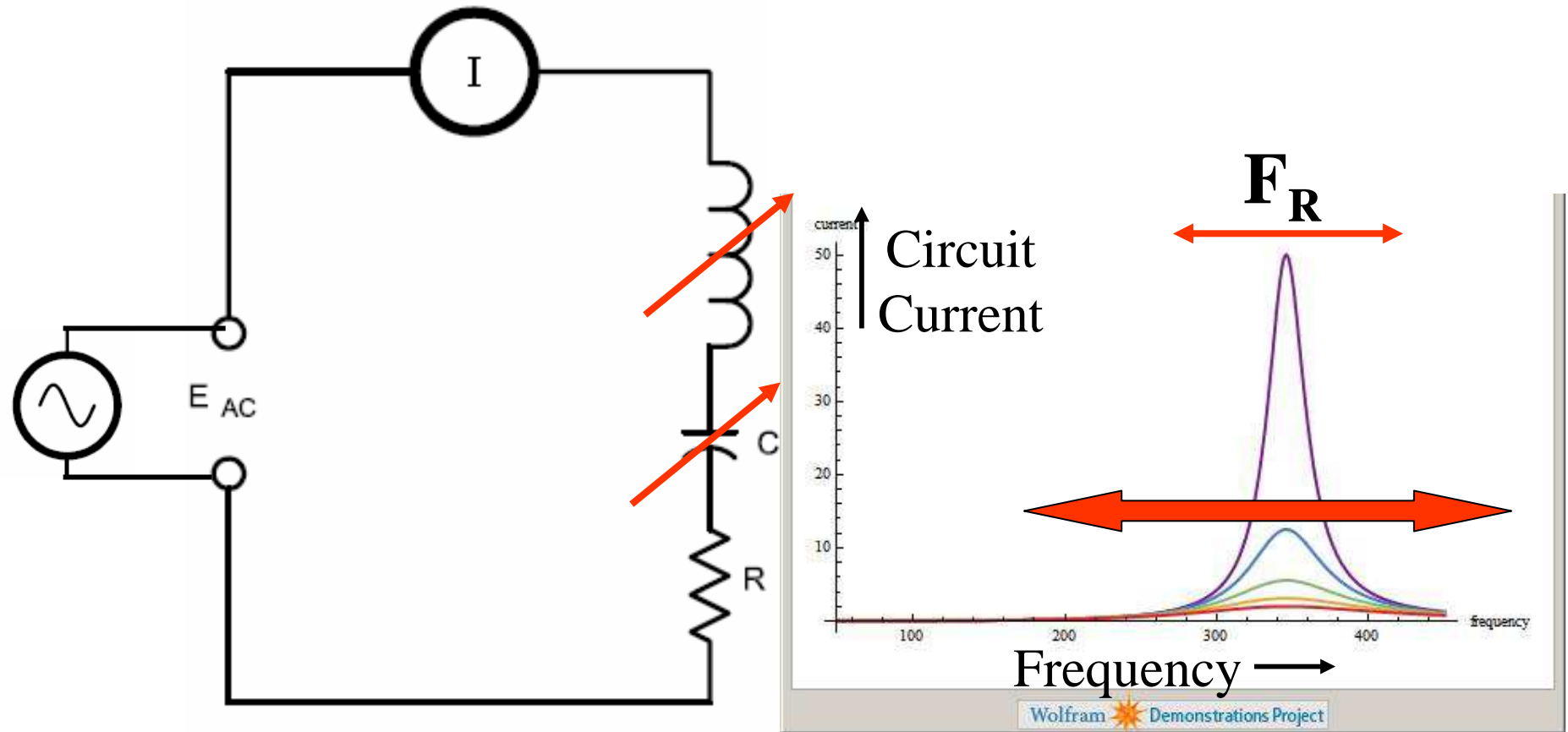

# Parallel LCR Circuits

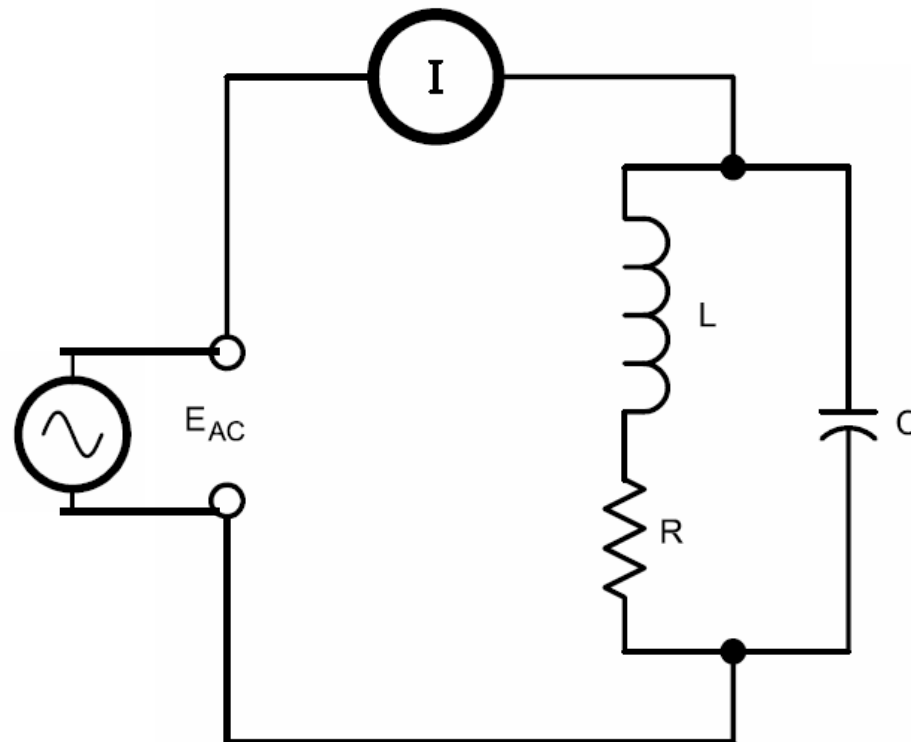




# Parallel LCR Circuits

- In a **Parallel LCR Circuit**, the **current** is **lowest at Resonance** (the **impedance** is at its **highest**).
- Parallel LCR circuits are used to **reject a specific frequency** while allowing all others to pass.


# Parallel LCR Circuit Impedance

L/C in Parallel .1H/.1uF

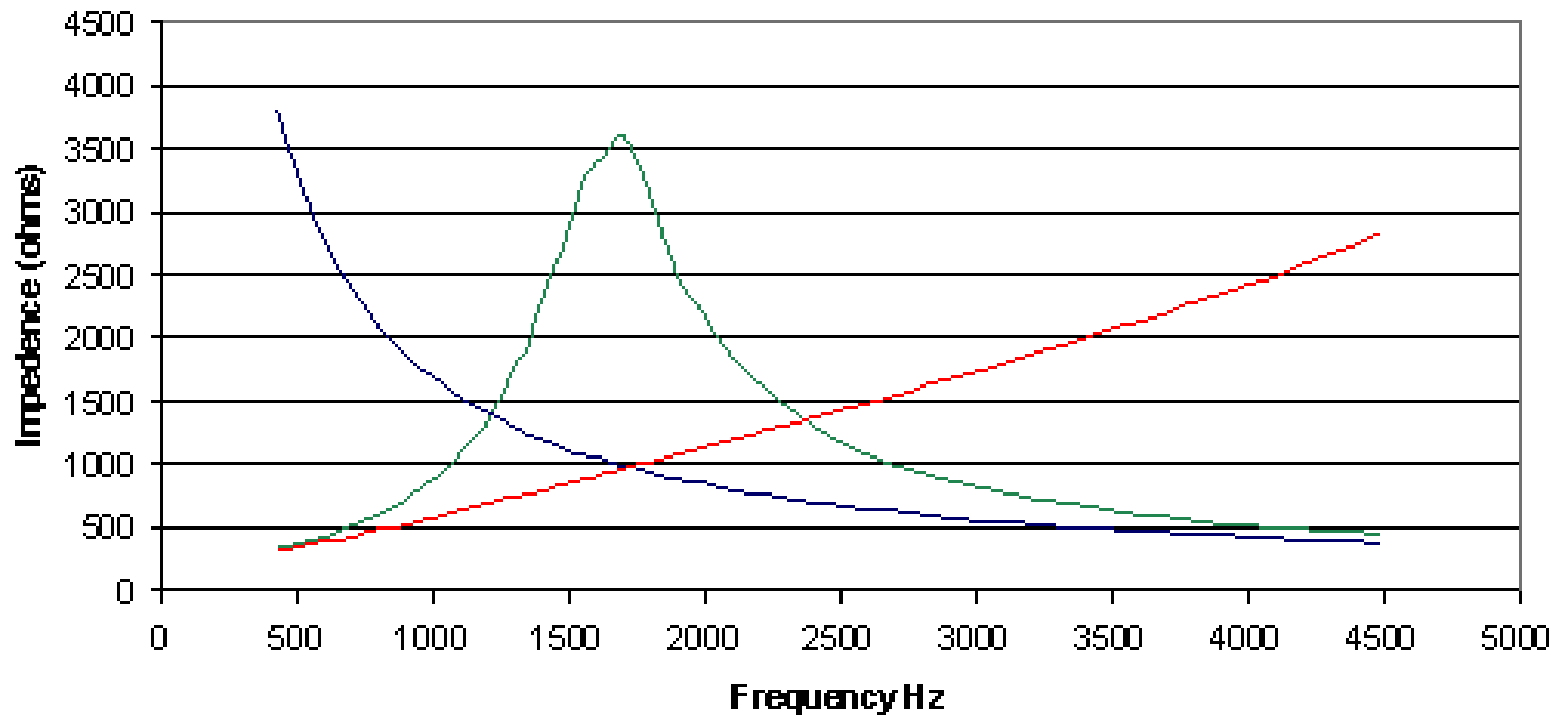

— Parallel — .1uF Cap — .1H Inductor

# Parallel LCR Circuit Current

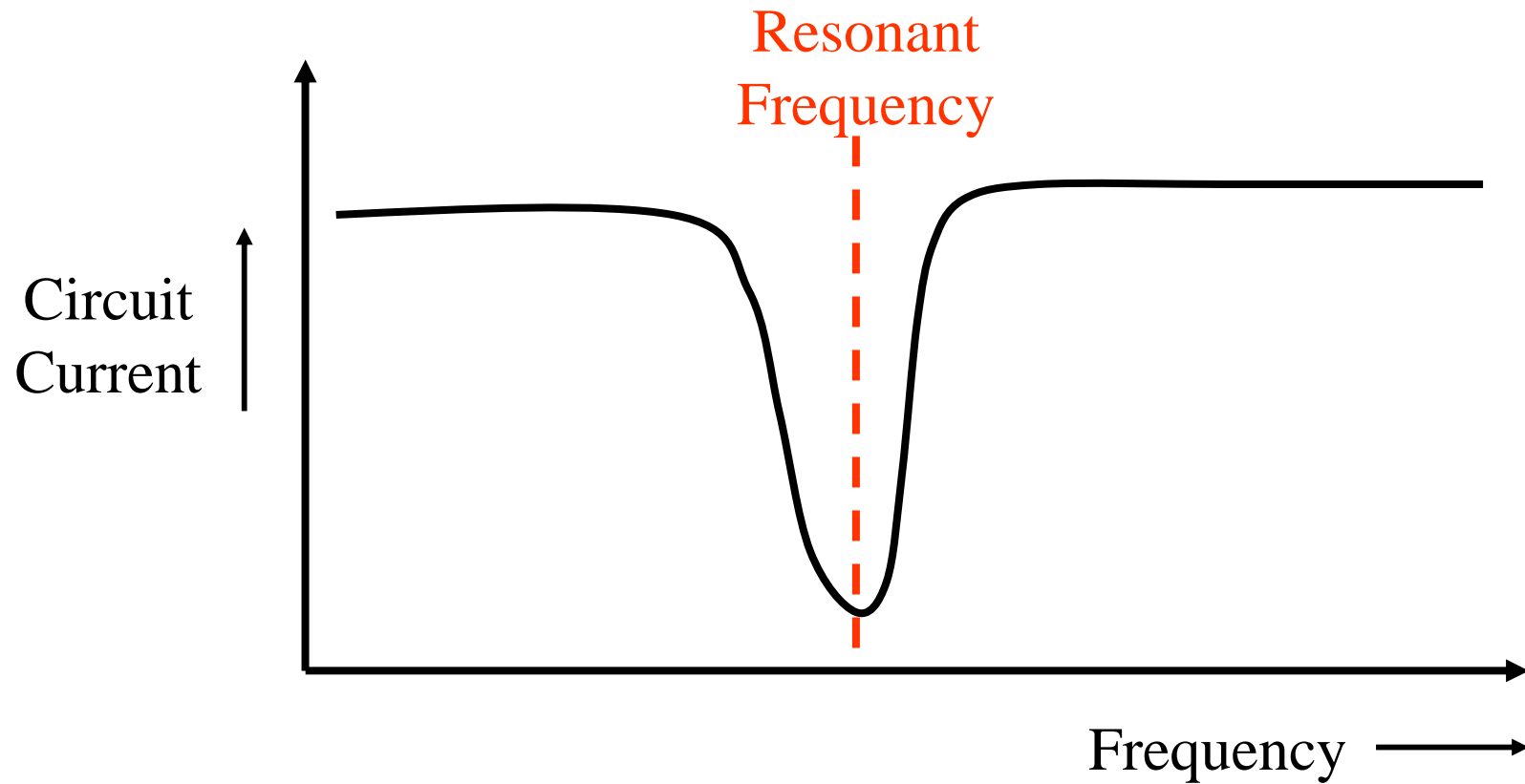


# Circuit Quality

- In a **resonant series LCR circuit**, energy is stored **alternately** in the **electric field of the capacitor**, and then the **magnetic field of the inductor**.
- This causes a **current** to flow **between them**.
- Anything that **removes energy** from this circuit **broadens the range of frequencies** affected by the circuit, but **increases the impedance** at the **resonant frequency**.


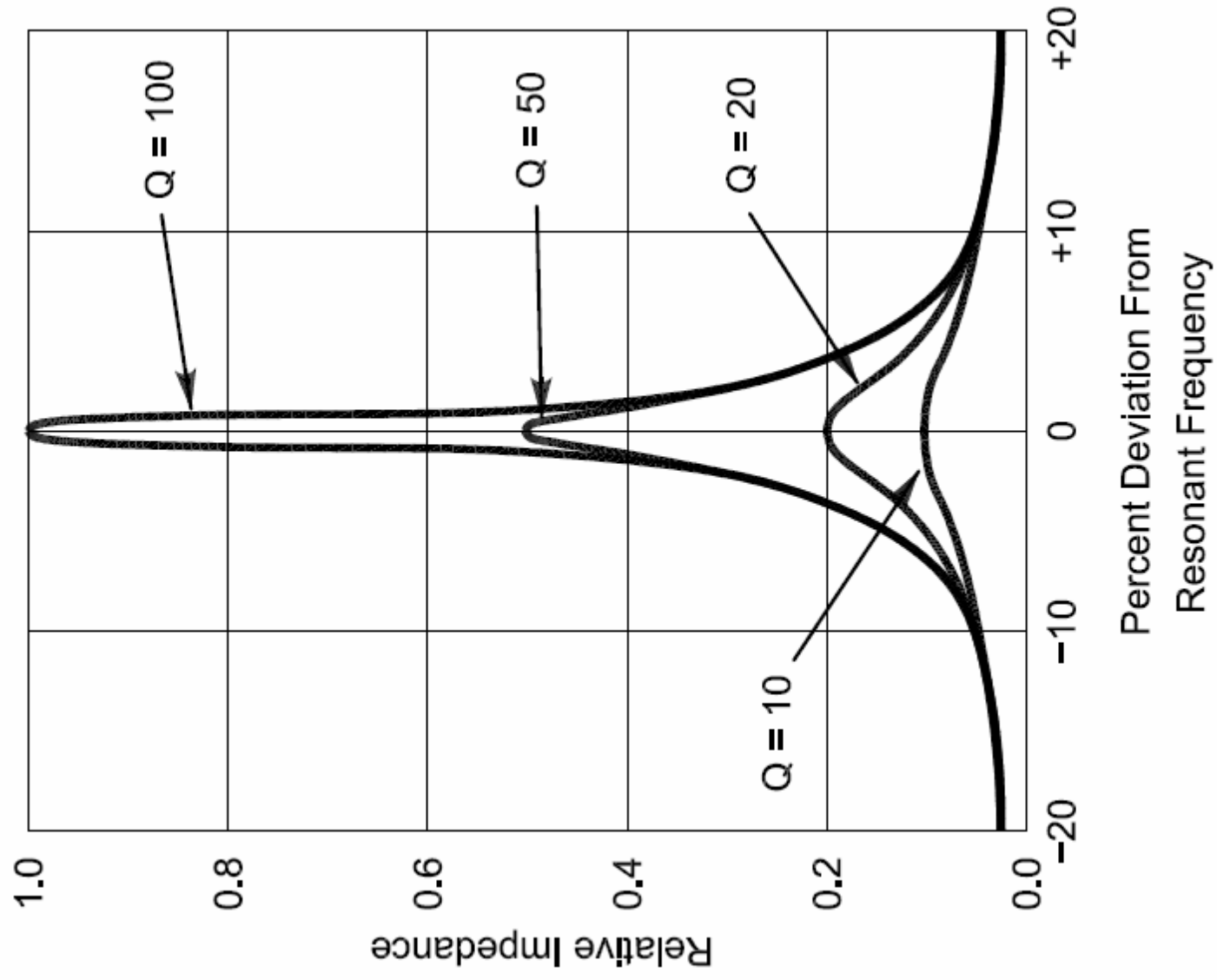
# Circuit Quality

- The “**Q**”, or **Quality** of a series LCR circuit is defined as the **ratio** of either  $X_C$  or  $X_L$  to the **resistance** in the circuit.
- **Below** resonance “**Q**” =  $X_C / R$
- **Above** resonance “**Q**” =  $X_L / R$
- At resonance  $X_C = X_L$
- A “**Q**” of **100** is **high**, while a “**Q**” of **10** is **low**.




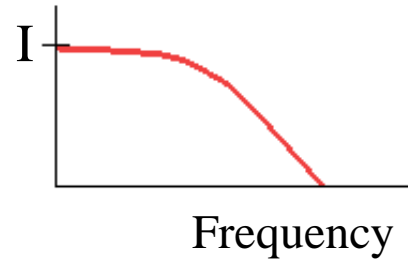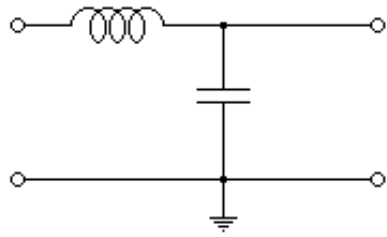
# Filters



- By the proper selection of capacitors and inductors, it is possible to design **Filters** that can **pass desired frequencies**, and **reject unwanted frequencies**.





**Low Pass Filter**

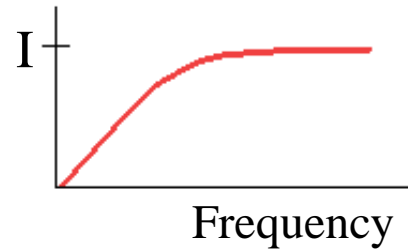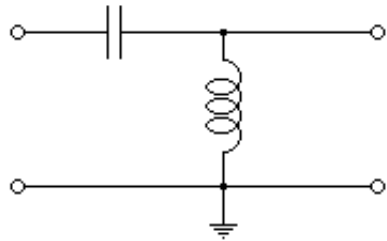

**High Pass Filter**

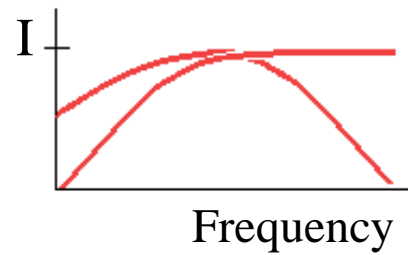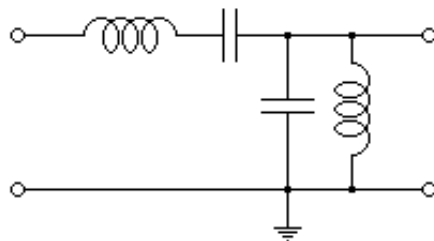


**Band Pass Filter**

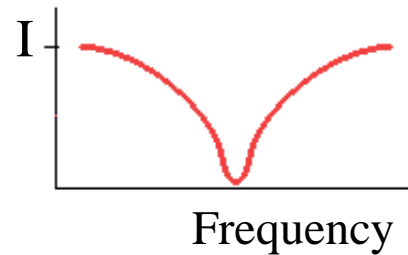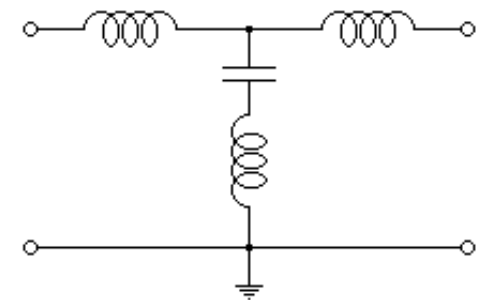


**Notch Filter**




# Crystal Radio Tuned Circuit

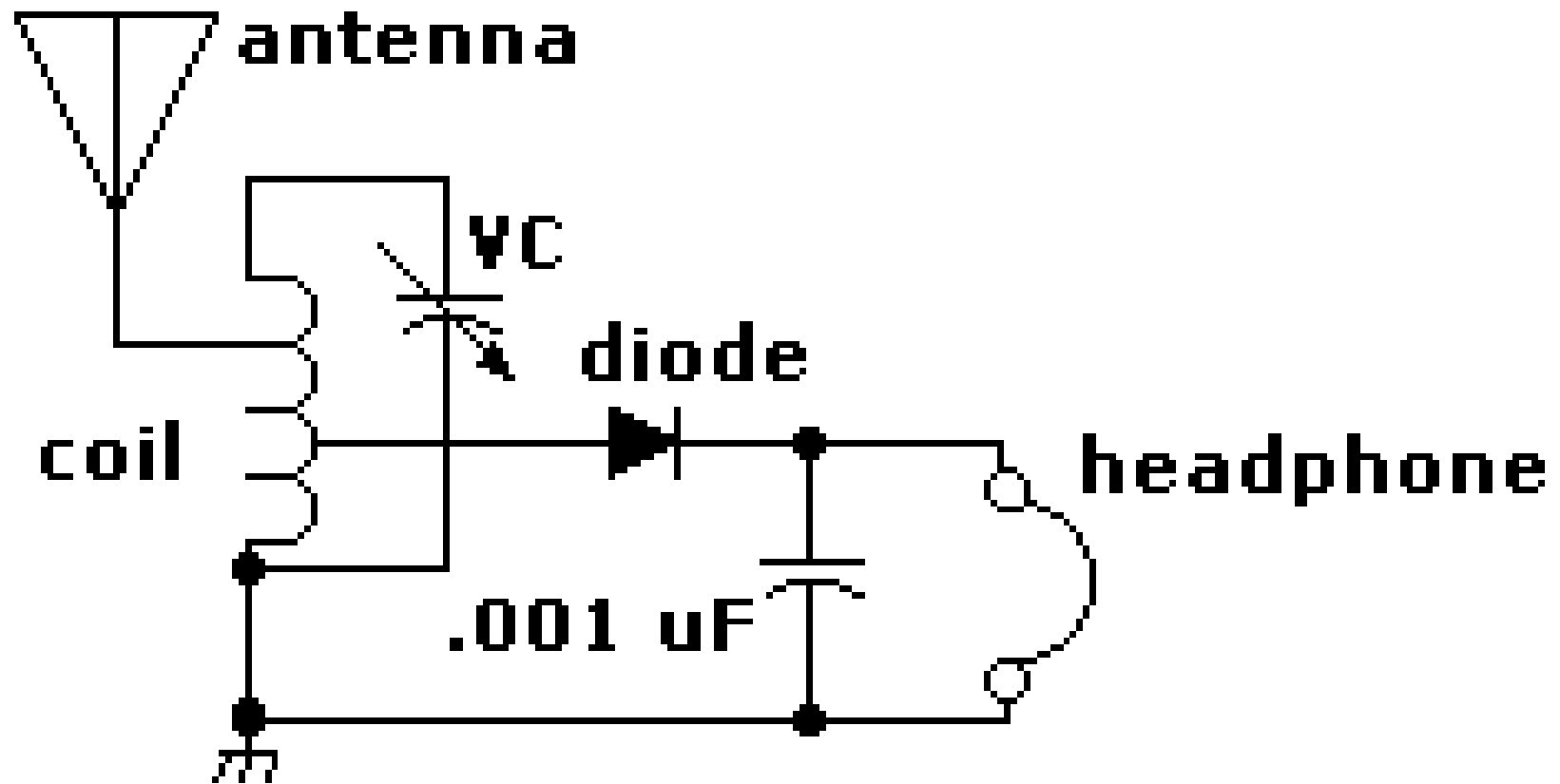

# 6 Transistor Radio

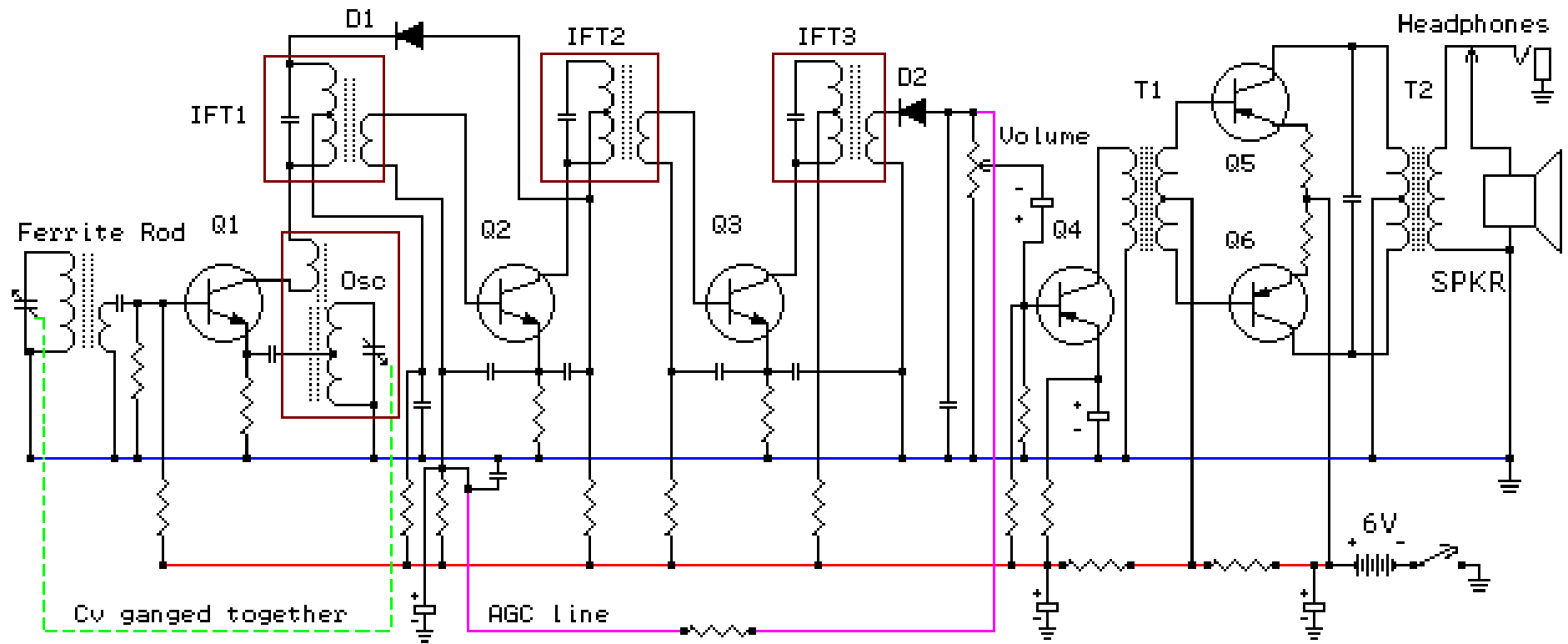


# 6 Transistor Radio

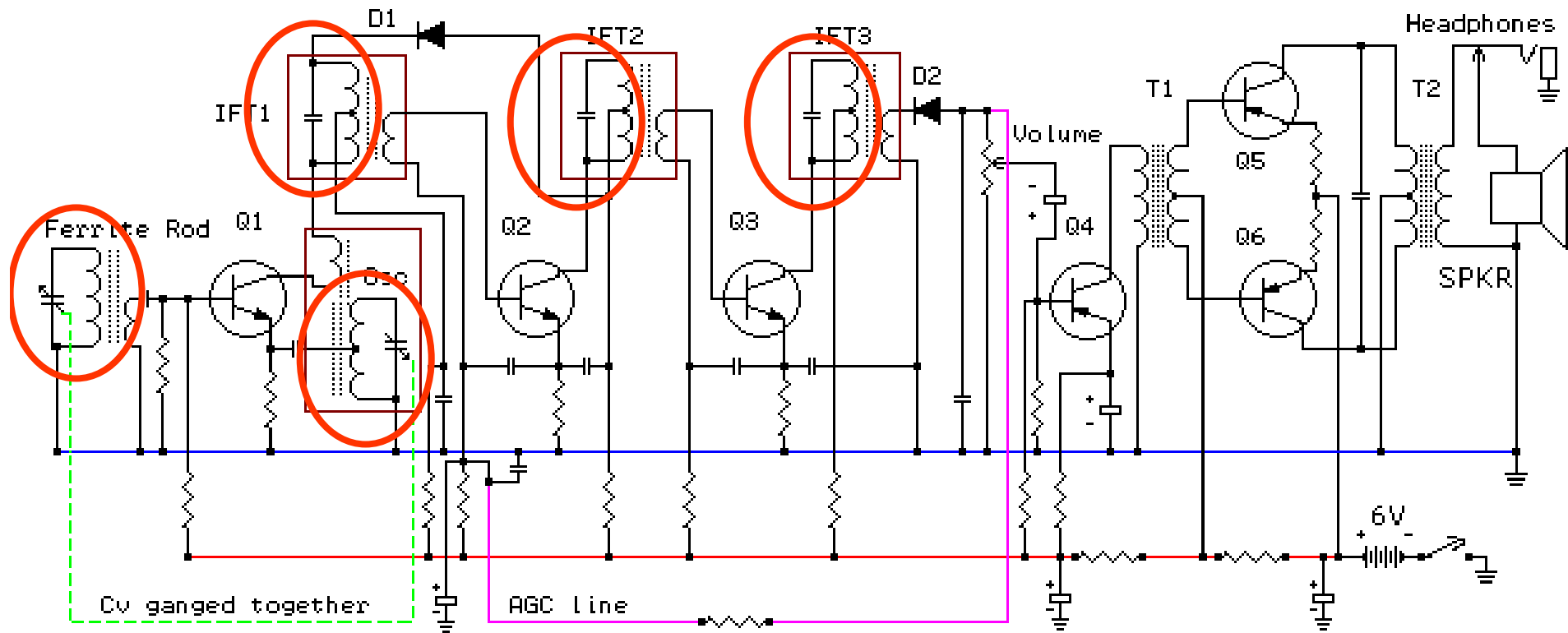

**Tuned Circuits**

# 6 Transistor Radio

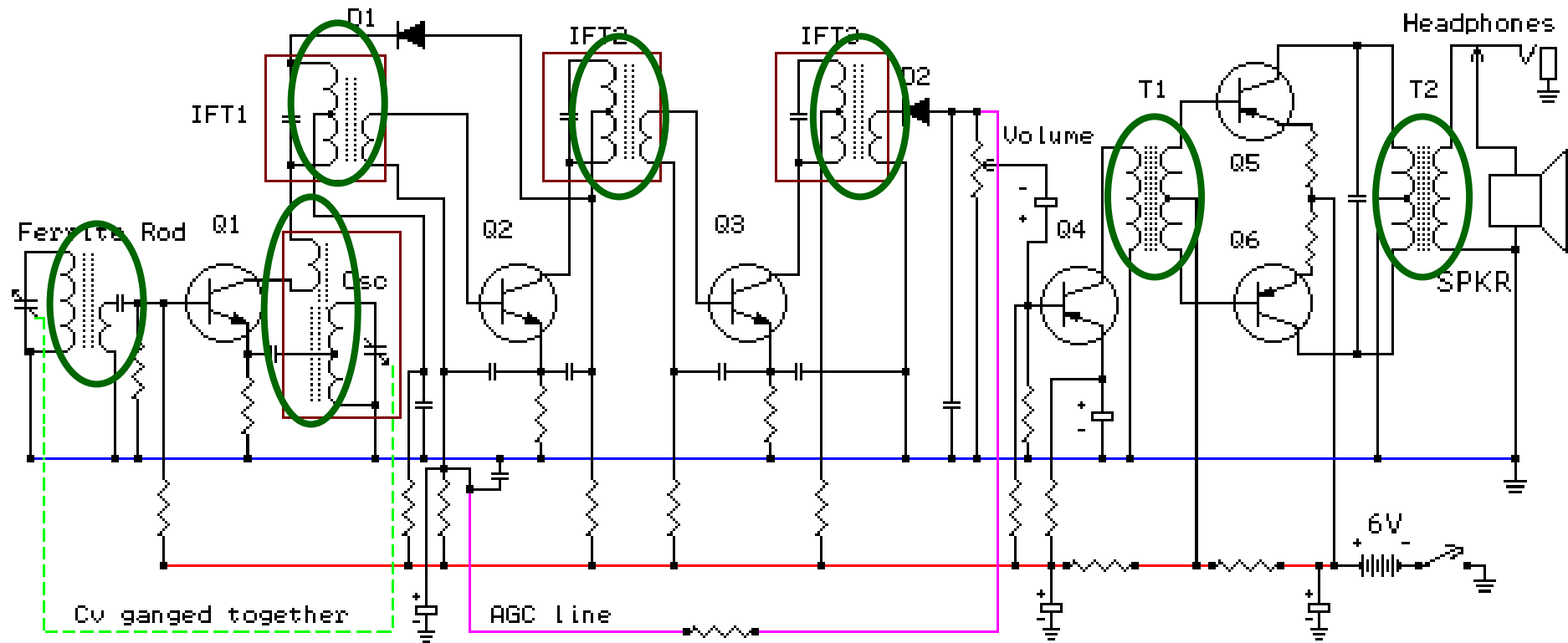



## Transformers




Questions?





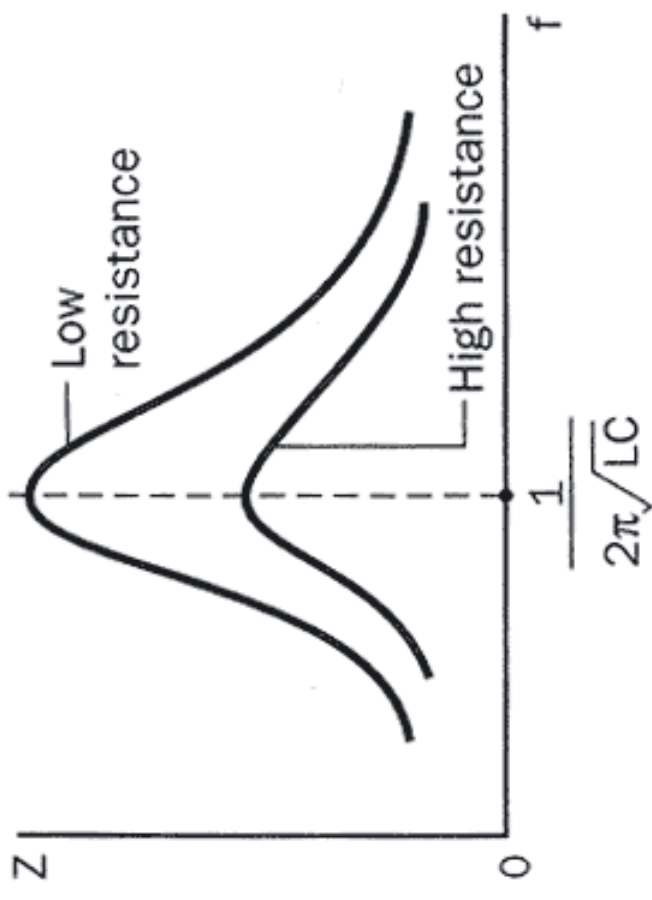

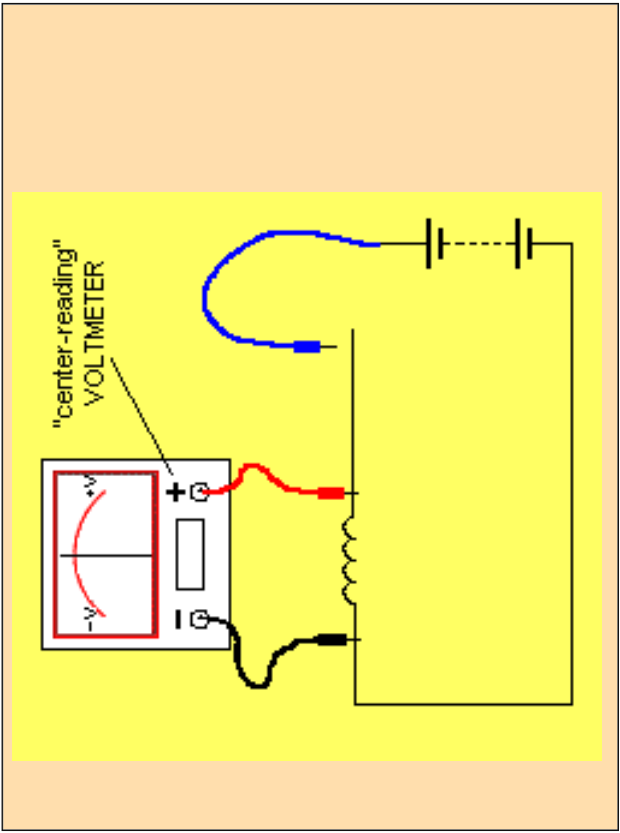




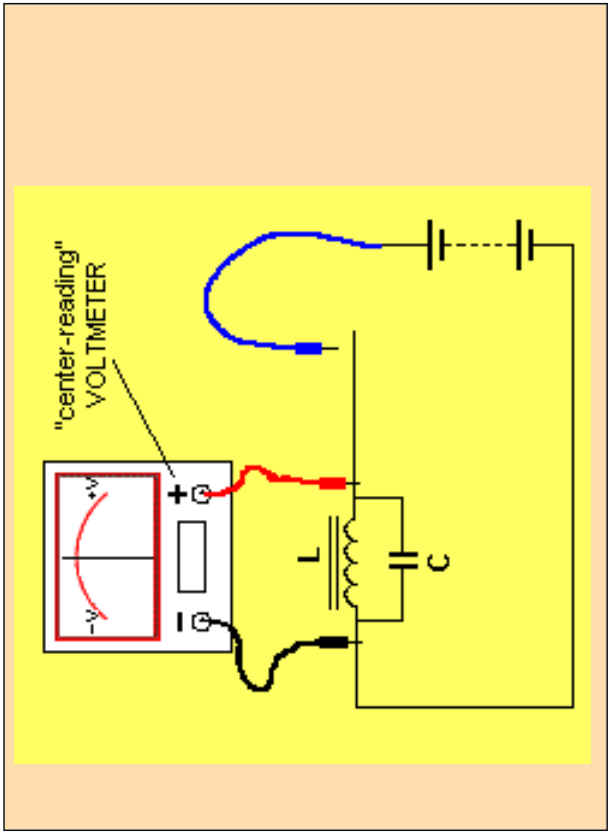

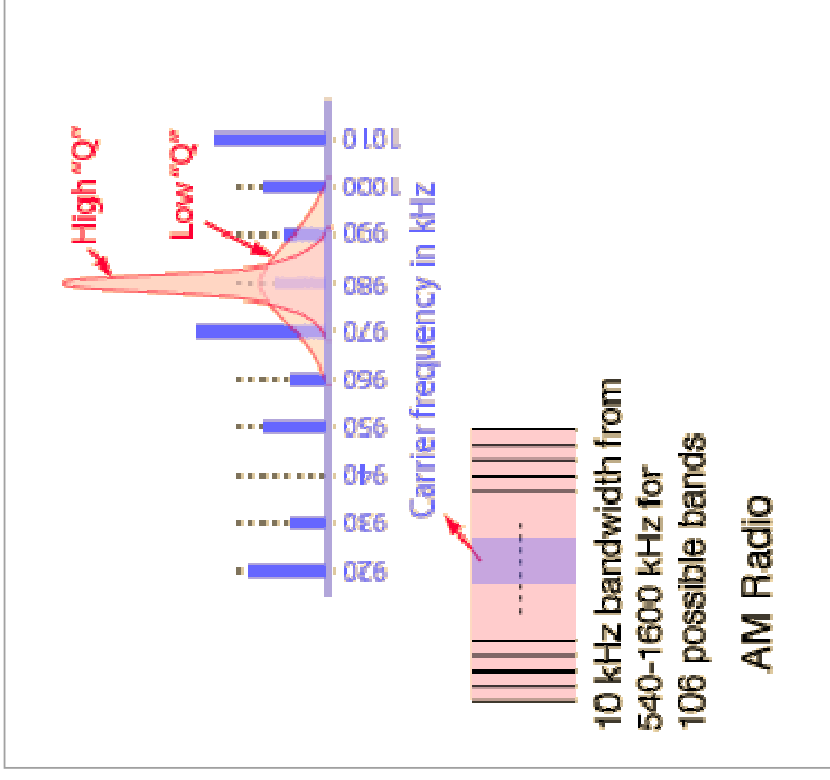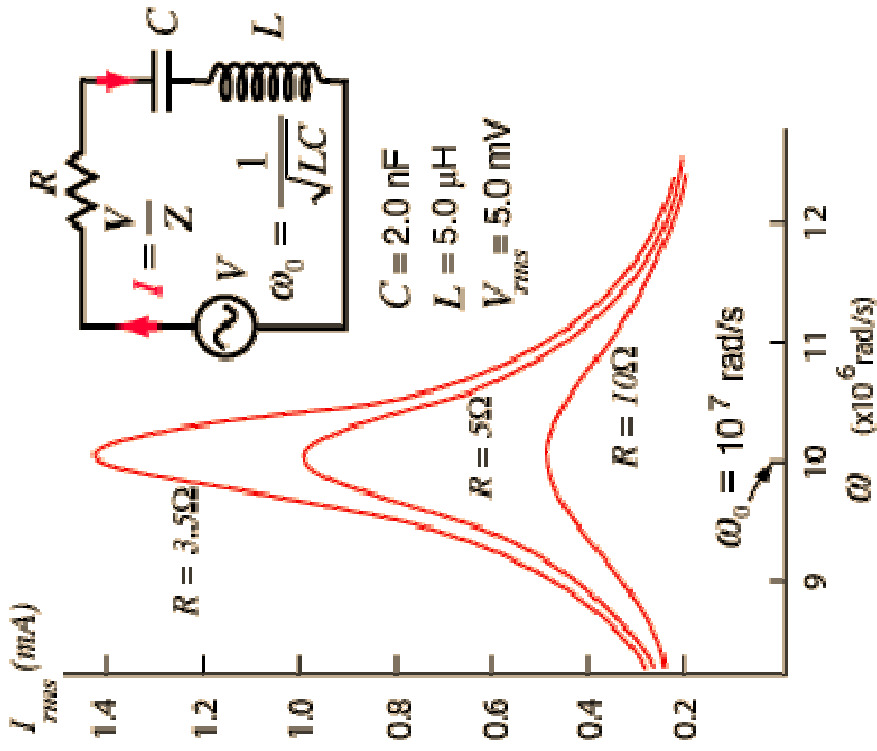


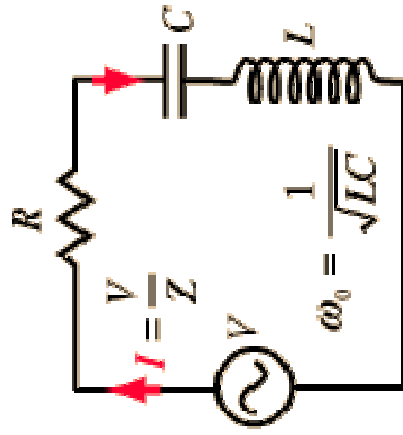Minimum impedance  
at resonant frequency




Series Resonance

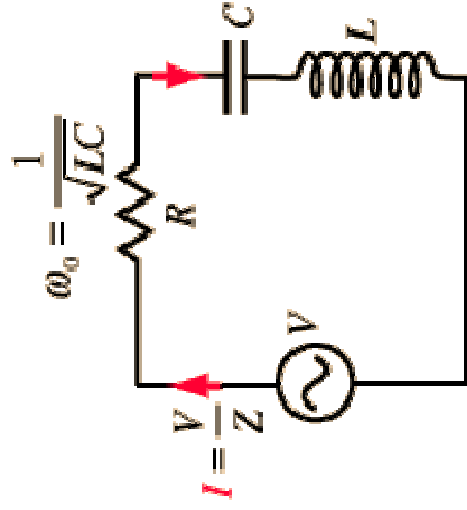Minimum impedance  
at resonant frequency





Series Resonance

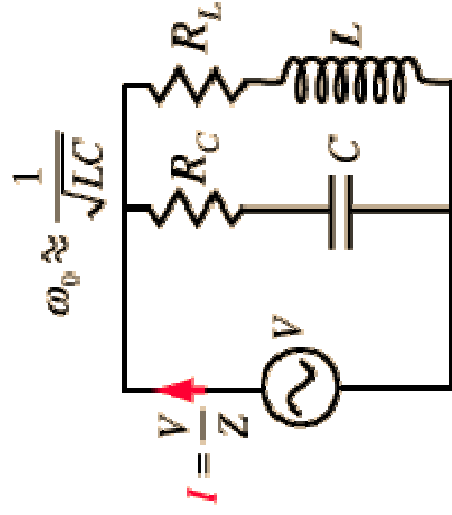
Maximum impedance  
at resonant frequency




Parallel Resonance

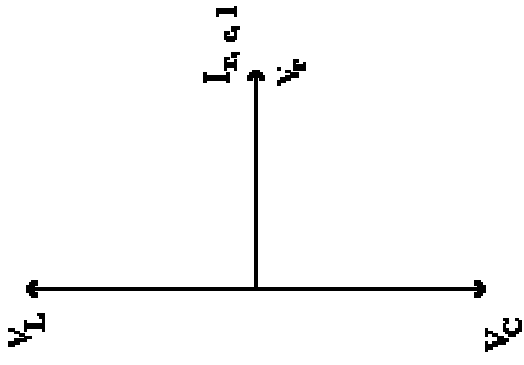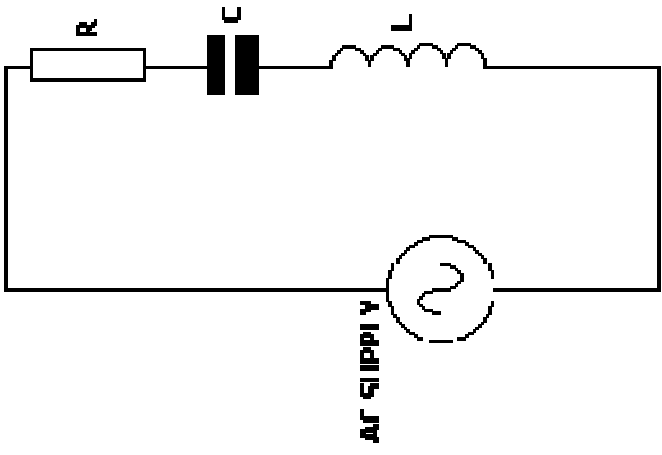


**CIVIL**

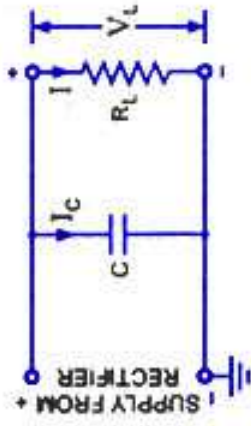


*Circuit Diagram*

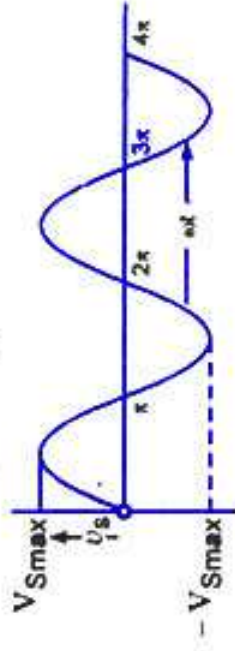


*Input Voltage Waveform To Rectifier*

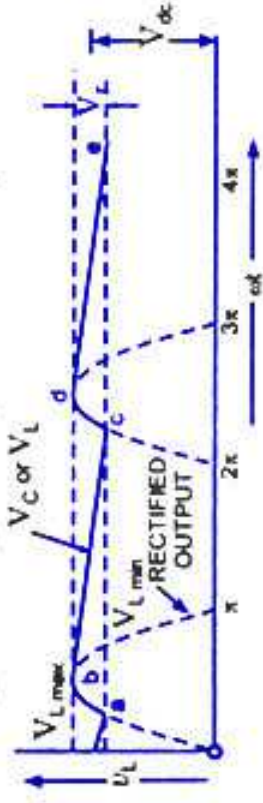

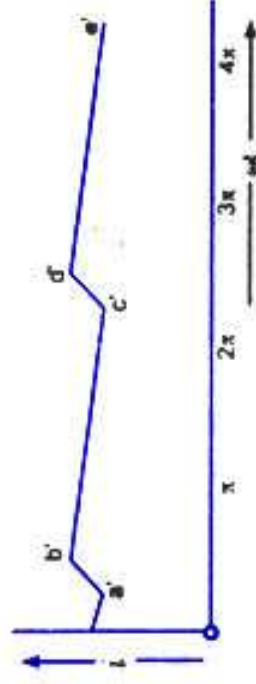*Rectified and Filtered Output Voltage Waveforms*



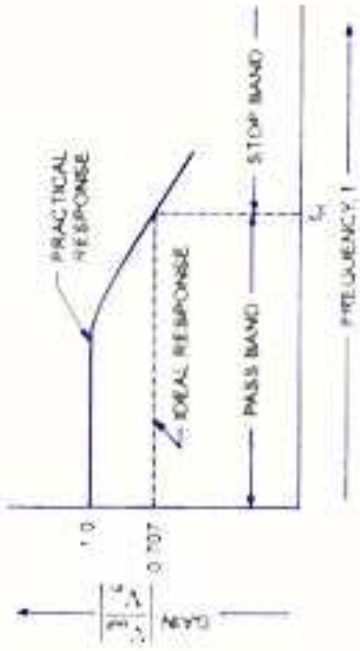
*Load Current Waveform  
Half-wave Rectifier With Shunt Capacitor Filter*




(a) Low-pass Filter



(b) High-pass Filter

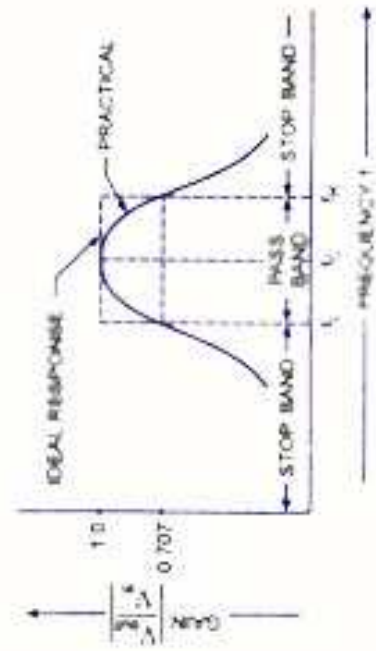

(c) Band-pass Filter

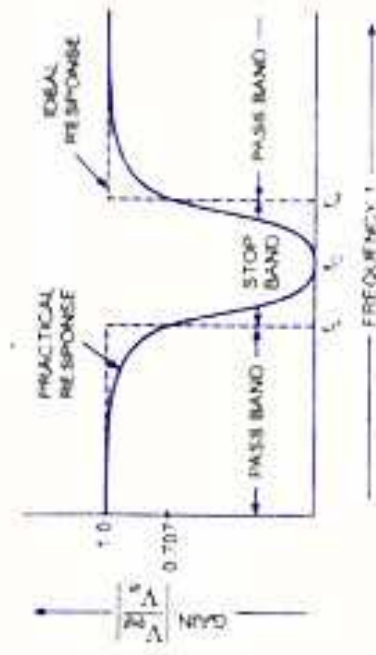

(d) Band-stop Filter



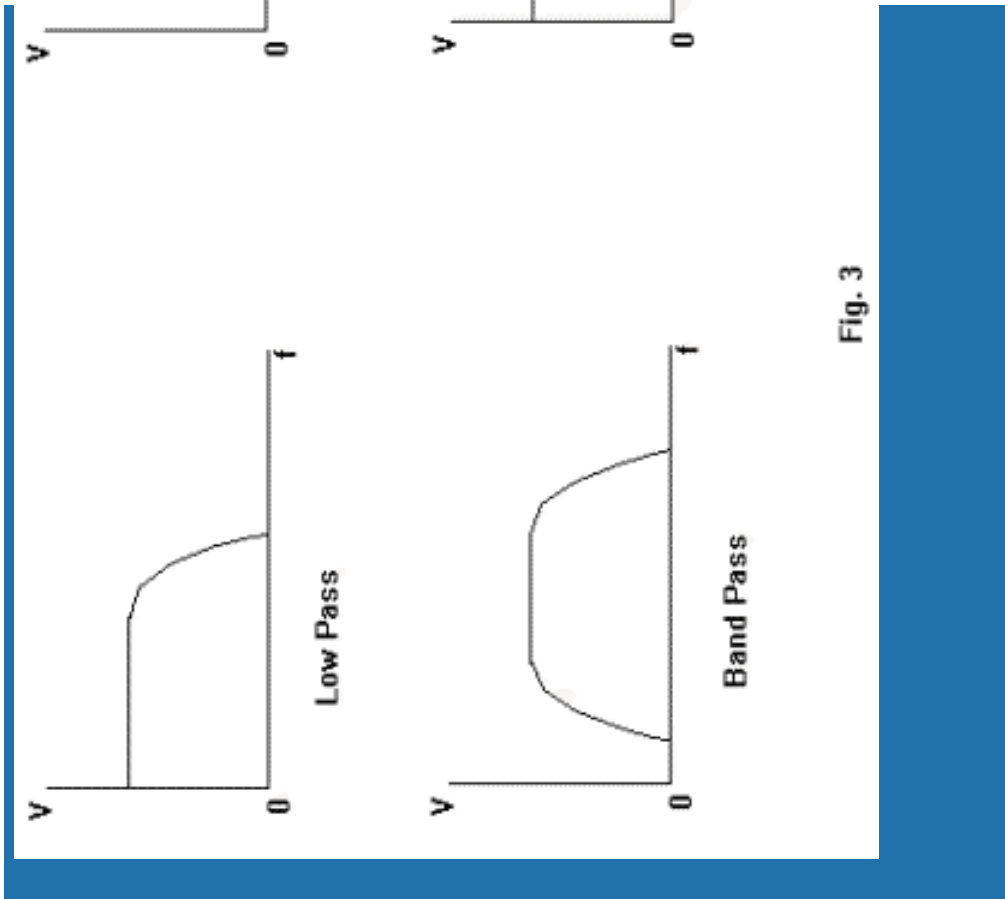


Fig. 3

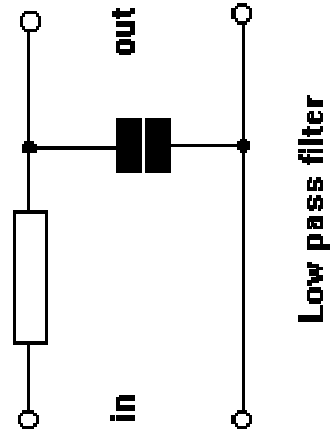

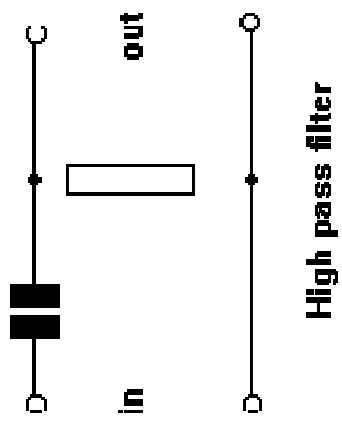

Low pass filter



High pass filter

Fig. 4