

Formulas


Ohm's Law

:

$$E = I \times R$$

$$I = E \div R$$

$$R = E \div I$$

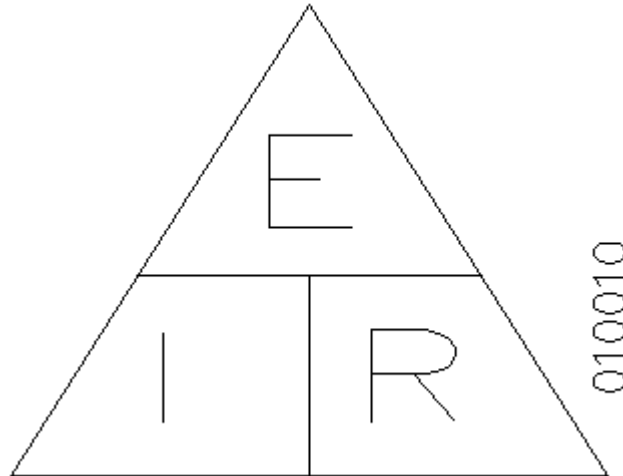

Remember:

E = voltage, in Volts
 I = current, in Amperes
 R = resistance, in Ohms

Ohms Law for Series Circuits:

Resistance in Series:

$$R_t = R_1 + R_2 + R_3 + \dots$$

where:

R_t = total resistance in series

R_1, R_2, \dots are individual resistors

Voltage in a Series Circuit:

$$E_t = E_1 + E_2 + E_3 \dots$$

where:

E_t = total voltage applied to the circuit

E_1, E_2, \dots = the voltage drops across the individual resistors

Rule: In a series circuit the total voltage drop equals the sum of the individual voltage drops.

Current in a Series Circuit:

$$I_t = I_1 = I_2 = I_3 \dots$$

where

I_t current in the series circuit

I_1, I_2, \dots currents through each resistor which are the same as the total current

Rule: There is only one path for current to flow in a series circuit, therefore the same current flows everywhere in the circuit and is always the same as the total current.

Ohms Law for Parallel Circuits:

Resistance in Parallel:

There are two formulas.

1. If only two resistors are in parallel, use the following formula:

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

2. If more than two resistors, use the following formula:

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots}$$

Note: The total resistance in parallel is always less than the value of the smallest resistor.

Voltage in a Parallel Circuit:

$$E_T = E_1 = E_2 \dots = E_N$$

Note: Voltage is common to all elements in a parallel circuit.

Current in a Parallel Circuit:

$$I_T = I_1 + I_2 + \dots + I_N$$

Note: the total current is the sum of all the individual currents flowing in all of the various branches of the parallel circuit.

Power:

$$P = E \times I$$

$$P = I^2 \times R$$

$$P = \frac{E^2}{R}$$

Where:

P = power in Watts

E = voltage in Volts

I = current in Amperes

Inductors:

Inductors in Series:

$$L_T = L_1 + L_2 + \dots + L_N$$

Note: same formula as resistors in series

Inductors in Parallel:

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$

Note: same formula as resistors in parallel.

Capacitors:

Capacitors in Parallel:

$$C_T = C_1 + C_2 + \dots + C_N$$

Note: same formula as resistors in series.

Capacitors in Series:

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$$

Note: same formula as resistors in parallel.

Reactance:

Inductive Reactance:

$$X_L = 2 \times \text{PI} \times f \times L$$

Where:

X = inductive reactance in ohms

$2 \times \text{PI} = 6.28$

f = frequency in hertz

L = inductance in henries

Capacitive Reactance:

$$X_C = \frac{1}{2 \times \text{PI} \times f \times C}$$

Where:

X = capacitive reactance in ohms

2 × PI = 6.28

f = frequency in hertz

C = capacitance in farads

Resonance:

$$f_R = \frac{1}{2 \times \text{PI} \times \text{SQRT}(L \times C)}$$

Where:

f = resonance frequency

2 PI = 6.28

L = inductance in henrys

C = capacitance in farads

SQRT is short for Square Root

Wavelength:

$$\text{Wavelength} = \frac{c}{f}$$

$$c = \frac{\text{Wavelength}}{f}$$

Where:

Wavelength is in metres

f = frequency in Hertz

c = speed of light (300 000 000 metres/second)

This can be simplified if we consider frequency in megahertz:

$$f = \frac{300}{\text{Wavelength}}$$

$$\text{Wavelength} = \frac{300}{f}$$

Where:

Wavelength is in metres

f = frequency in Hertz

c = speed of light (300 000 000 metres/second)

Remember: this is for a full wavelength. Divide by two for a half wavelength.

Frequency and Period Relationships:

$$\text{frequency} = \frac{1}{\text{time}}$$

$$f = \frac{1}{t}$$

$$\text{time} = \frac{1}{\text{frequency}}$$

$$t = \frac{1}{f}$$

Where:

t is the time, called *period* in this case

f is the frequency

Example: what is the frequency of a waveform having a period of 0.001 seconds?

$$f = \frac{1}{\text{---}}$$

$$t = \frac{1}{f}$$
$$f = \frac{1}{0.001 \text{ (sec)}}$$
$$f = 1\,000 \text{ (Hz)}$$

Example: what is the period of a signal of 500 Hz?

$$t = \frac{1}{f}$$
$$t = \frac{1}{500 \text{ (Hz)}}$$
$$t = 0.002 \text{ (seconds)}$$

(this is the time it takes for 1 cycle to occur.)