

Capacitance

Al Penney

VO1NO




Capacitance

- **Capacitance** is the property of an electrical circuit that **opposes a change in voltage**.
- When a **voltage** applied across a circuit is **increased or decreased, capacitance resists that change**.


Construction of a Capacitor

- A basic capacitor consists of **2 conducting metallic plates** separated by a **layer of air or other insulating material** such as glass, mica or even oil.
- The **insulating material** is called the **Dielectric**.

Axial Lead Capacitor

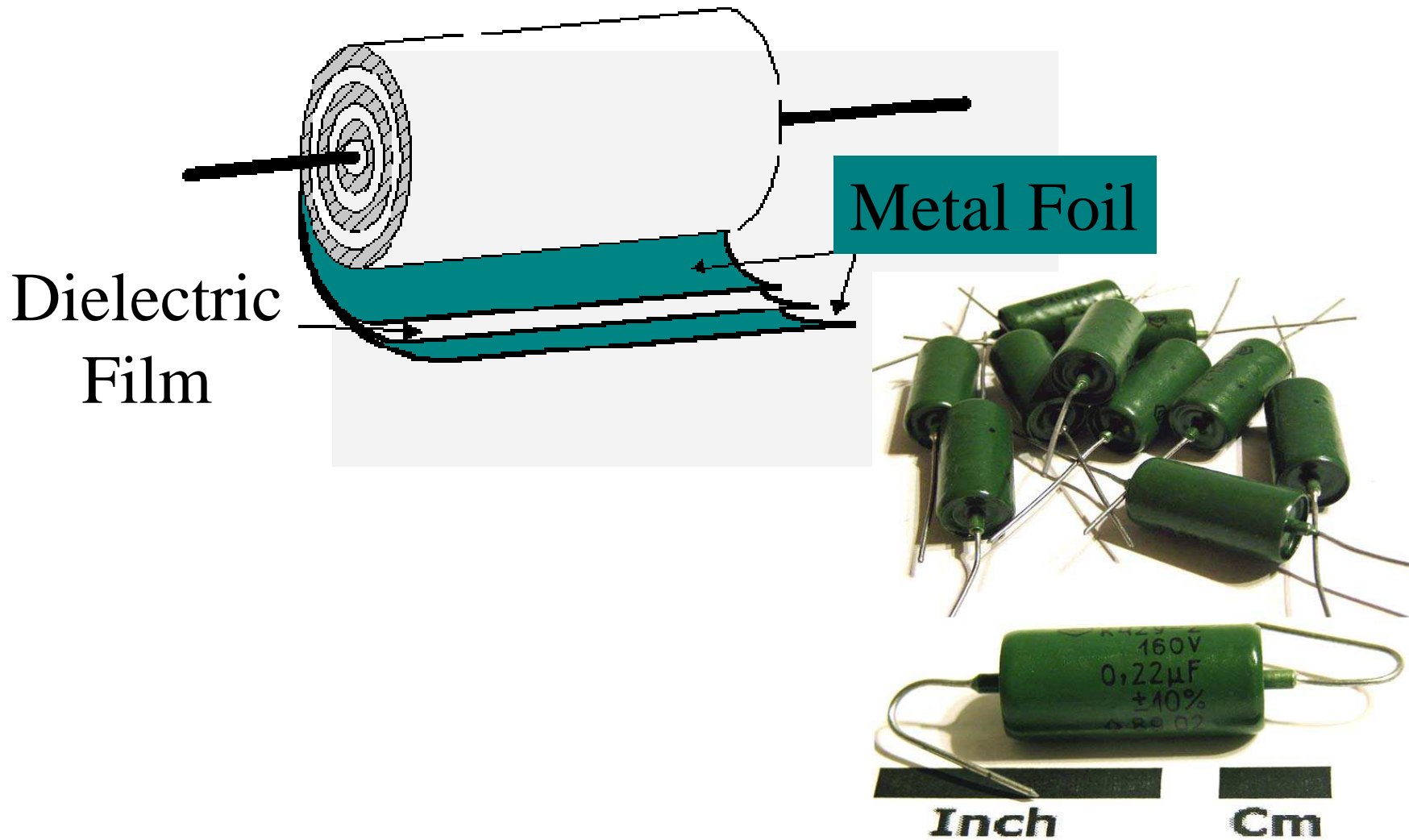


Electrolytic Capacitor

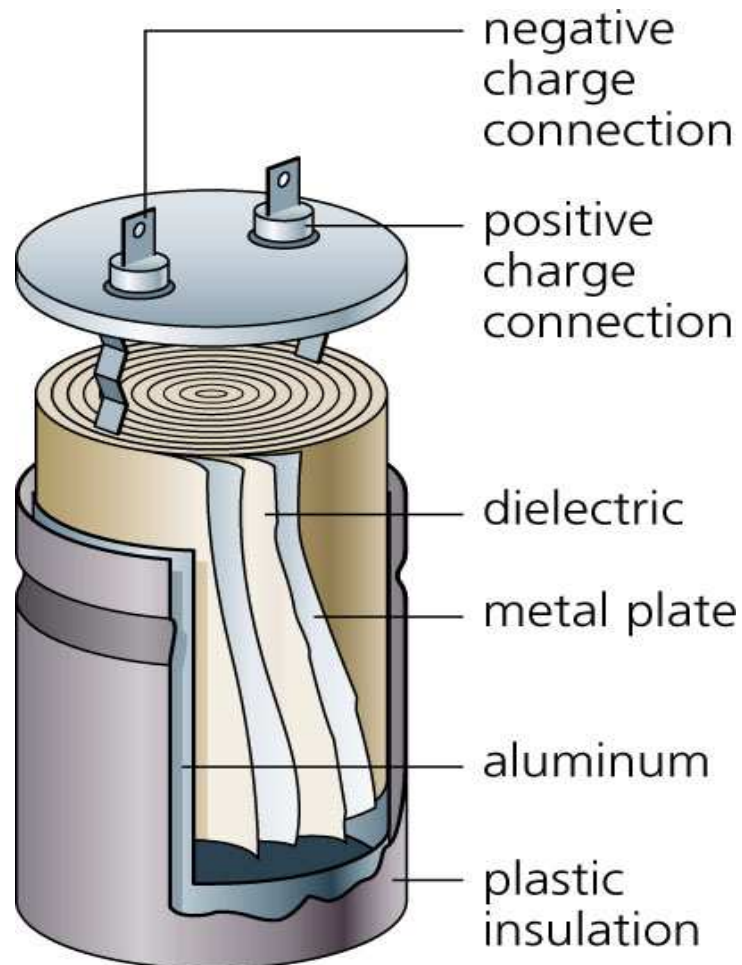

www.interfacebus.com


Radial Lead Capacitor

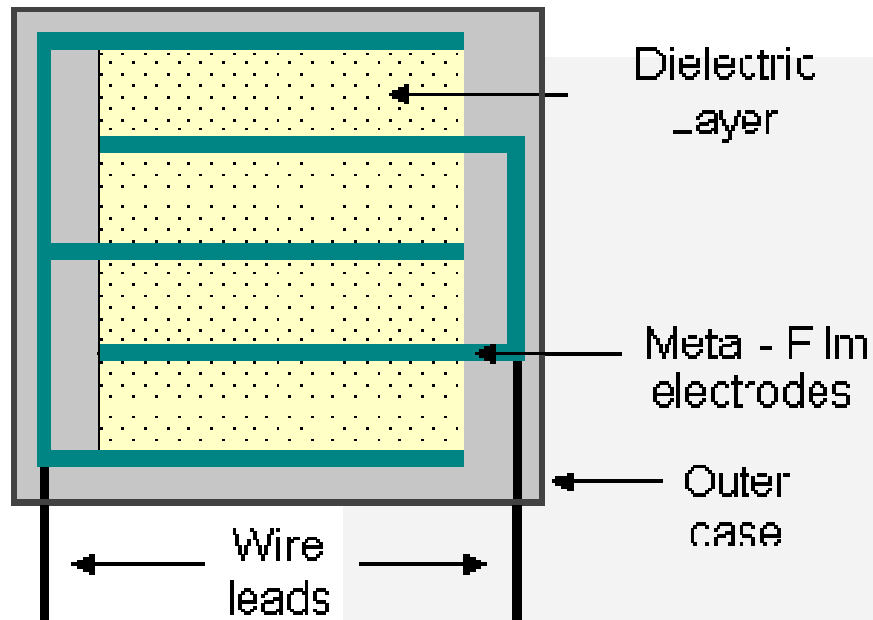


Ceramic Disc Capacitor




Variable Capacitor

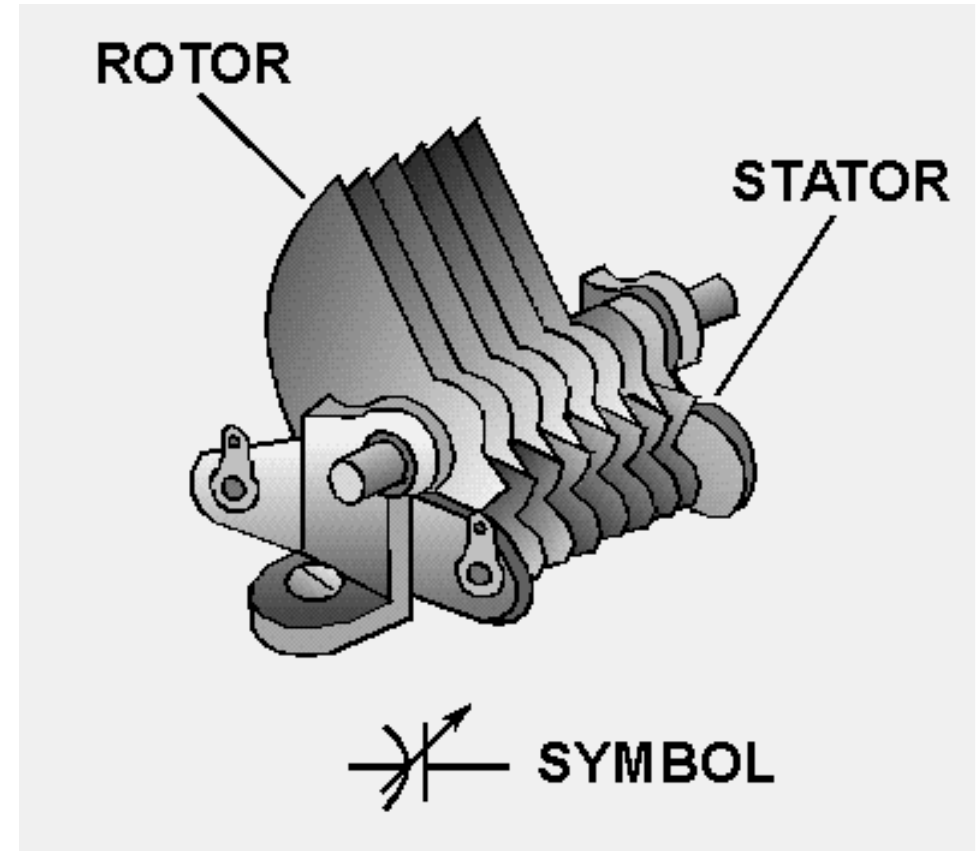

Trimmer Capacitors

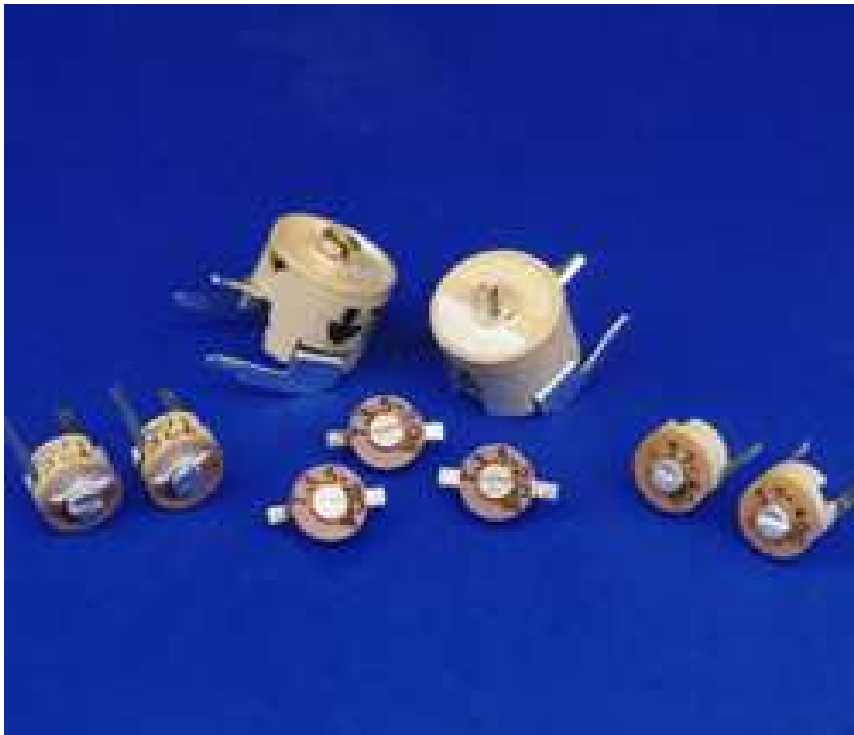


**MICA
DIELECTRIC**

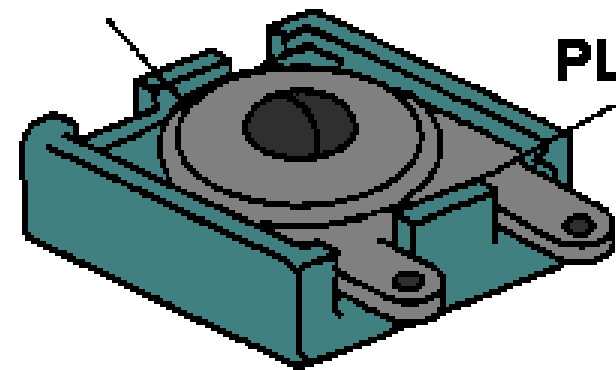


PLATES

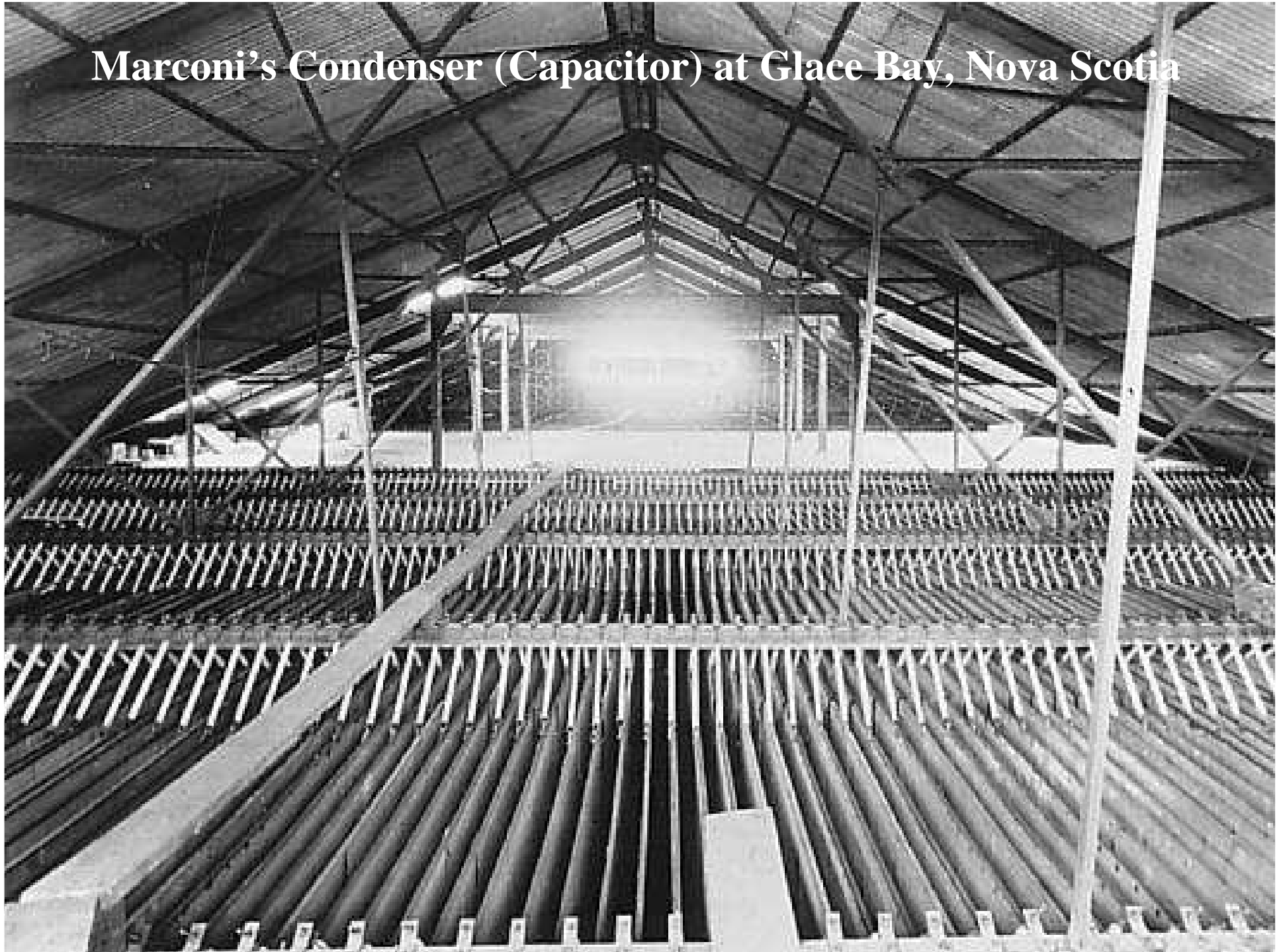 **SYMBOL**


Marconi's Condenser (Capacitor) at Glace Bay, Nova Scotia



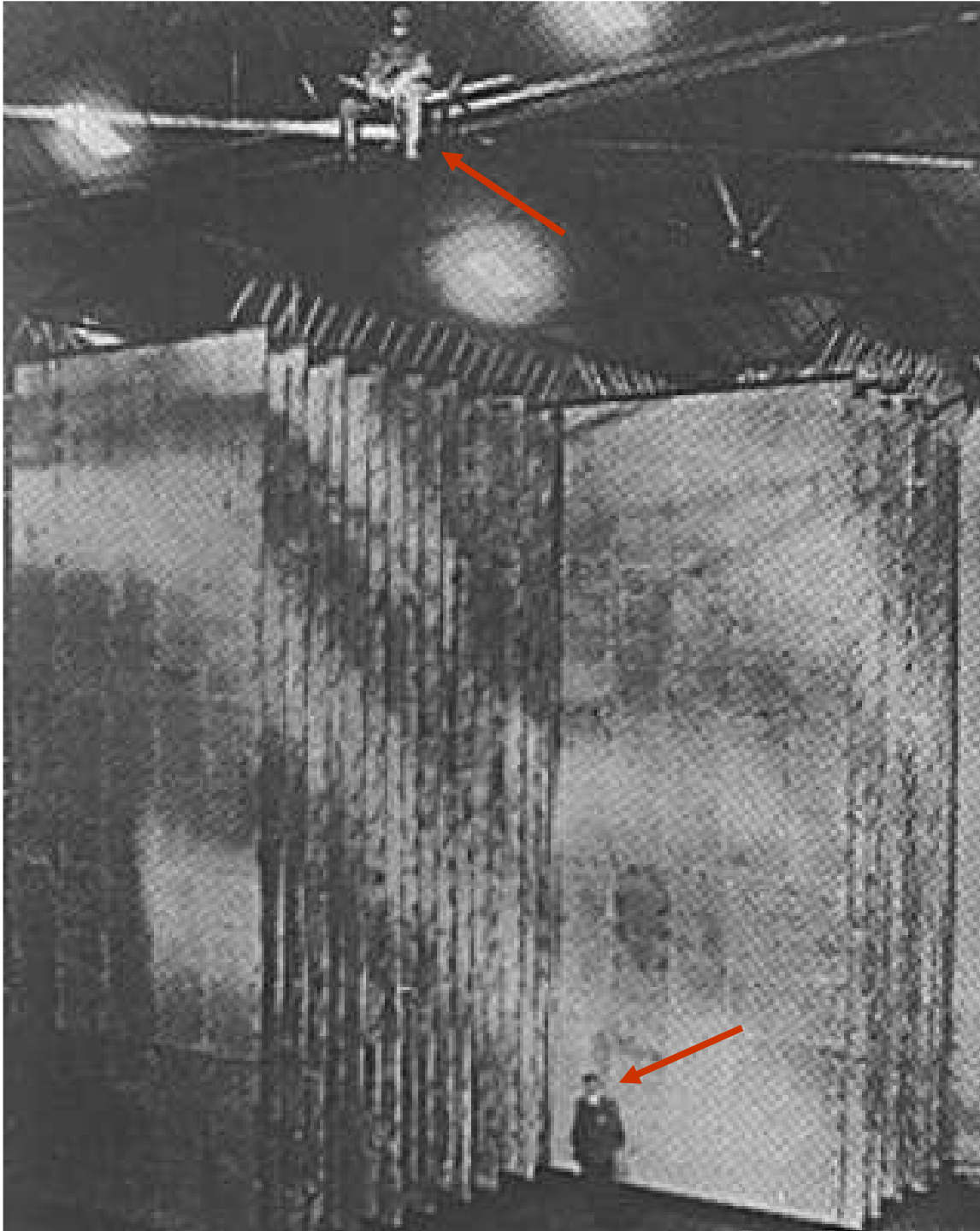


A similar capacitor at Marconi's station in Clifden, Ireland. Note the size of the two men!


Capacitor Symbols

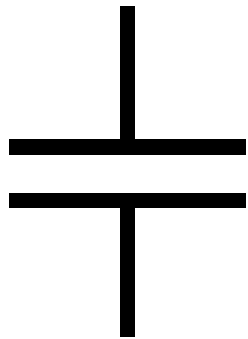


Normal

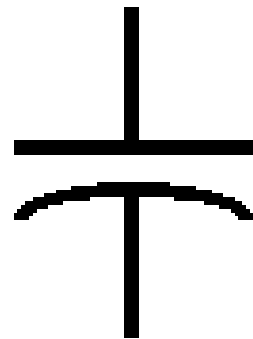

Normal

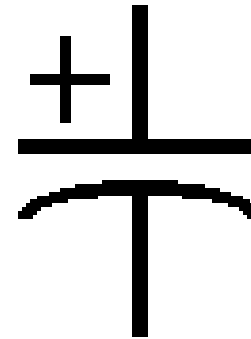


Electrolytic

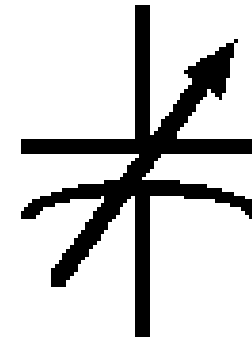

Variable

Capacitors in a DC Circuit

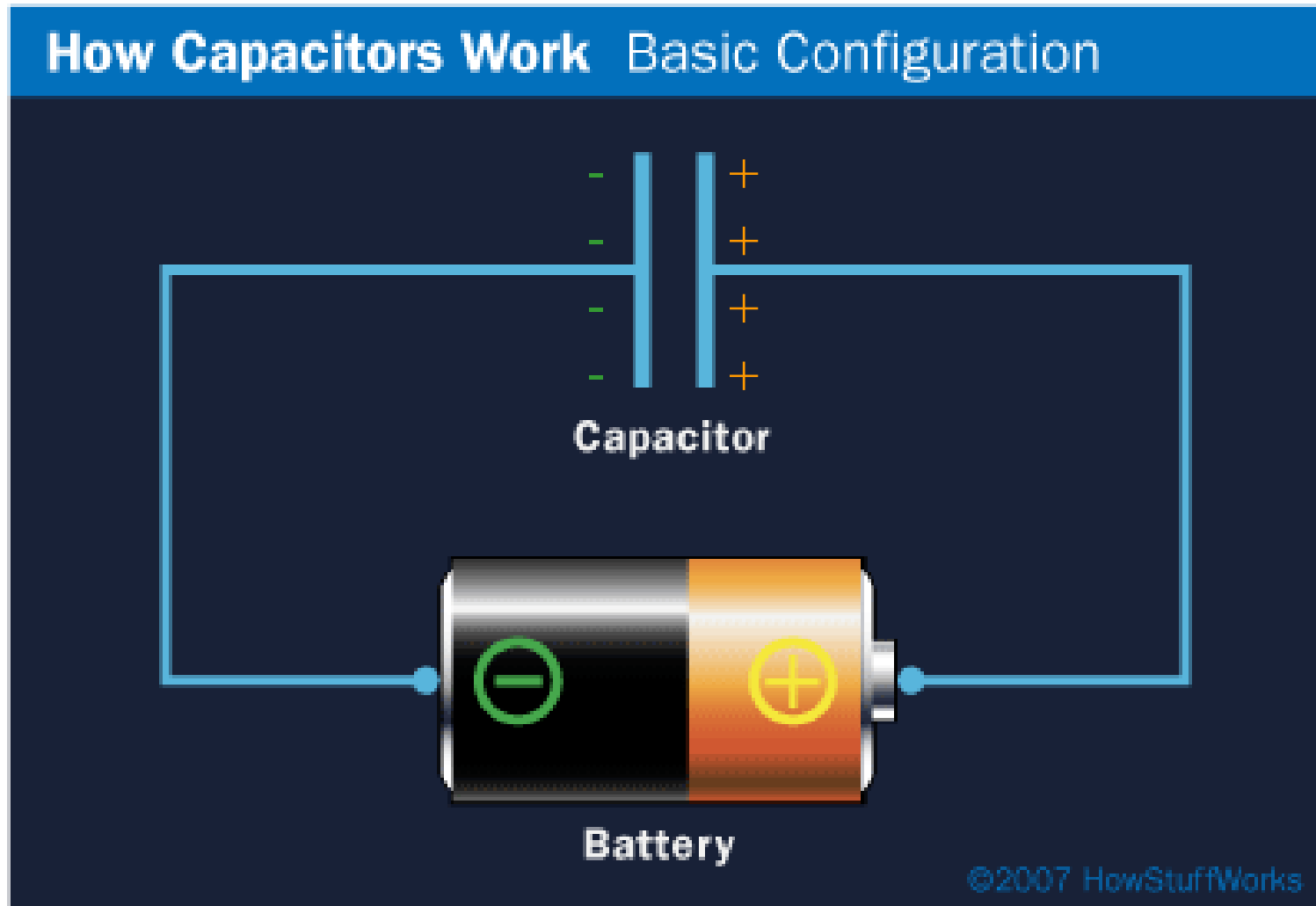



Capacitors in a DC Circuit

- When **first connected** to a battery, **electrons flow** from the **negative battery terminal** to the **capacitor plate** and remain there because the dielectric prevents them from travelling to the opposite plate.
- **Electrons** on the **opposite plate** are **attracted** to the **positive battery terminal**.
- Eventually, the capacitor reaches the **same voltage** as the battery, and **no more electrons flow**.
- The capacitor is then said to be **Charged**.
- **Capacitors block the flow of DC**.


Capacitors in an AC Circuit

- **Current cannot** pass through a capacitor but **Alternating Current appears to.**
- If the **voltage** across the plates of the capacitor is **continuously varied**, the **number of electrons varies.**
- As the voltage changes then, **it appears as though a current is flowing** even though **electrons do not actually traverse the dielectric.**

Capacitors in an AC Circuit

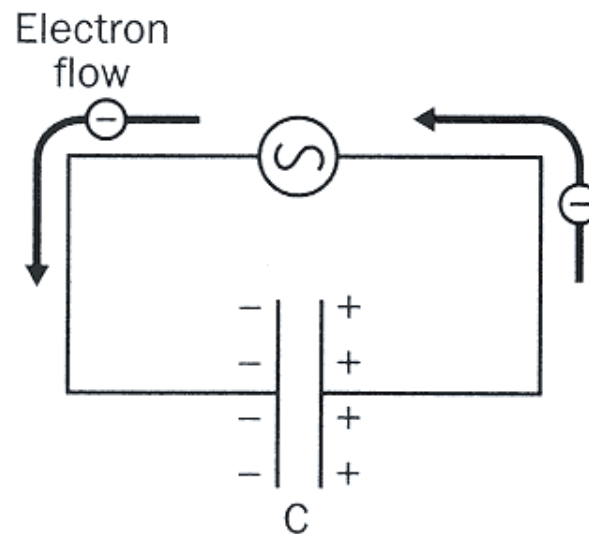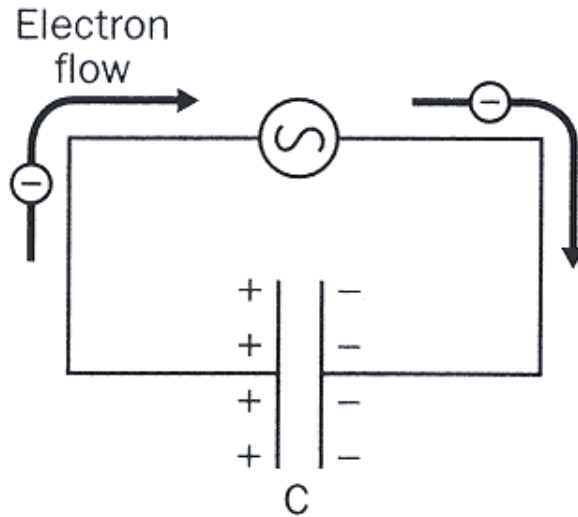

Water Reservoir Analogy

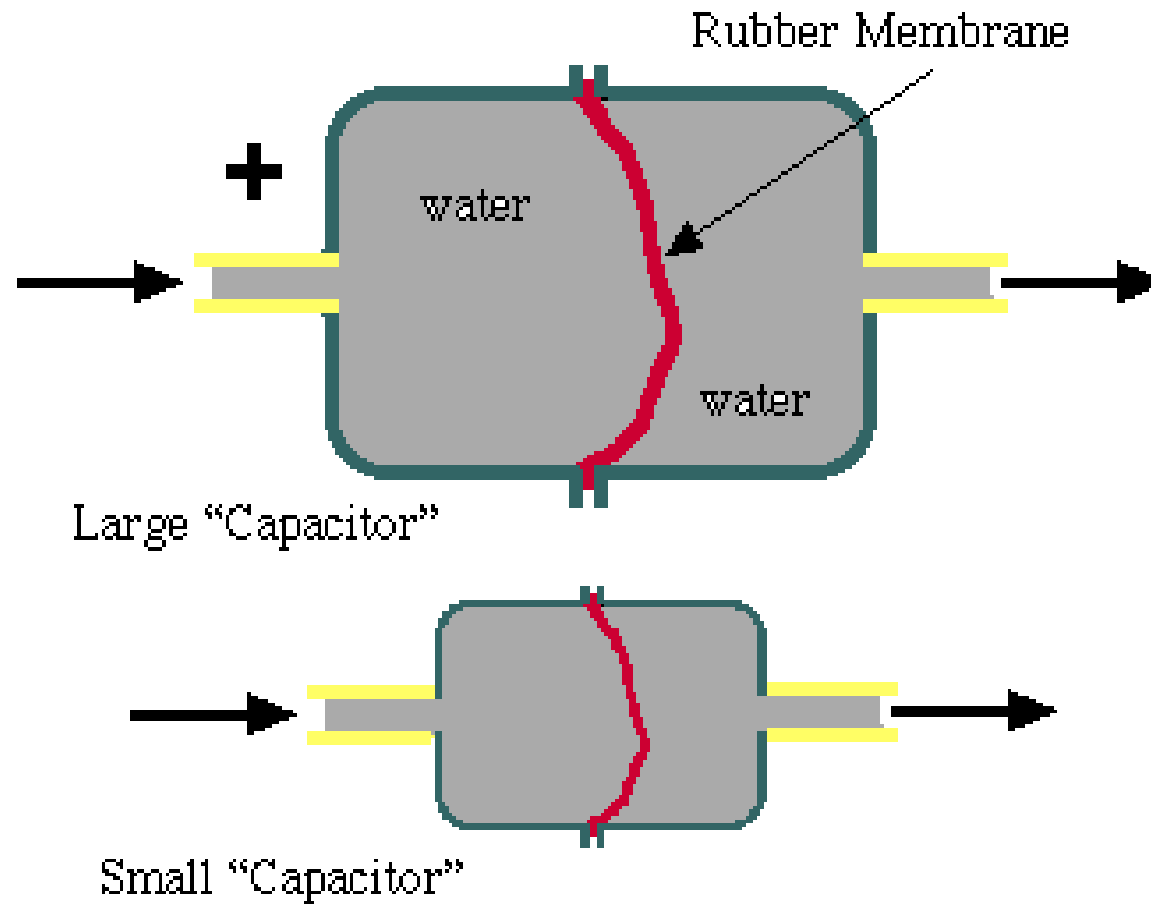

Electrons

- **Individual electrons** are **too small** to have an effect in everyday electronics, so we use a **larger number** of them to make **practical measurements**.
- The **Coulomb** is equal to **6.3×10^{18} electrons** (6,300,000,000,000,000,000 electrons).
- For example, one Ampere = 1 Coulomb per Second.

The Farad

- The **unit of measure** for capacitance is the **Farad**.
- One **Farad** is the **capacitance** in which a charge of **1 Coulomb** produces a **difference of 1 Volt** between the plates.
- One **Farad** is **much too large** a value for practical circuits however.

Practical Capacitor Units

- Practical capacitors are measured in:
 - **Microfarads**, or **millionths of a Farad**. They are abbreviated as μf , and equal to 1×10^{-6} **Farads**. The old abbreviation was mfd.
 - **Picofarads**, or **millionth millionths of Farads**, are equal to 1×10^{-12} **Farads**. They are abbreviated as pf. They were originally called Micromicrofarads, and you may still encounter the abbreviation mmf.

Factors Affecting Capacitance

- **Plate Area:** The larger the plate area, the greater the capacitance.
- **Distance Between the Plates:** The closer together the plates, the greater the capacitance. Of course, it is necessary to prevent the charge from jumping the gap (arcing).
- **Changing the Dielectric:** Greater capacitance can be obtained by using a dielectric other than air. Glass, mica, oil and mylar are some of the materials that have a greater **Dielectric Constant** than air. This is because they **permit the plates** to be **closer together**, and because they have **electrons** that can **move slightly**.

Dielectric Materials


Relative Dielectric Constants of Common Capacitor Dielectric Materials

<i>Material</i>	<i>Dielectric Constant (k)</i>	<i>(O)rganic or (I)norganic</i>
Vacuum	1 (by definition)	
Air	1.0006	
Ruby mica	6.5 - 8.7	
Glass (flint)	10	
Barium titanate (class I)	5 - 450	
Barium titanate (class II)	200 - 12000	
Kraft paper	≈ 2.6	O
Mineral Oil	≈ 2.23	O
Castor Oil	≈ 4.7	O
Halowax	≈ 5.2	O
Chlorinated diphenyl	≈ 5.3	O
Polyisobutylene	≈ 2.2	O
Polytetrafluoroethylene	≈ 2.1	O
Polyethylene terephthalate	≈ 3	O
Polystyrene	≈ 2.6	O
Polycarbonate	≈ 3.1	O
Aluminum oxide	≈ 8.4	
Tantalum pentoxide	≈ 28	
Niobium oxide	≈ 40	
Titanium dioxide	≈ 80	

(Adapted from: Charles A. Harper, *Handbook of Components for Electronics*, p 8-7.)


Capacitors in Parallel

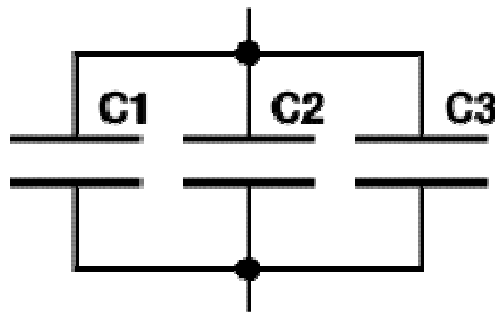- **Capacitors in Parallel add their values.**
- This is because it is **equivalent** to a **single capacitor** with a **greater surface area**.



$$C_T = C1 + C2 + C3$$

Example of Capacitors in Parallel

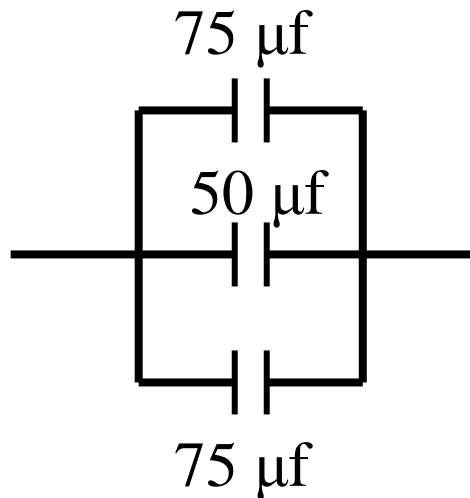


$$C_T = C_1 + C_2 + C_3$$

$$C_T = 75\ \mu\text{f} + 50\ \mu\text{f} + 75\ \mu\text{f}$$

$$C_T = 200\ \mu\text{f}$$

Capacitors in Series

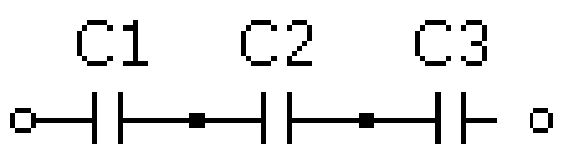
- Capacitors in Series must be treated the same way that resistors and inductors in parallel are treated.



The diagram shows three capacitors, labeled C1, C2, and C3, connected in series. Each capacitor is represented by two parallel vertical lines of unequal length. The circuit starts with an open terminal on the left, followed by capacitor C1, then capacitor C2, then capacitor C3, and ends with an open terminal on the right.

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

Example of Capacitors in Series

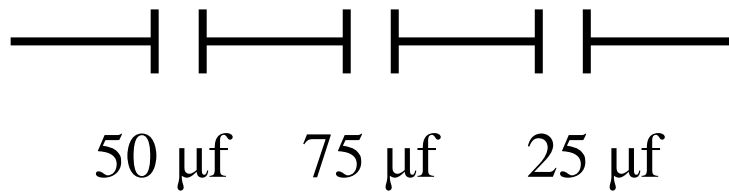

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$C_T = \frac{1}{\frac{1}{50} + \frac{1}{75} + \frac{1}{25}}$$

$$C_T = \frac{1}{\frac{3}{150} + \frac{2}{150} + \frac{6}{150}}$$

$$C_T = \frac{1}{11} = 150/11 \mu\text{f} = 13.64 \mu\text{f}$$

Working Voltage

- All capacitors have a **characteristic working voltage**, sometimes called the **voltage rating**.
- It is the **maximum DC voltage** that the capacitor can **sustain continuously** without **excessive leakage** or **breaking down** – ie: having the charge jump from one plate to the other (**arc**).
- **Arcing will destroy most capacitors**. Electrolytics can **self-heal** after small arcs. Even **air-gap variable capacitors** can be **damaged** by arcing.

Surge Voltage

- **Surge voltage** is the **maximum voltage** that can be **withstood** for a **few seconds** after the start-up of a circuit.
- It was an important parameter for **tube circuits**, but is **not very relevant** for modern solid-state circuits.


Reactance

- **Reactance** is the **opposition** to the **flow of Alternating Current (AC)**.
- **Reactance** has **no effect** on the flow of **Direct Current (DC)**.


Capacitive Reactance

- **Capacitive Reactance** is the **opposition** to the **flow of AC** by capacitance.
- As the **frequency of the AC** increases, **Capacitive Reactance** decreases.
- The **Symbol for Capacitive Reactance** is X_C .
- X_C is expressed in **ohms**.
- Even though it is expressed in ohms, **power is not dissipated by Reactance!** Energy stored in a **capacitor** during **one part of the AC cycle** is simply **returned to the circuit** during the **next part of the cycle!**

Capacitive Reactance

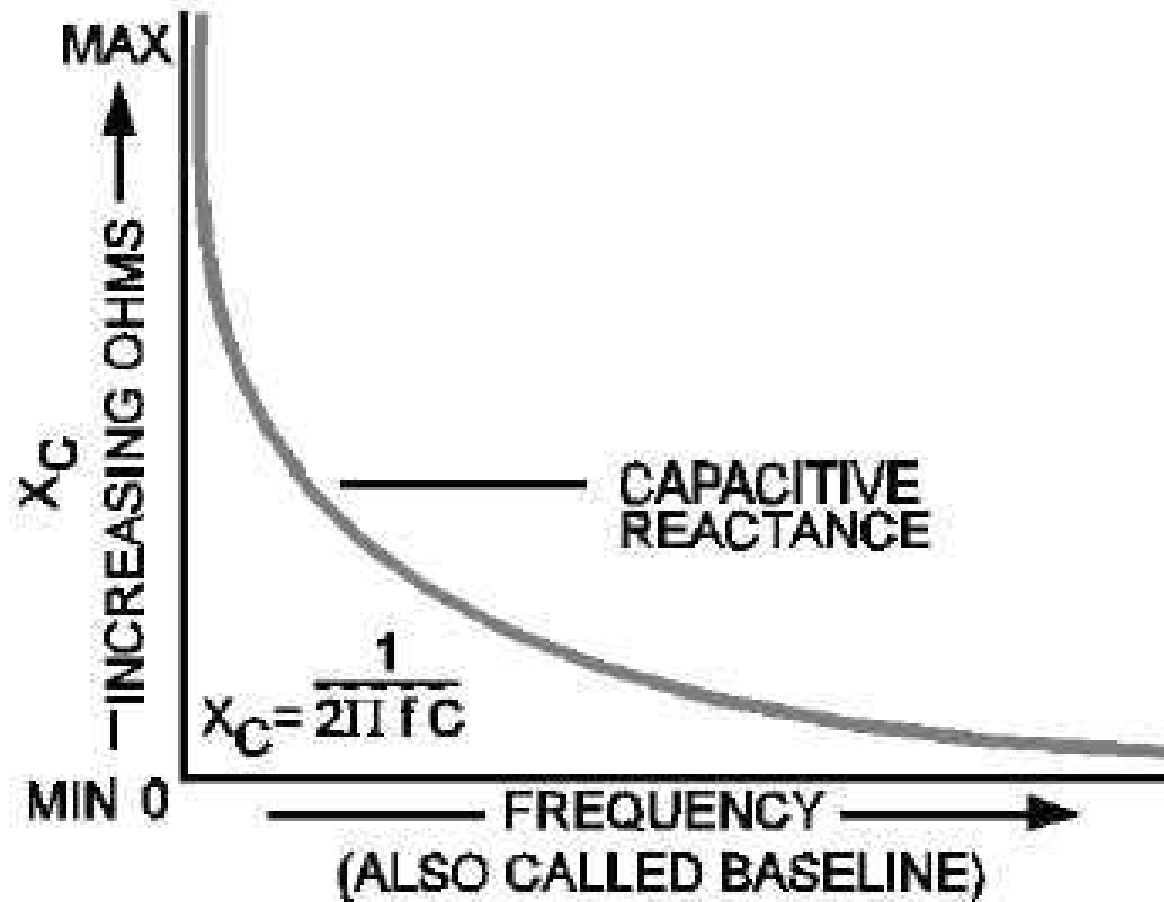

Energy Storage and Release

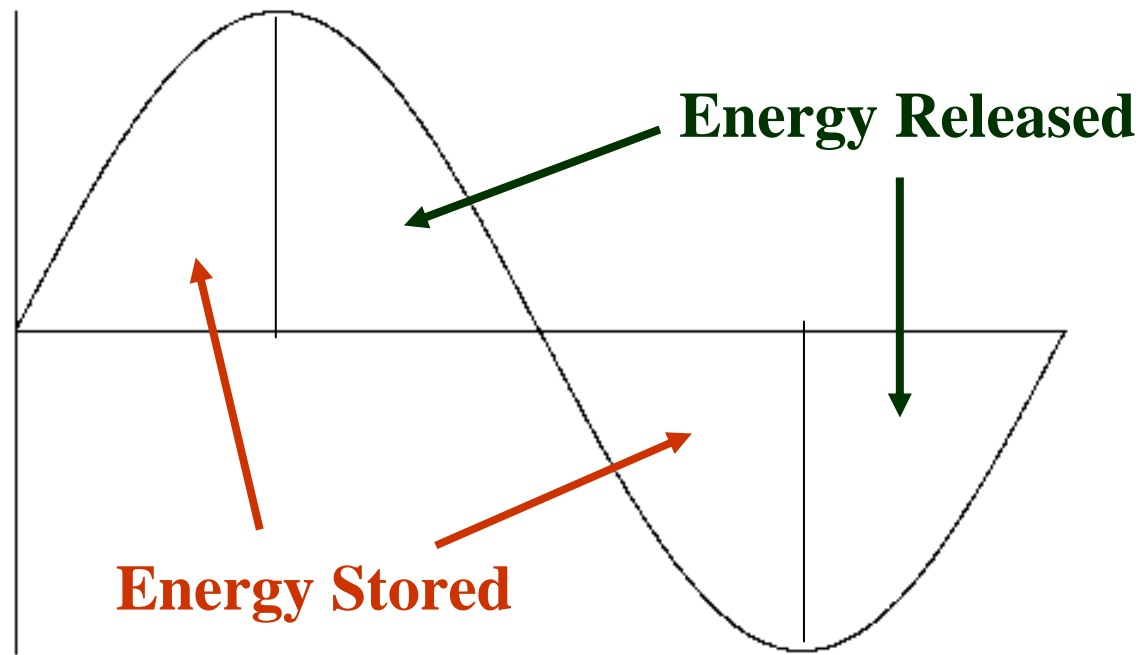

Capacitive Reactance

$$X_C = \frac{1}{2 \pi f C}$$

- Where:

F = frequency in Hertz

C = capacitance in Farads

$\pi = 3.14$

Capacitive Reactance

$$X_C = \frac{1}{2 \pi f C}$$

However, Farads and Hertz are cumbersome units, so we can use other units:

F = frequency in Megahertz (MHz)

C = capacitance in Microfarads (μf)

$\pi = 3.14$

Capacitive Reactance Example 1

- What is the capacitive reactance of a 470 pf capacitor at a frequency of 7.15 MHz?
 - Remember that 470 pf = 0.000470 μf.

$$\begin{aligned}X_C &= \frac{1}{2 \pi f C} \\&= \frac{1}{2 \pi \times 7.15 \text{ MHz} \times 0.000470 \text{ } \mu\text{F}} \\&= \frac{1 \text{ } \Omega}{0.0211} = 47.4 \text{ } \Omega\end{aligned}$$

Capacitive Reactance Example 2


- What is the capacitive reactance of that same 470 pf capacitor at a frequency of 14.29 MHz?
 - Again, remember that 470 pf = 0.000470 μf.

$$\begin{aligned}X_C &= \frac{1}{2 \pi f C} \\&= \frac{1}{2 \pi \times 14.30 \text{ MHz} \times 0.000470 \text{ } \mu\text{F}} \\&= \frac{1 \text{ } \Omega}{0.0422} = 23.7 \text{ } \Omega\end{aligned}$$







Capacitive Reactance Examples

- Note that as the **frequency increased** from 7.15 MHz to 14.290 MHz, the **Capacitive Reactance decreased** from 47.4 ohms to 23.7 ohms.
- **Remember:**
 - **Capacitors block DC;**
 - **Capacitors store energy** as an electrical charge; and
 - **As the frequency increases, capacitive reactance decreases (and vice versa!).**

Questions?

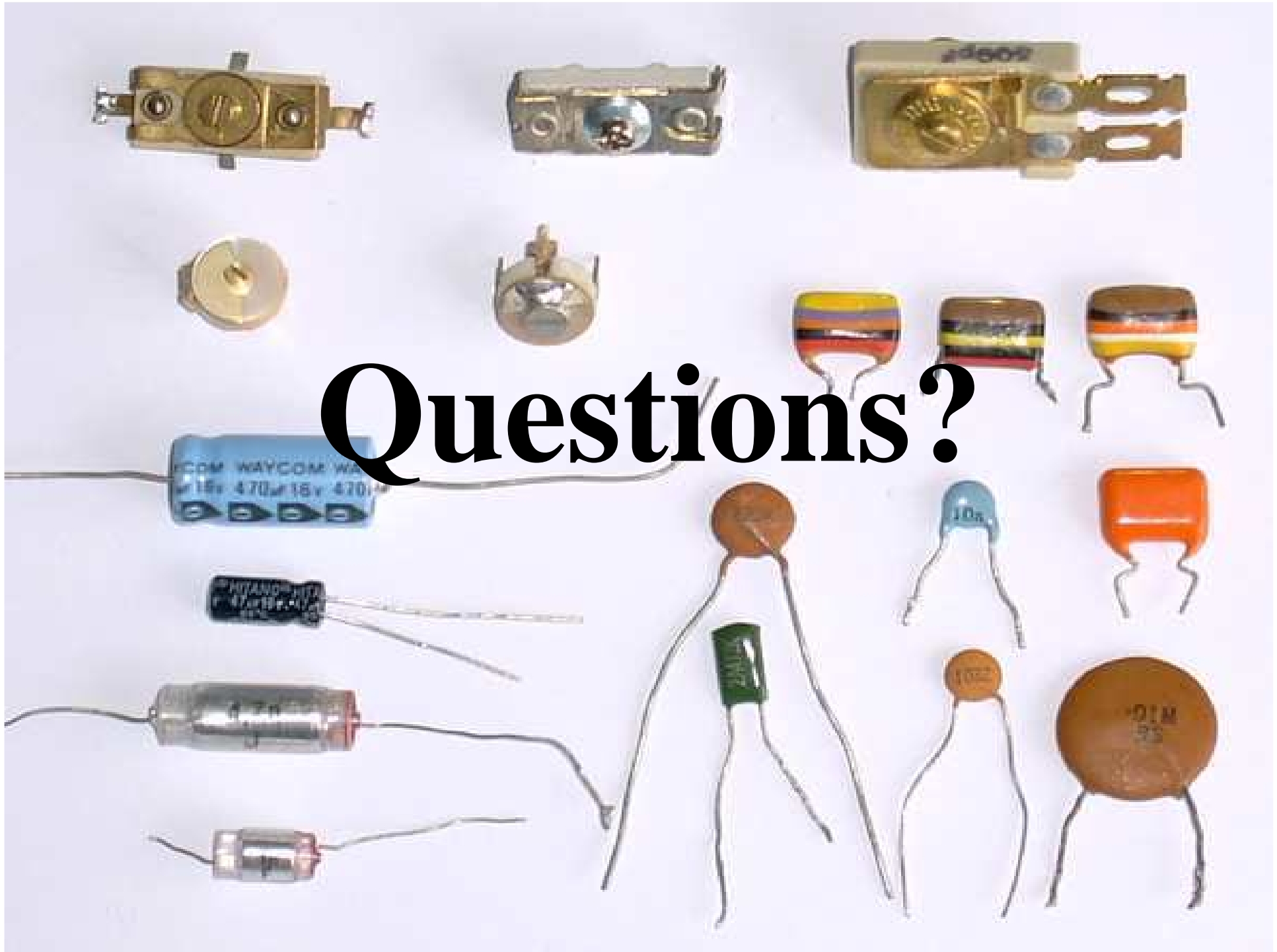

Current and Voltage

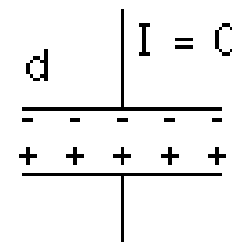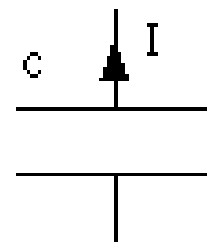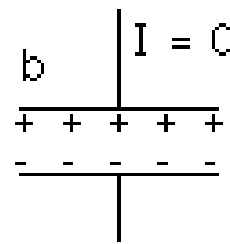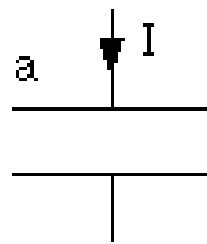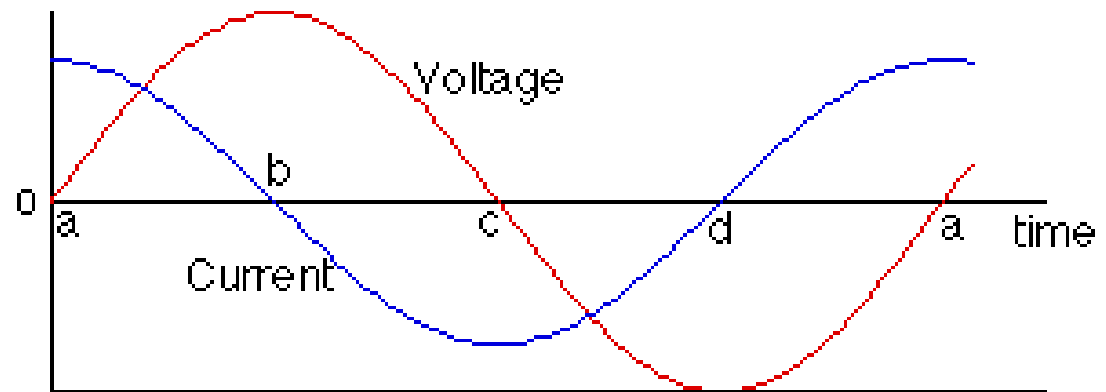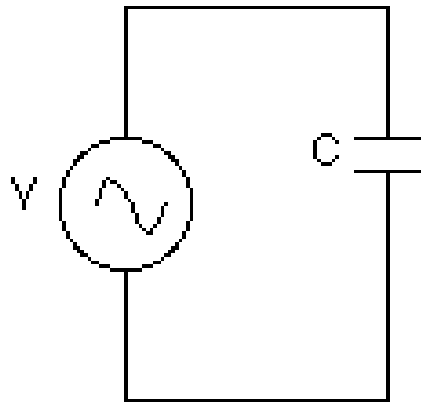

Inductive Reactance

$$X_L = \omega L$$

(units in ohms = Ω)

Capacitive Reactance

$$X_C = \frac{1}{\omega C}$$

(units in ohms = Ω)

Impedance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

(units in ohms = Ω)

Phase Angle

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

Ohm's Law for A.C. Circuits

$$V = IZ$$