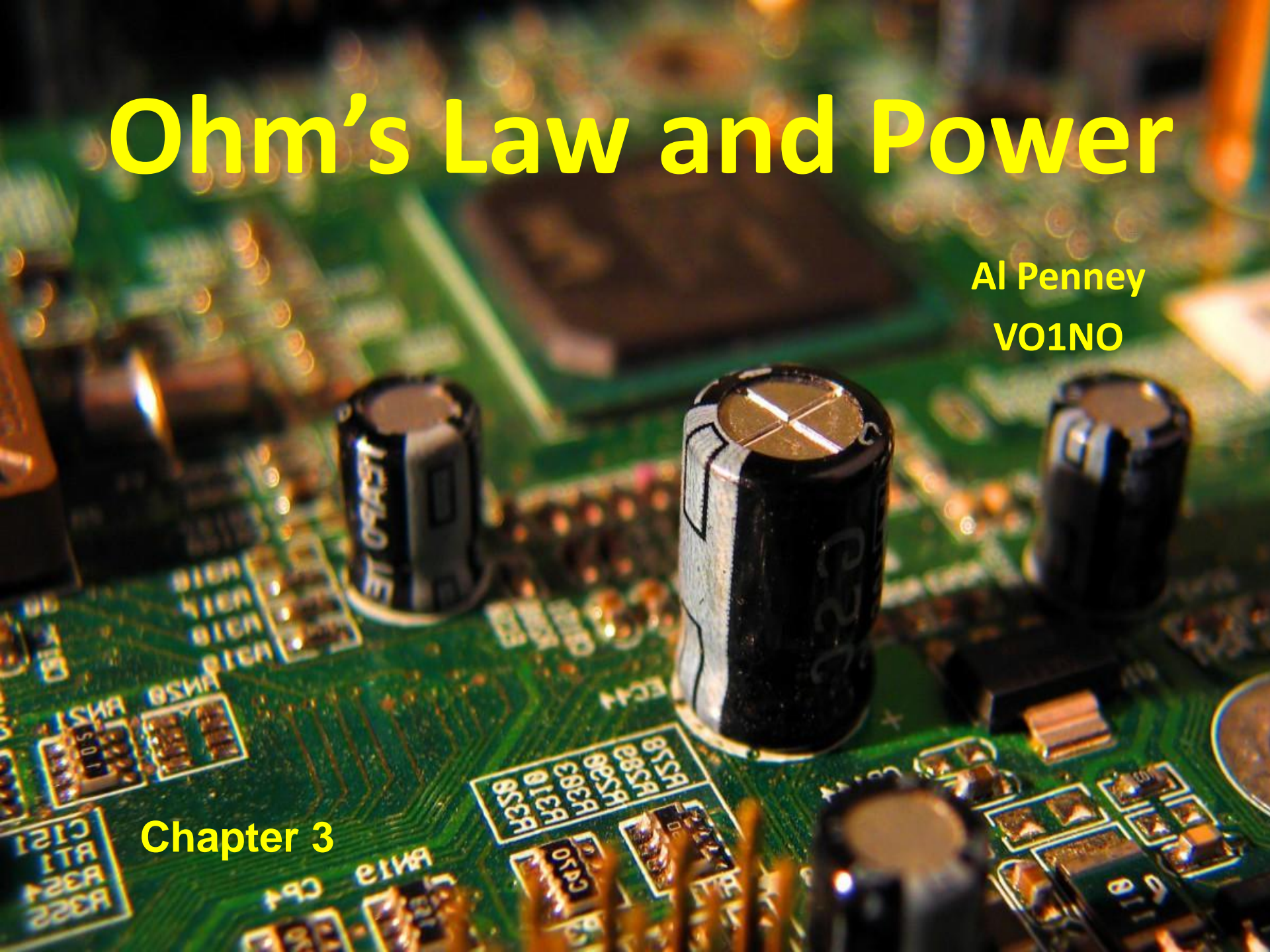



# Ohm's Law and Power

Al Penney  
VO1NO


Chapter 3



# Voltage and Current

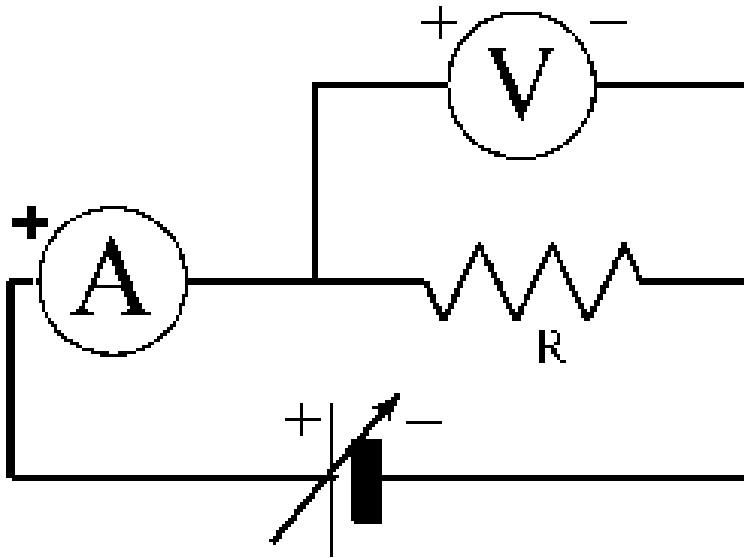

Current  
In Amps

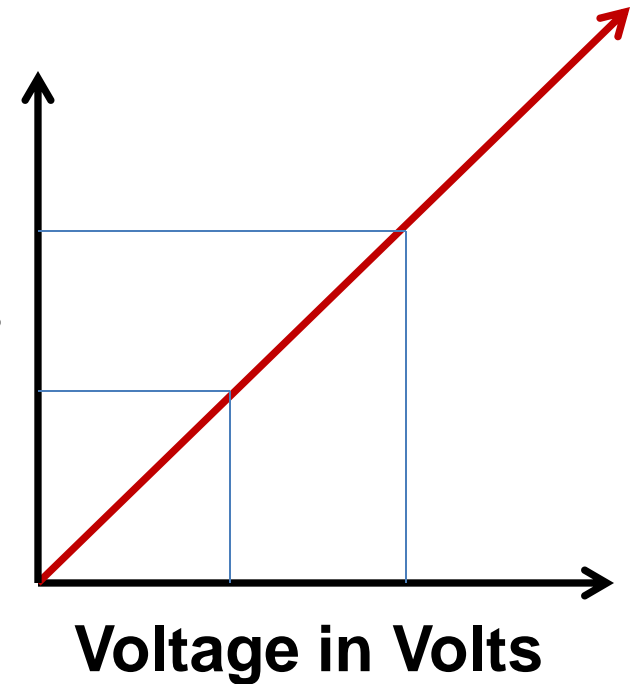

**As Voltage is increased, Current also increases.**

# Ohm's Law

- Relationship between Voltage, Current and Resistance can be expressed mathematically as:

$$E = I \times R$$

Where

E is measured in Volts;

I is measured in Amps; and

R is measured in Ohms.


# Ohm's Law

The equation can be re-written to determine any of the 3 variables if the other two are known:

$$I = E / R$$


And

$$R = E / I$$

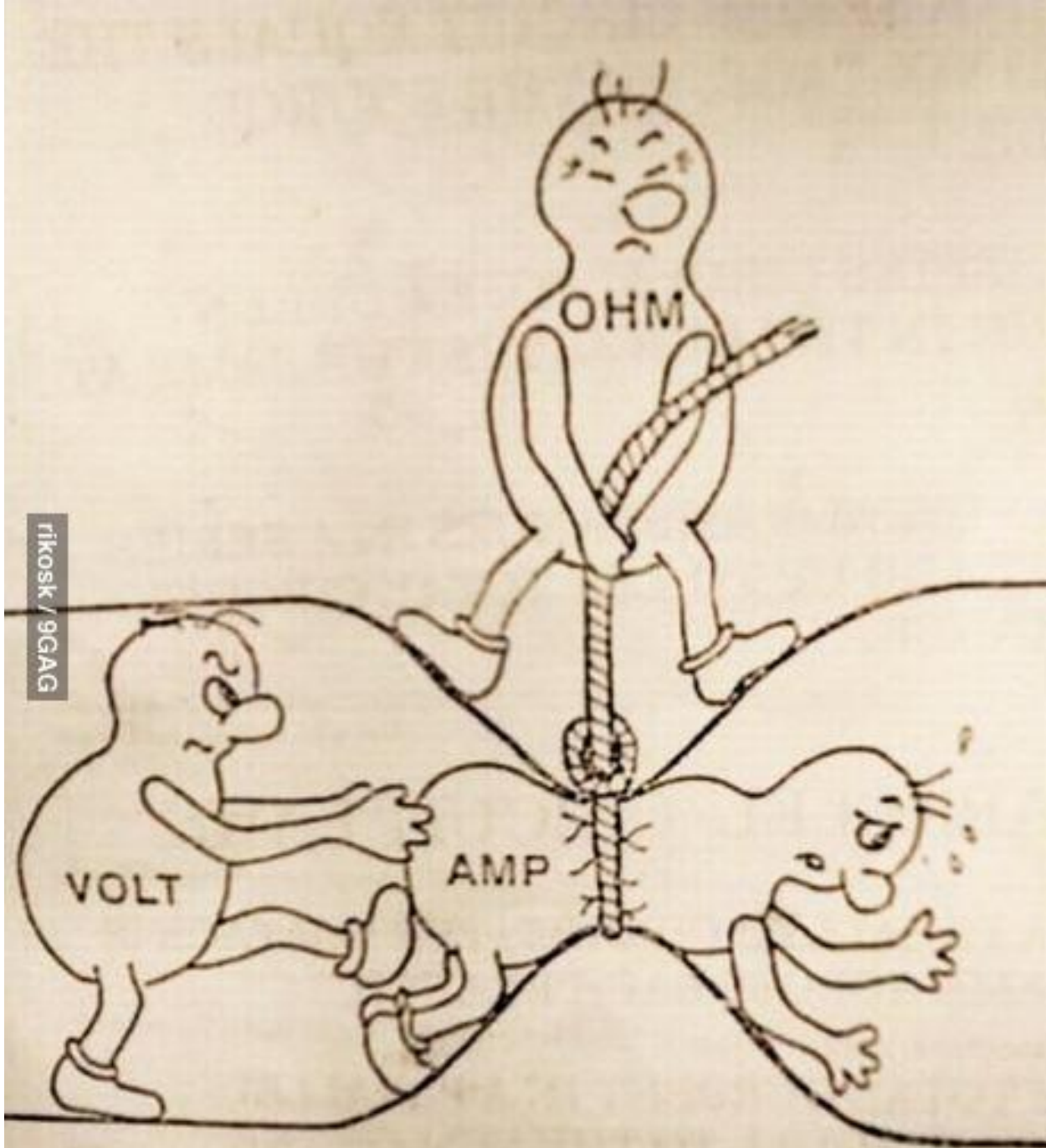



# Ohms Law Triangle

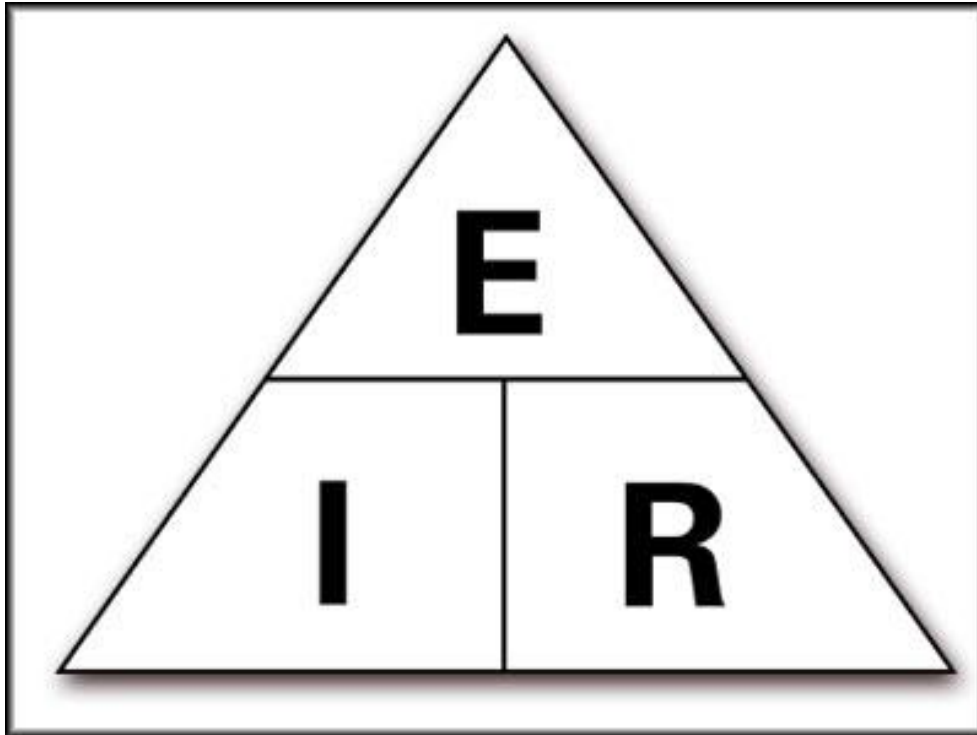


Remember the Units:


- E is measured in **VOLTS**
- I is measured in **AMPS**
- R is measured in **OHMS**

# Ohms Law Triangle


(Okay – Circle!)

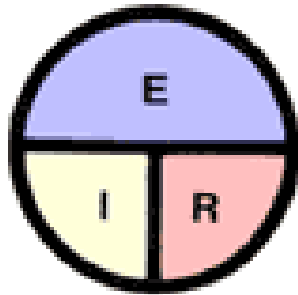

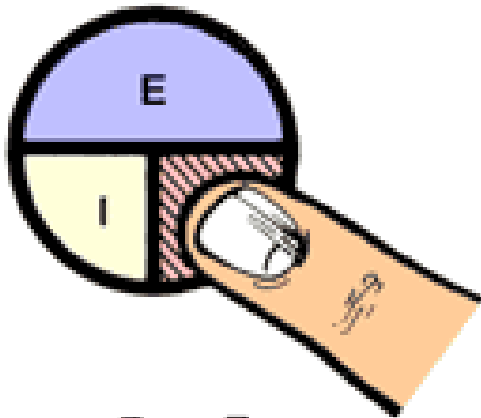
I = AMPERES (CURRENT)  
R = OHMS (RESISTANCE)  
E = VOLTS (ELECTROMOTIVE FORCE)



$$R = \frac{E}{I}$$

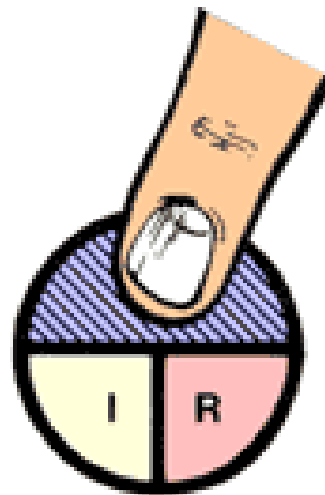


$$E = I \times R$$

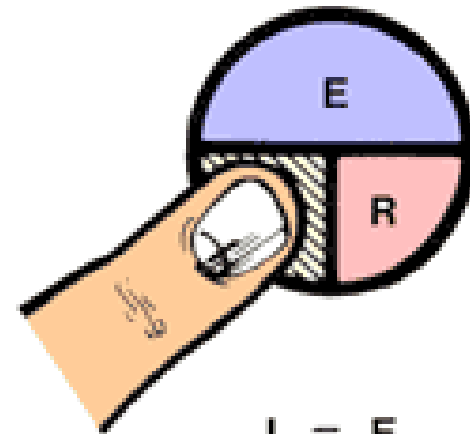

$$I = \frac{E}{R}$$

# Ohms Law Problem #1


What is the current?

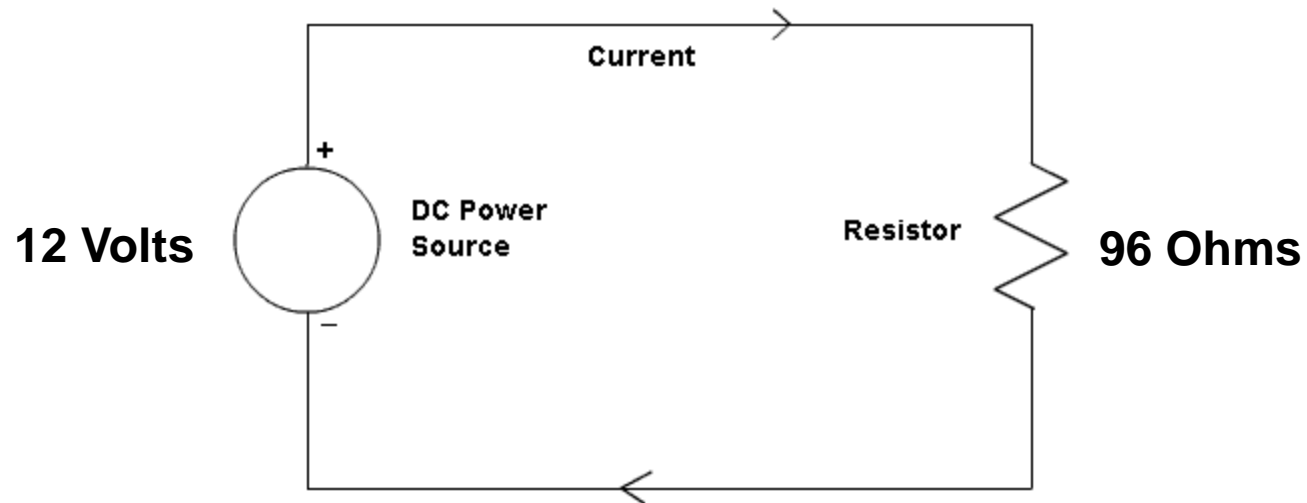




# Ohms Law Problem #1

What is the current?

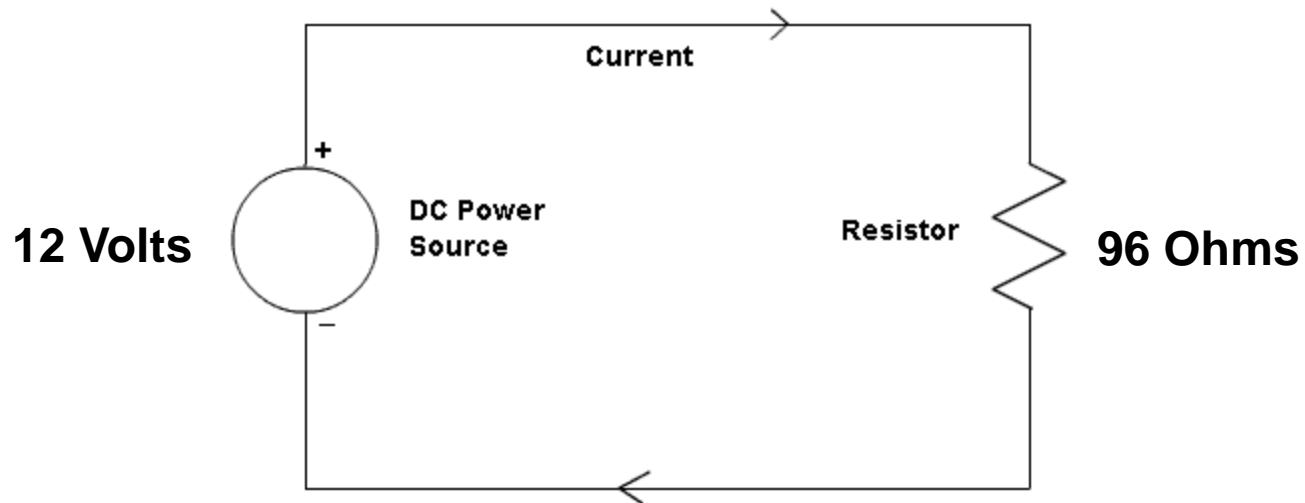


Consult the Ohms Law Triangle:

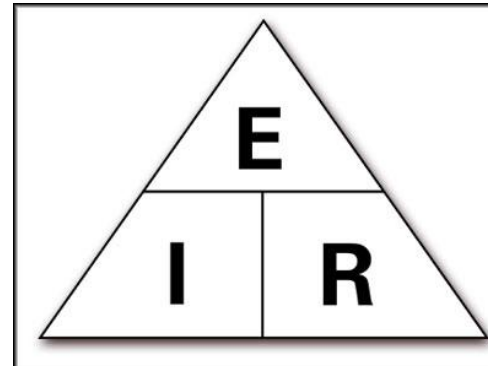


# Ohms Law Problem #1

What is the current?

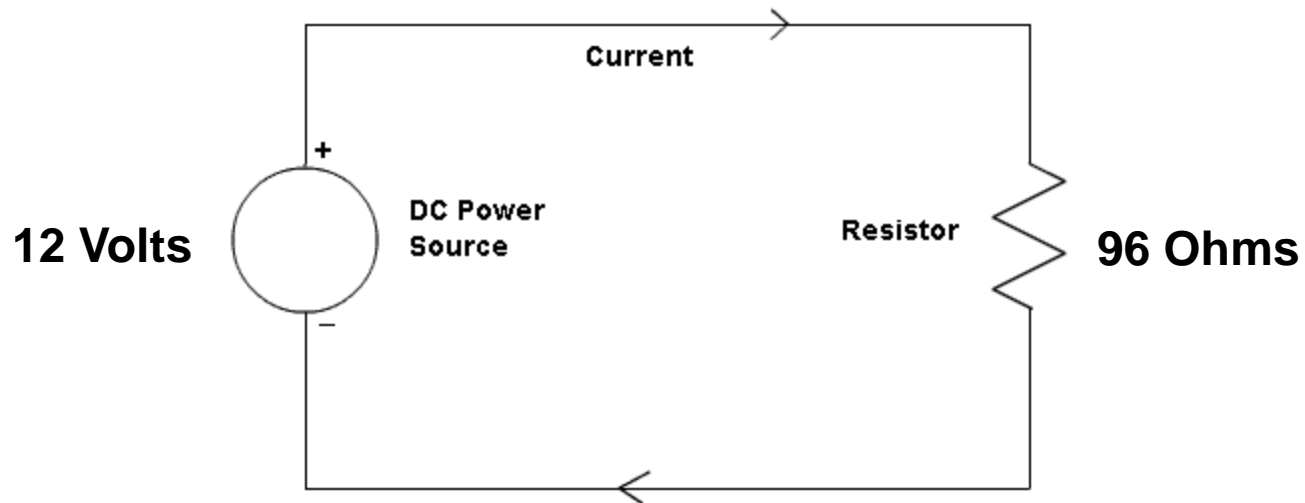


Consult the Ohms Law Triangle:

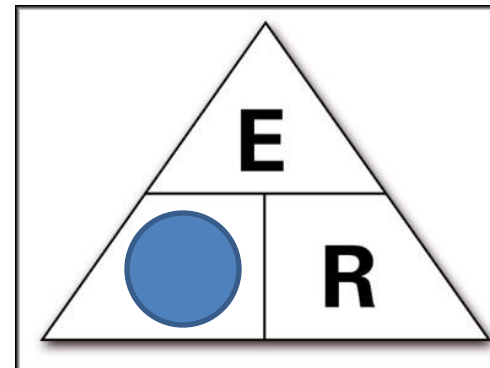

$$I = E / R$$

# Ohms Law Problem #1

What is the current?

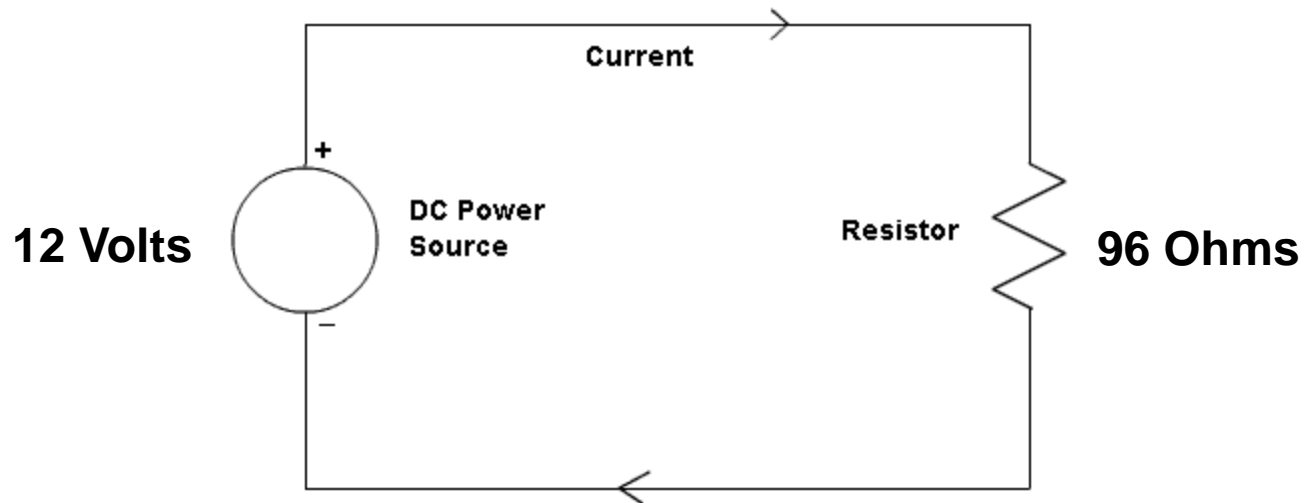


$$I = E / R$$

$$I = 12 \text{ Volts} / 96 \text{ Ohms}$$

$$I =$$

# Ohms Law Problem #1

What is the current?

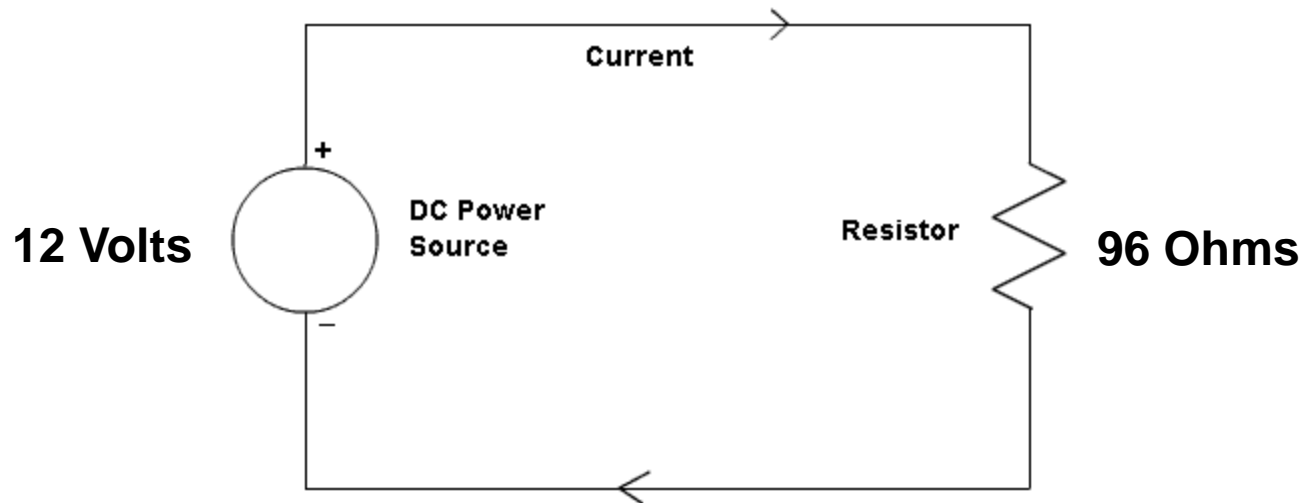


$$I = E / R$$

$$I = 12 \text{ Volts} / 96 \text{ Ohms}$$

$$I = 0.125 \text{ Amps}$$


# Ohms Law Problem #2

What is the voltage?

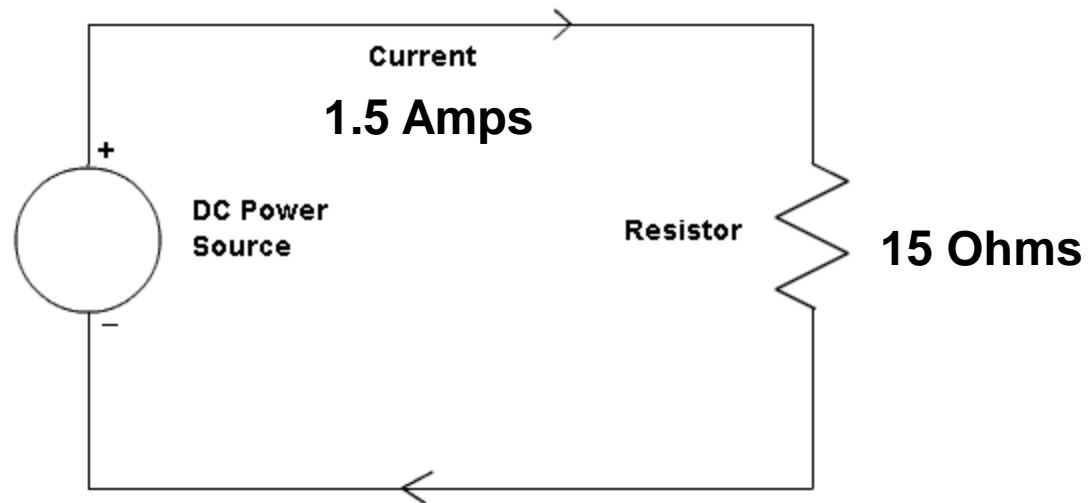


# Ohms Law Problem #2

What is the voltage?

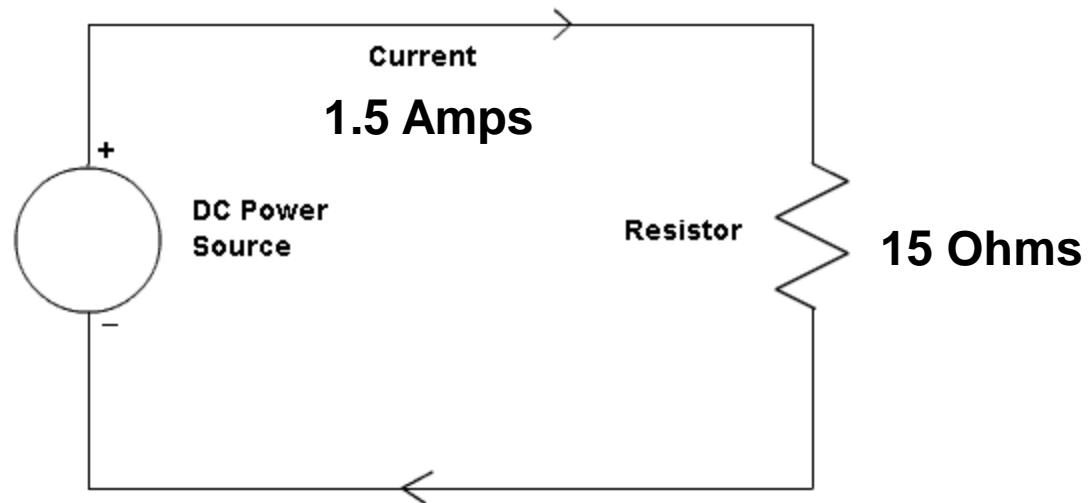


Consult the Ohms Law Triangle:

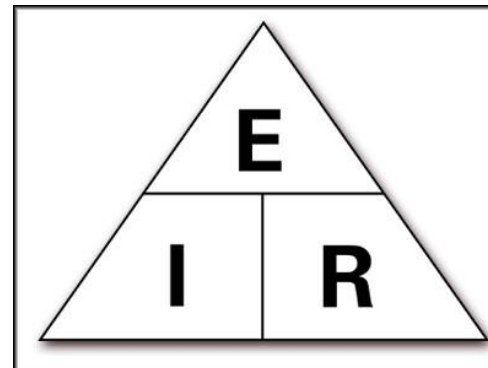


# Ohms Law Problem #2

What is the voltage?

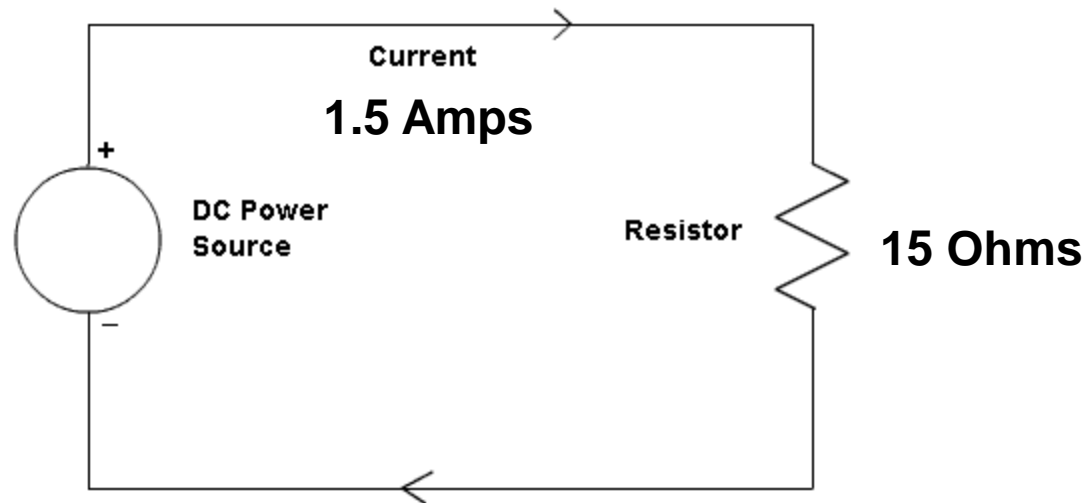

Consult the Ohms Law Triangle:

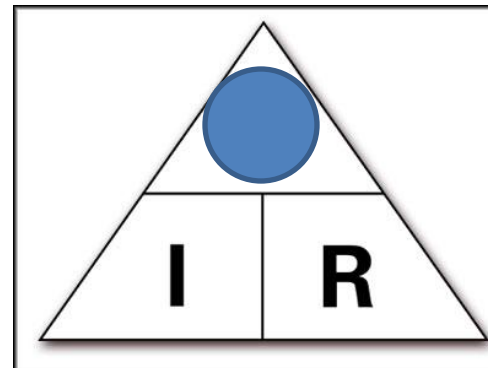


$$E = I \times R$$



# Ohms Law Problem #2


What is the voltage?

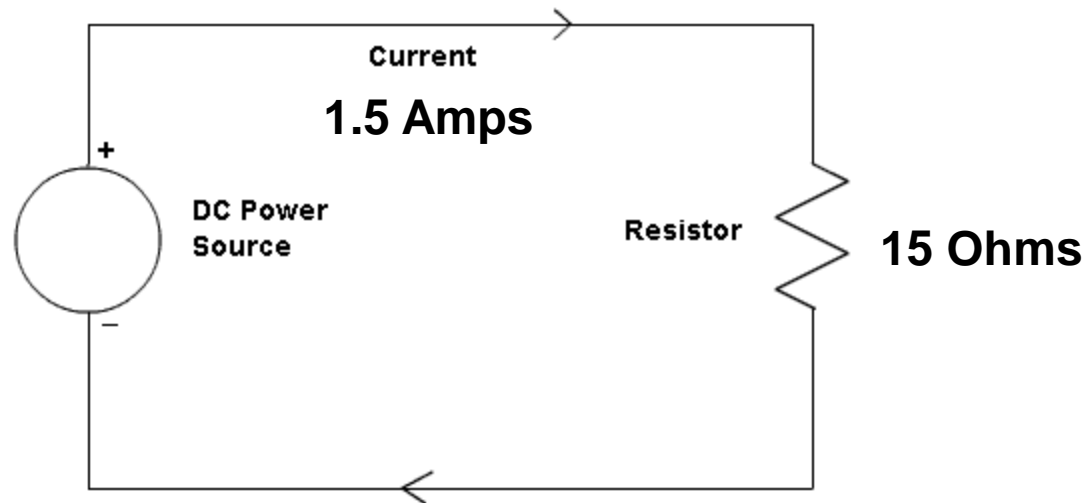

$$\begin{aligned} E &= I \times R \\ &= 1.5 \text{ Amps} \times 15 \text{ Ohms} \end{aligned}$$

# Ohms Law Problem #2


What is the voltage?

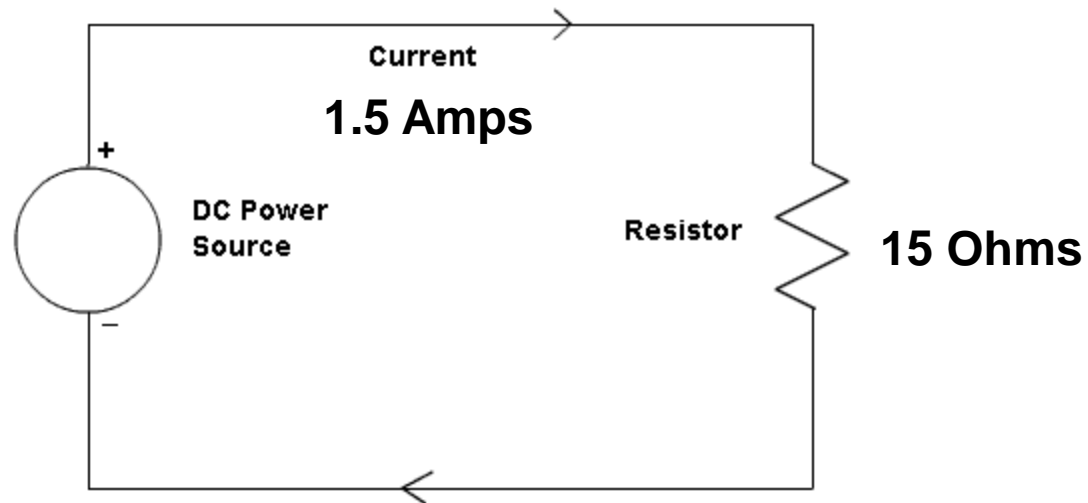

$$\begin{aligned} E &= I \times R \\ &= 1.5 \text{ Amps} \times 15 \text{ Ohms} \\ &= 22.5 \text{ Volts} \end{aligned}$$


# Ohms Law Problem #3

What is the resistance?

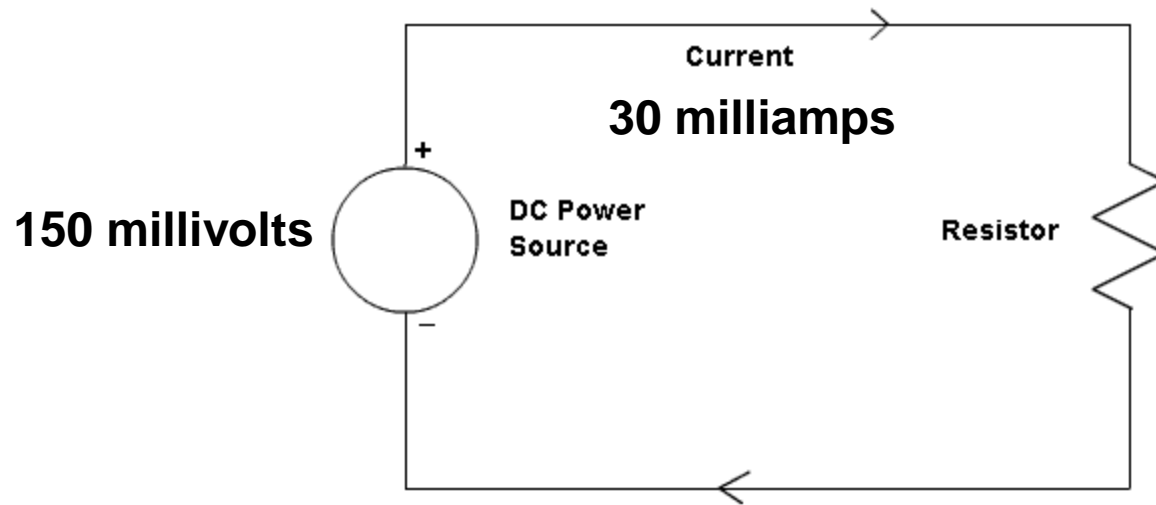


# Ohms Law Problem #3

What is the resistance?

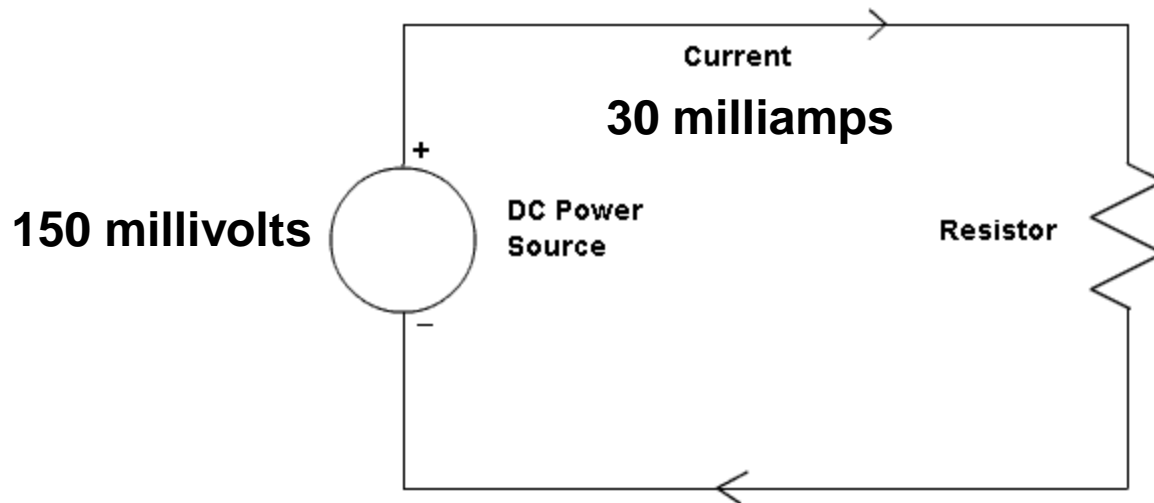


Consult the Ohms Law Triangle:

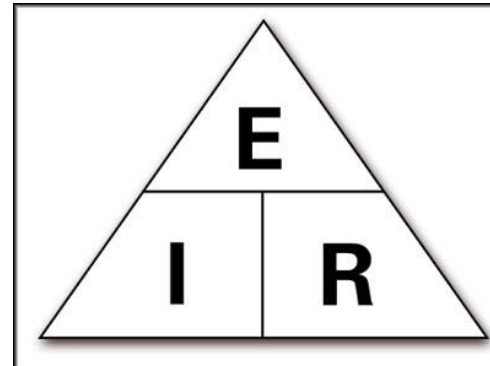


# Ohms Law Problem #3

What is the resistance?

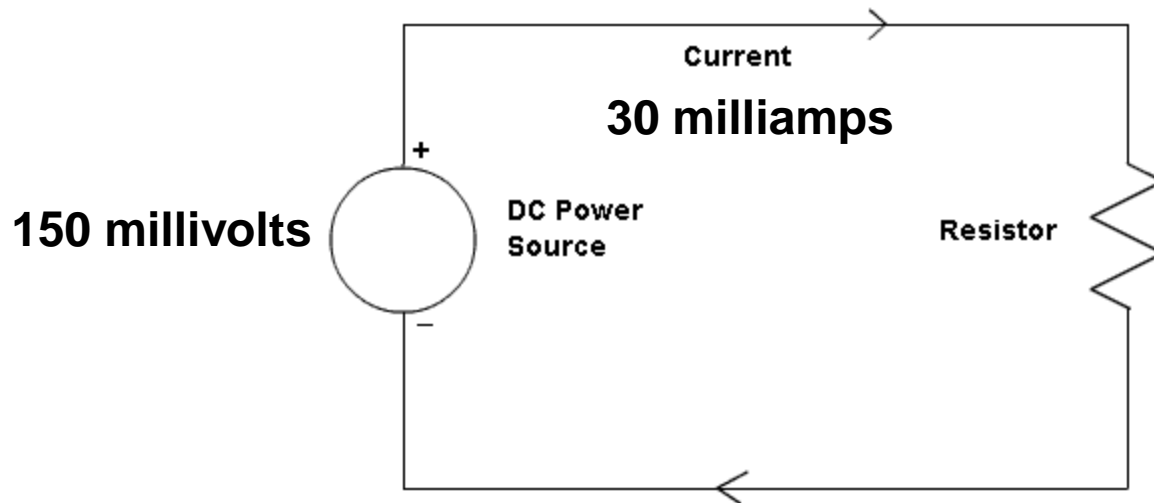


Consult the Ohms Law Triangle:

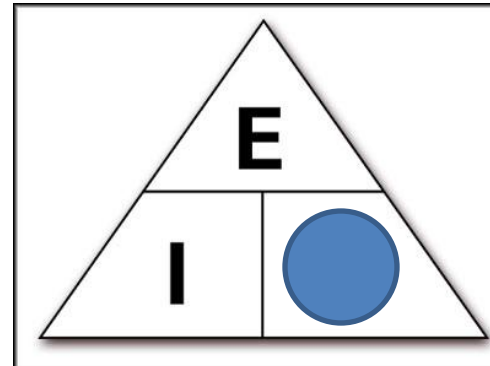

$$R = E / I$$

# Ohms Law Problem #3

What is the resistance?

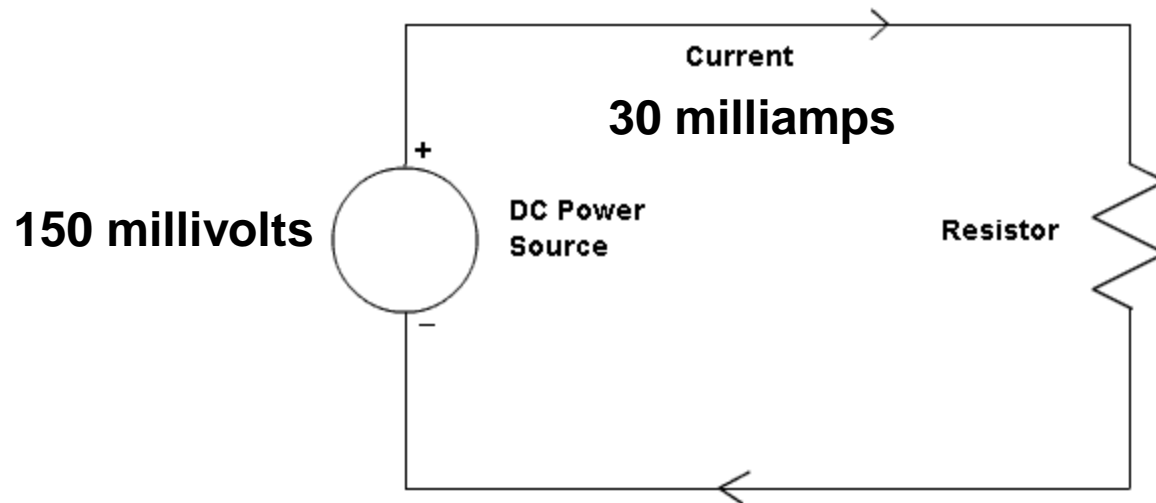

$$\begin{aligned} R &= E / I \\ &= 150 \text{ millivolts} / 30 \text{ milliamps} \end{aligned}$$


# Ohms Law Problem #3

- **REMEMBER the UNITS!**
  - 150 millivolts =  $150 / 1000$  volts = 0.15 volts
  - 30 milliamps =  $30 / 1000$  amps = 0.03 amps



# Ohms Law Problem #3


What is the resistance?

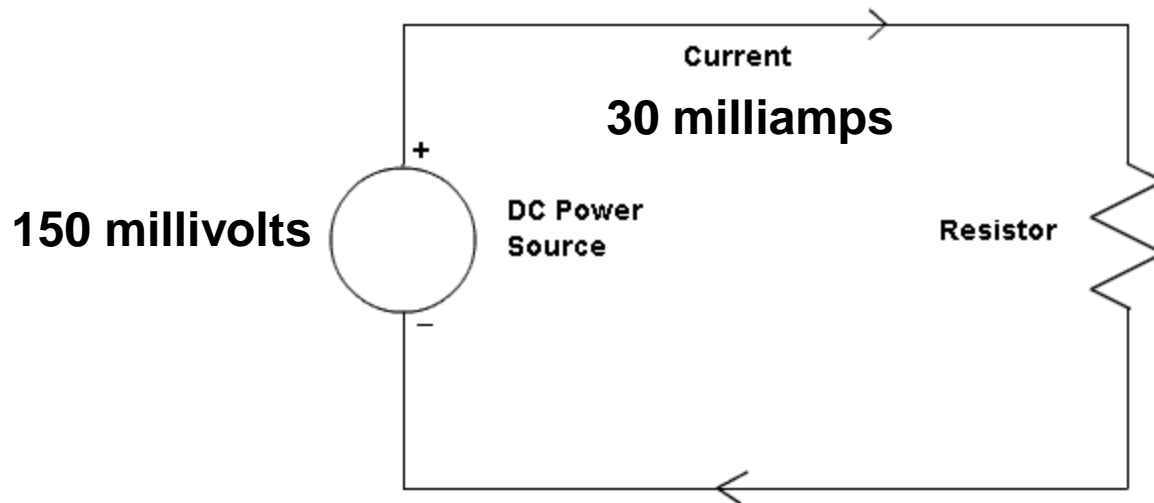

$$\begin{aligned} R &= E / I \\ &= 150 \text{ millivolts} / 30 \text{ milliamps} \\ &= 0.15 \text{ Volts} / 0.03 \text{ Amps} \end{aligned}$$

# Ohms Law Problem #3


What is the resistance?

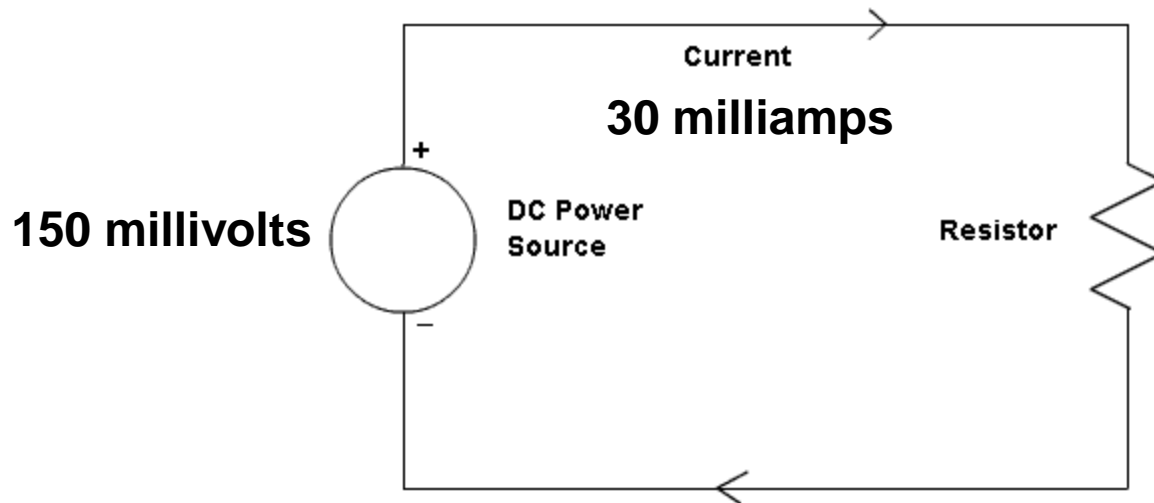

$$\begin{aligned} R &= E / I \\ &= 150 \text{ millivolts} / 30 \text{ milliamps} \\ &= 0.15 \text{ Volts} / 0.03 \text{ Amps} \\ &= 5 \text{ Ohms} \end{aligned}$$

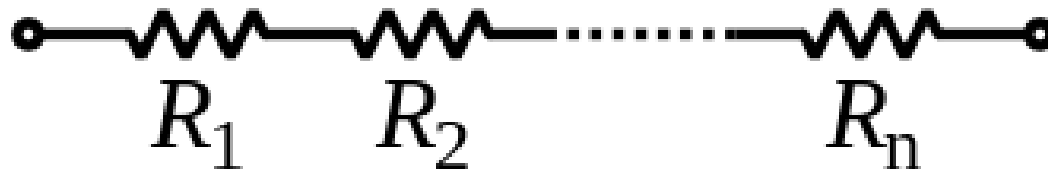
# Resistors in Series

- When resistors are in **SERIES**, the total resistance is the **SUM** of the individual resistances.




$$R_{\text{Total}} = R_1 + R_2 + R_3 + \dots + R_N$$

# Resistors in Series

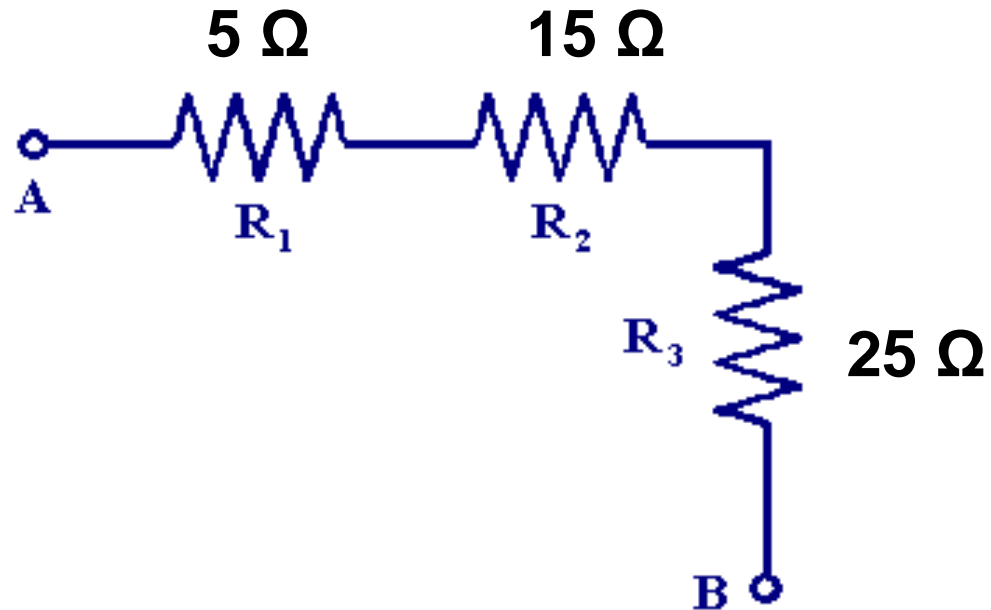


# Resistors in Series

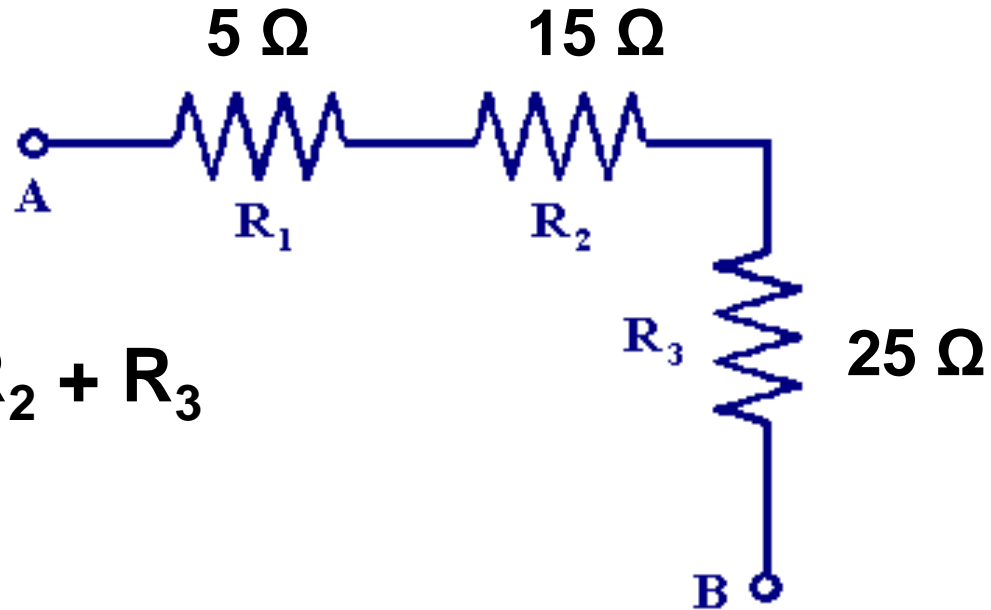

$$R_{\text{Total}} = R_1 + R_2 + R_3$$


# Resistors in Series

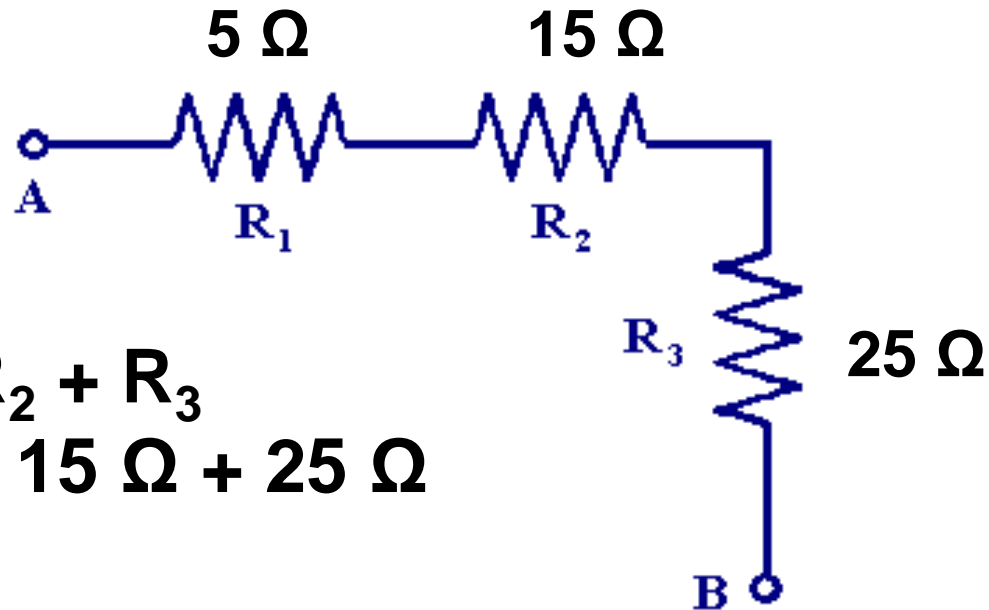

$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$R_{\text{Total}} = 5\ \Omega + 15\ \Omega + 25\ \Omega$$

# Resistors in Series

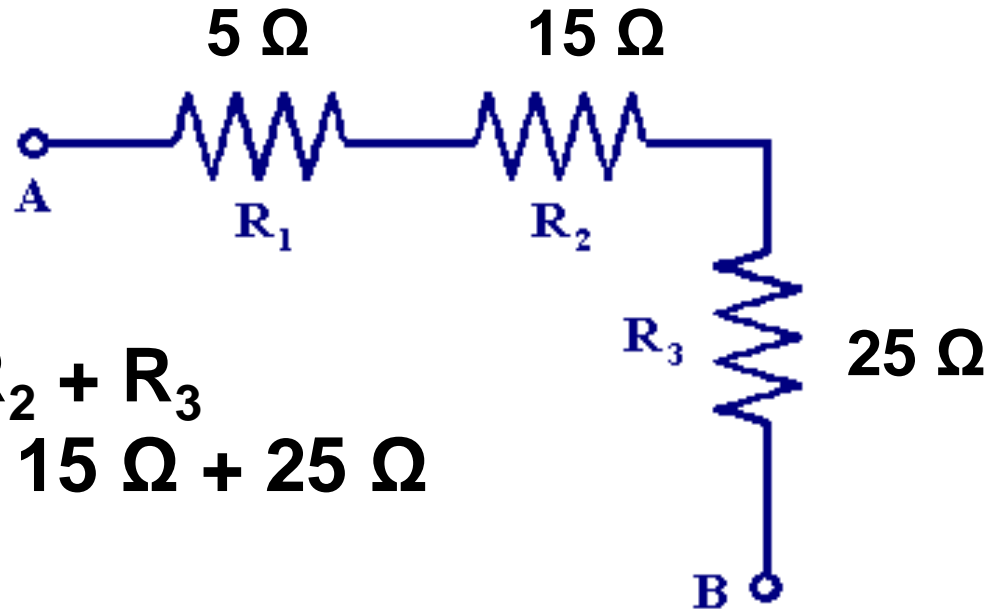

$$R_{\text{Total}} = R_1 + R_2 + R_3$$

$$R_{\text{Total}} = 5\ \Omega + 15\ \Omega + 25\ \Omega$$


$$R_{\text{Total}} = 45\ \Omega$$



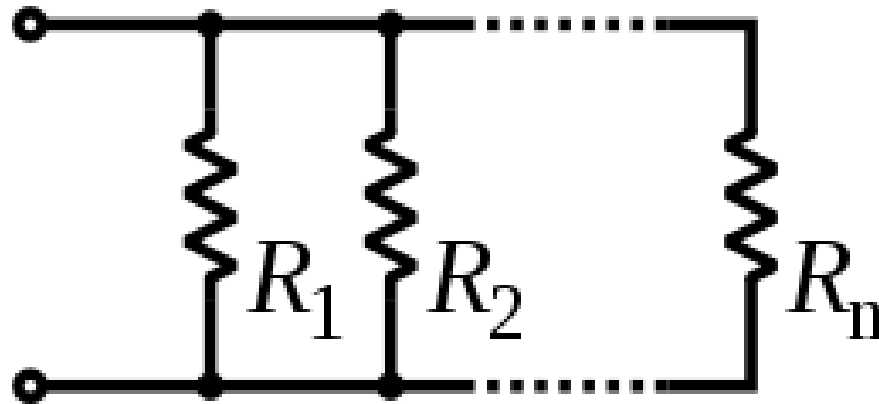
# Resistors in Parallel

- When resistors are in Parallel, the total resistance is given by the following equation:


$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$



# Resistors in Parallel

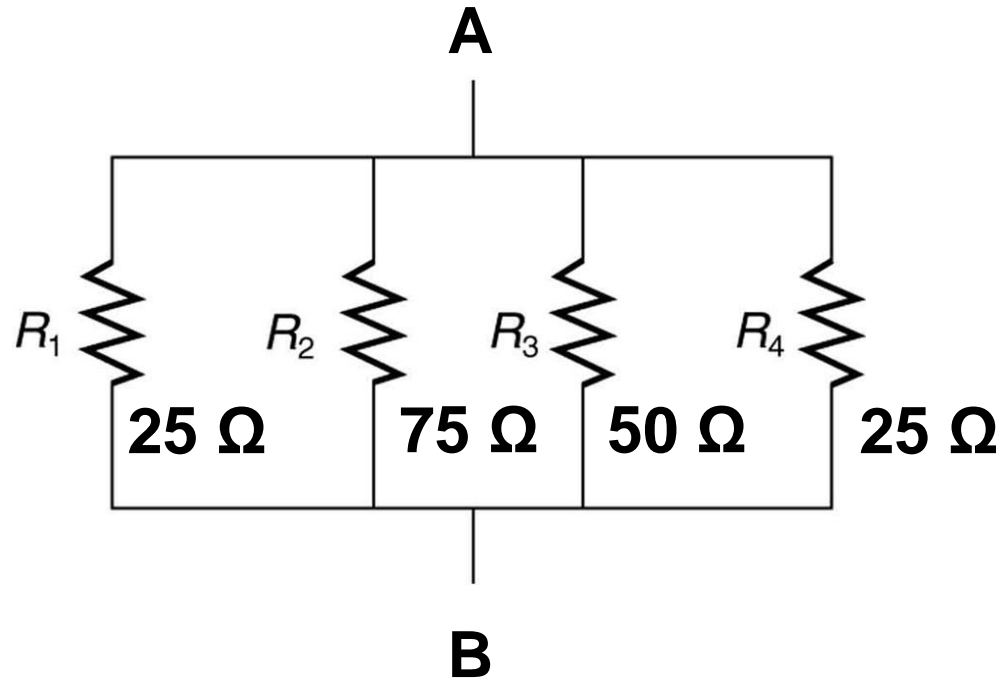


# Resistors in Parallel

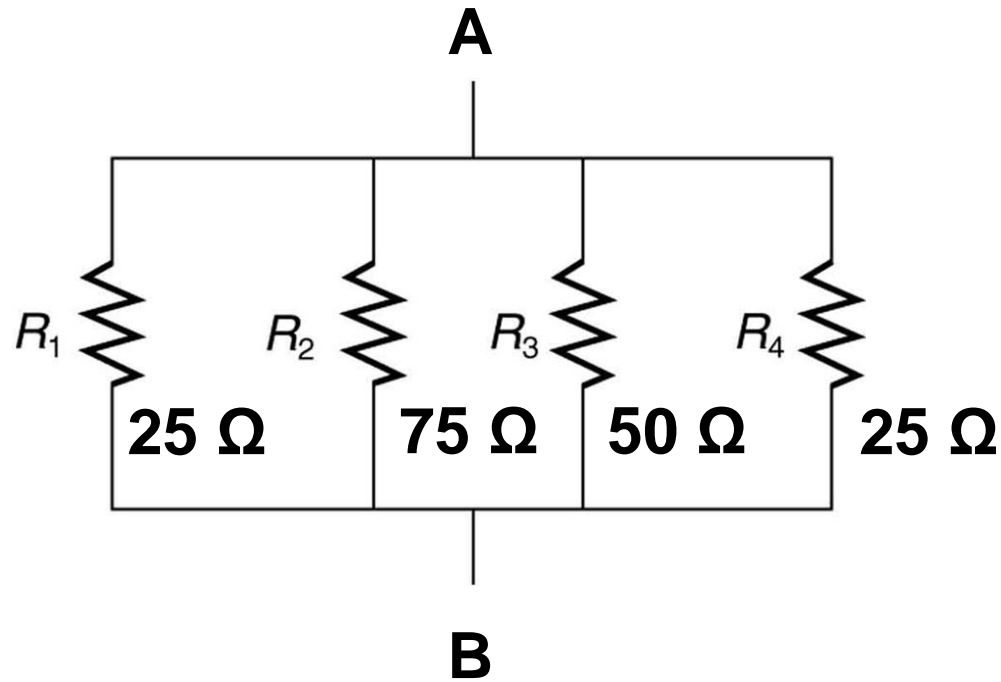

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$


# Resistors in Parallel

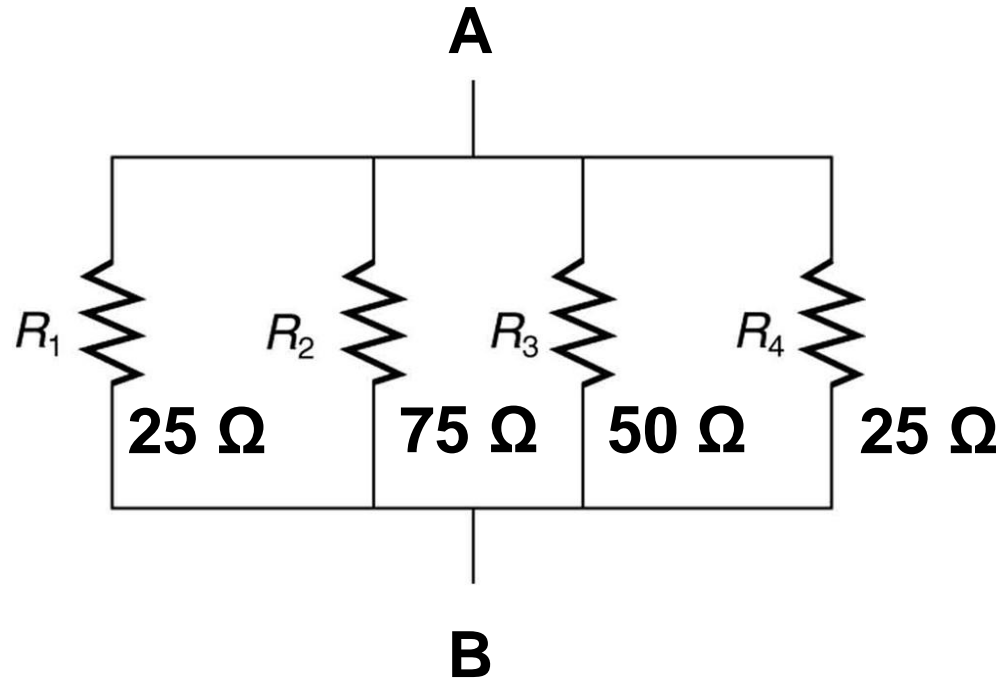

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_{\text{Total}}} = \frac{1}{25} + \frac{1}{75} + \frac{1}{50} + \frac{1}{25}$$


# Resistors in Parallel

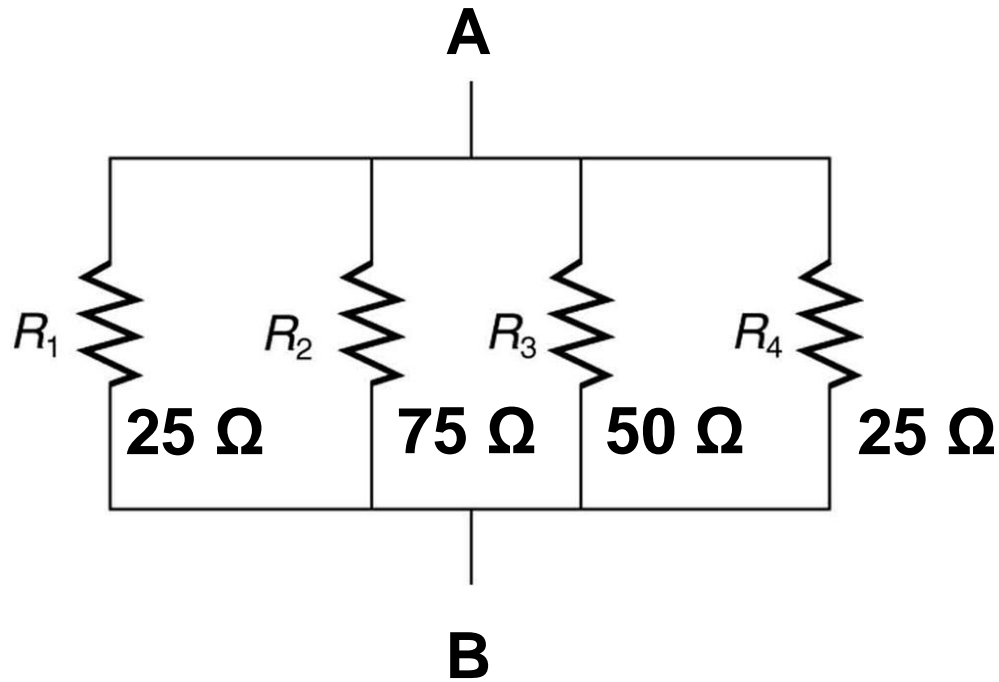

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_{\text{Total}}} = \frac{1}{25} + \frac{1}{75} + \frac{1}{50} + \frac{1}{25} = \frac{6}{150} + \frac{2}{150} + \frac{3}{150} + \frac{6}{150}$$

# Resistors in Parallel

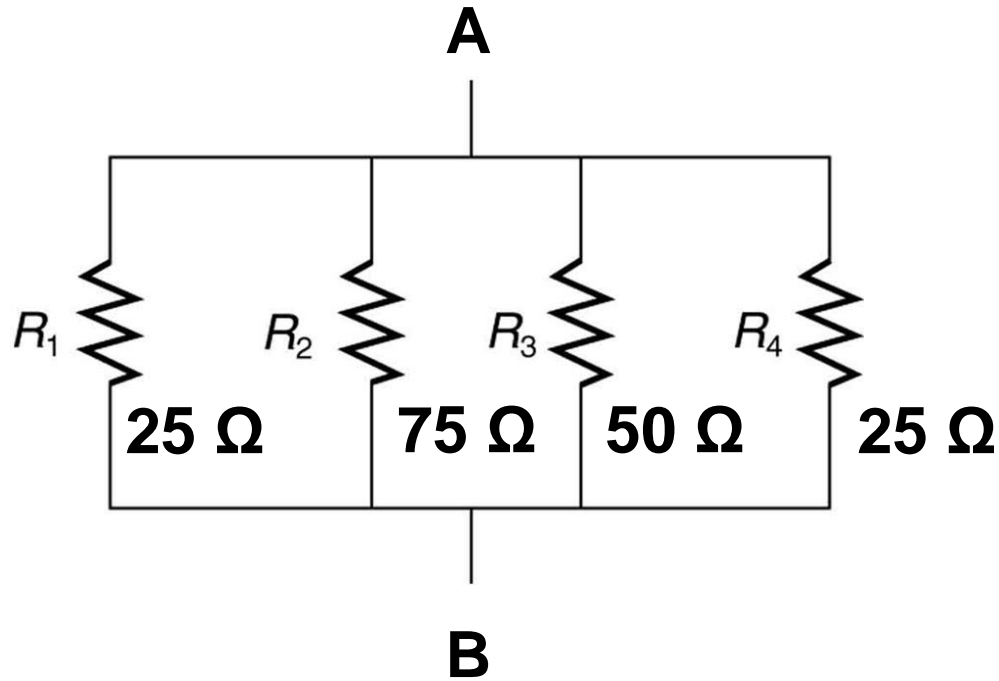


$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$

$$1/R_{\text{Total}} = 1/25 + 1/75 + 1/50 + 1/25 = 6/150 + 2/150 + 3/150 + 6/150$$

$$1/R_{\text{Total}} = 17/150\ \Omega$$

# Resistors in Parallel

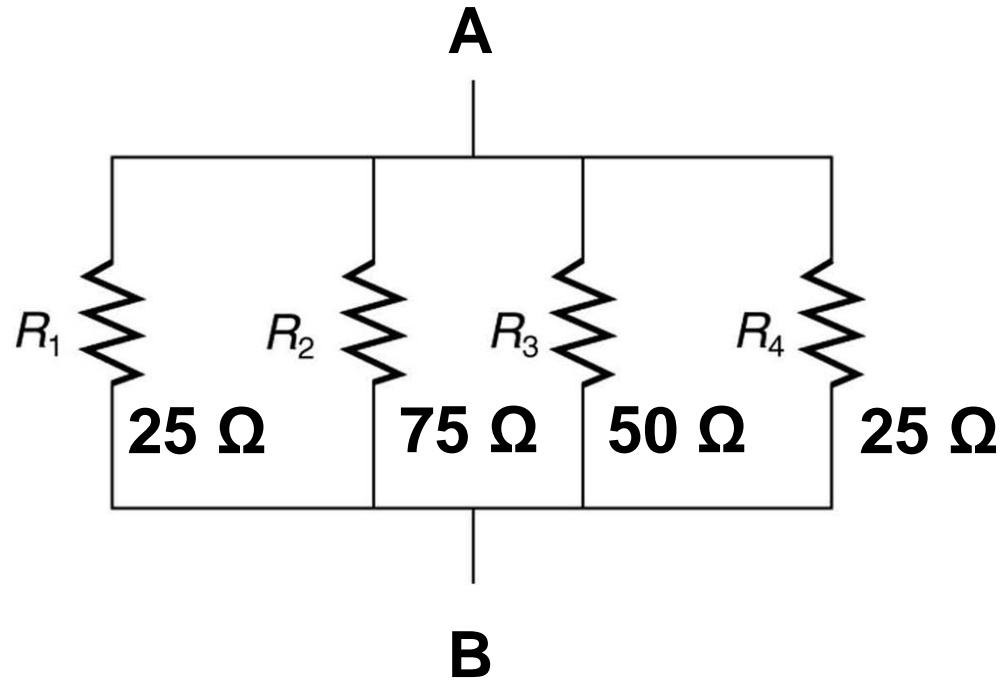

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$


$$1/R_{\text{Total}} = 1/25 + 1/75 + 1/50 + 1/25 = 6/150 + 2/150 + 3/150 + 6/150$$

$$1/R_{\text{Total}} = 17/150 \Omega$$


$$R_{\text{Total}} = 150/17 \Omega = 8.82 \Omega$$



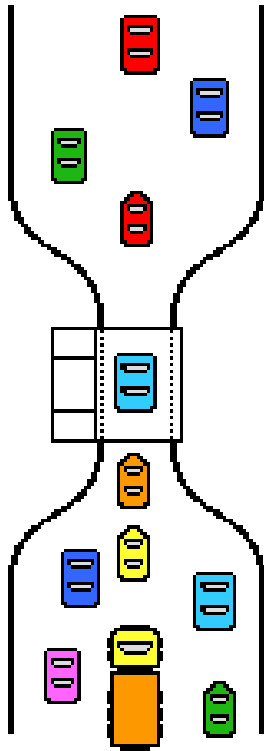
## Influencing the Flow Rate on a Tollway



**A Single Resistor**

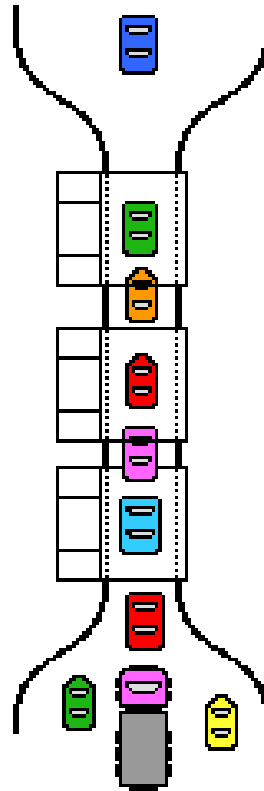


**Three Resistors  
Placed in Series**

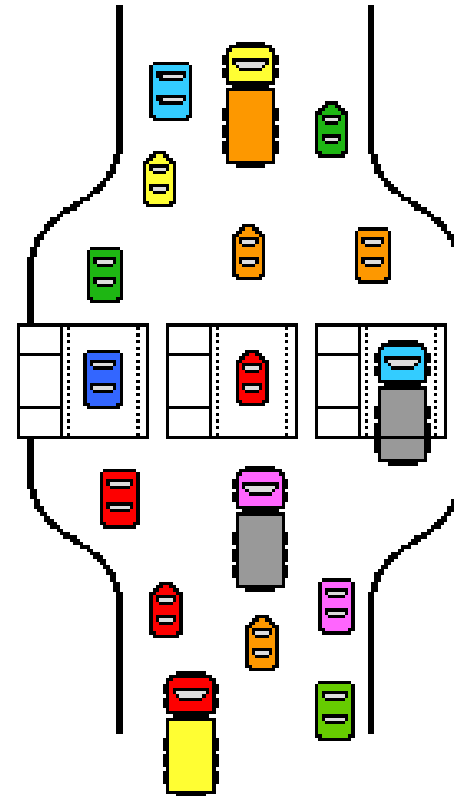

**Three Resistors  
Placed in Parallel**
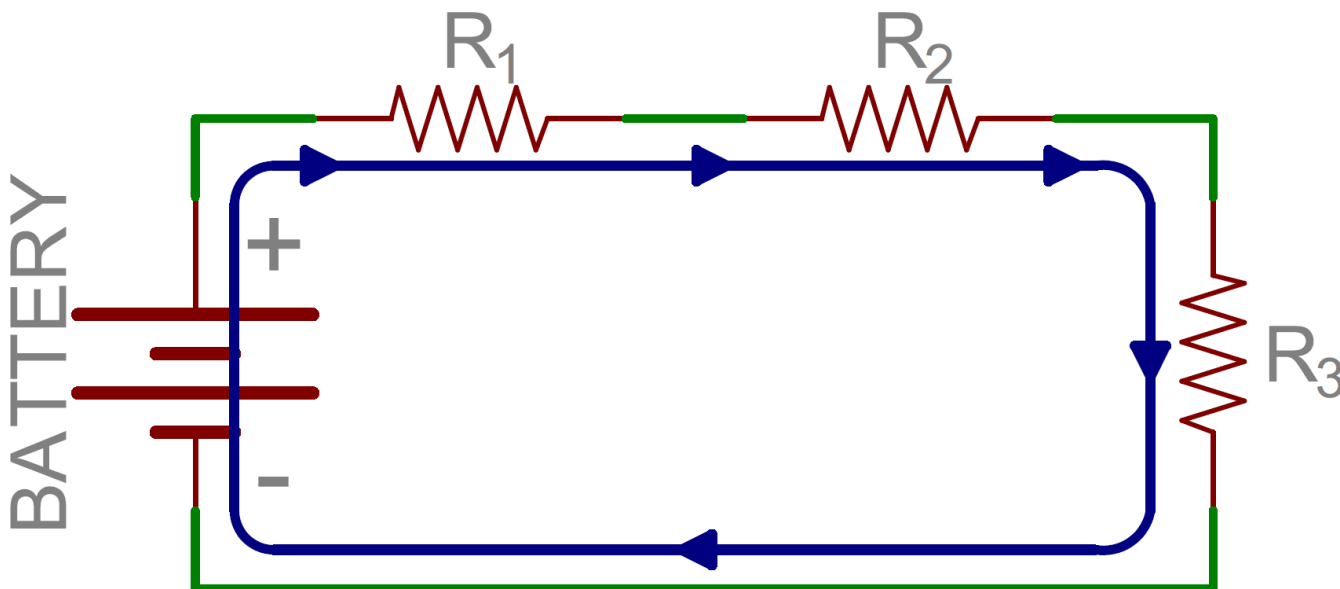
# Current in a Series Circuit


- The current through each resistor in a Series Circuit is identical.



$$I_{\text{Total}} = I_{R1} = I_{R2} = I_{R3}$$

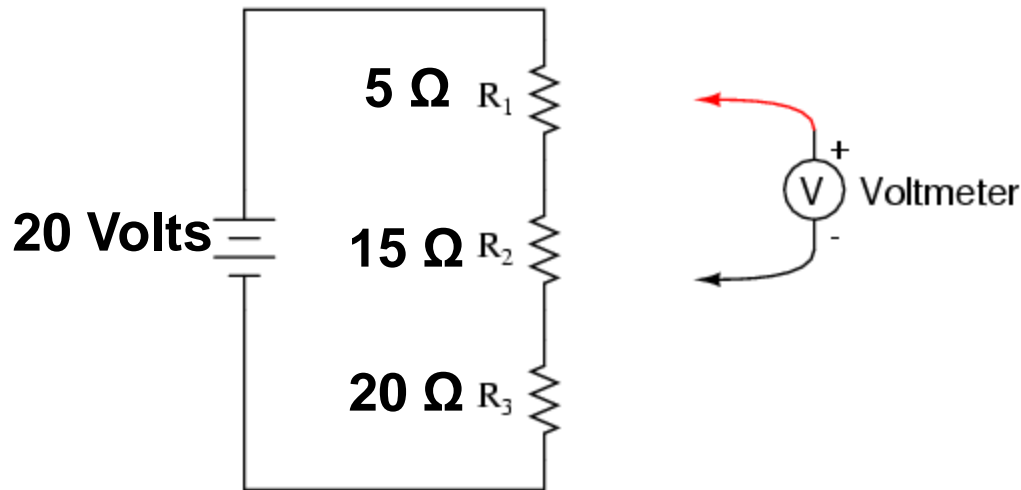
# Voltage in Series Circuits

- The sum of all the voltages across each resistor in a Series Circuit will equal the source voltage.




$$E_{\text{source}} = E_{R1} + E_{R2} + E_{R3}$$

# To Calculate Voltage Drop...

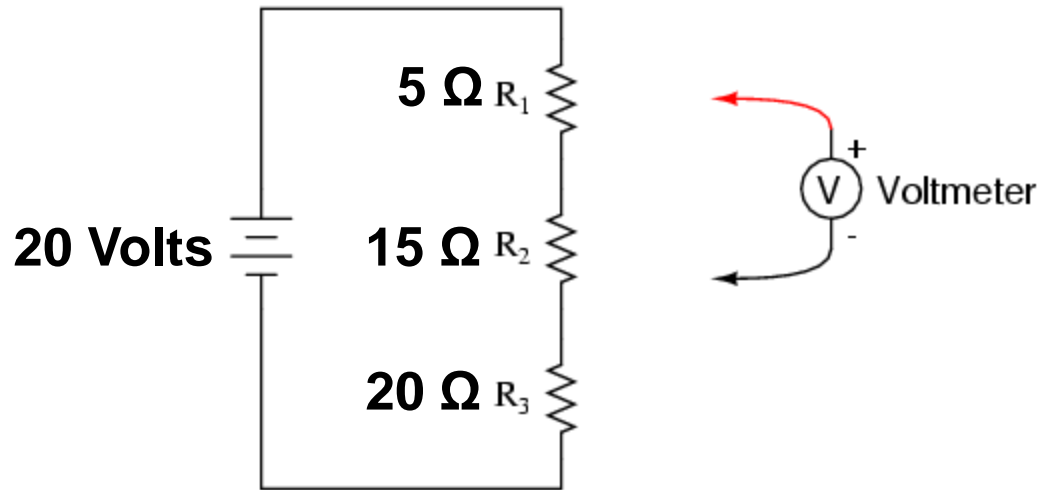



# 1. Determine Total Resistance

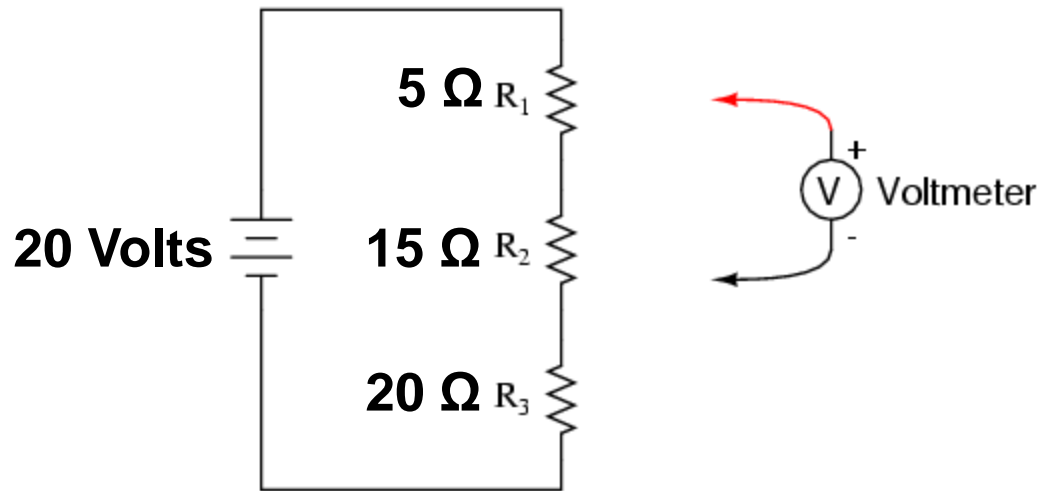

$$R_{\text{Total}} = R_1 + R_2 + R_3$$



$$R_{\text{Total}} =$$

# 1. Determine Total Resistance

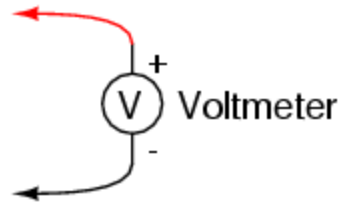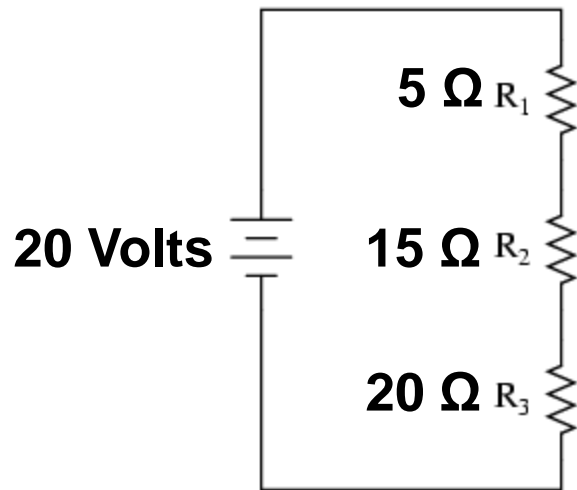

$$\begin{aligned}R_{\text{Total}} &= R_1 + R_2 + R_3 \\R_{\text{Total}} &= 5\ \Omega + 15\ \Omega + 20\ \Omega \\R_{\text{Total}} &= 40\ \Omega\end{aligned}$$

## 2. Determine Current

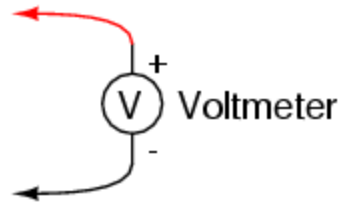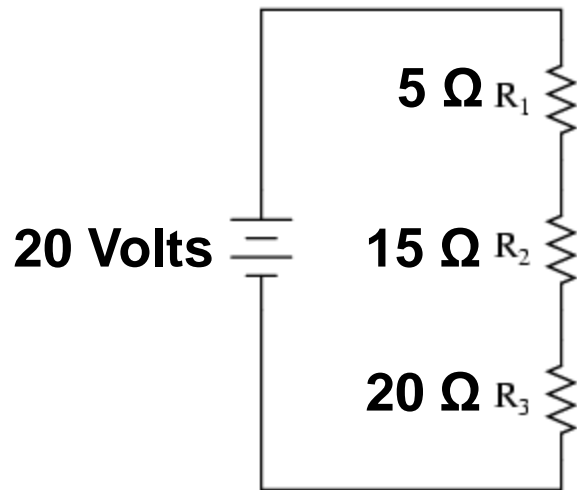


$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5\ \Omega + 15\ \Omega + 20\ \Omega$$
$$R_{\text{Total}} = 40\ \Omega$$

$$I = E / R$$

$$I =$$

## 2. Determine Current

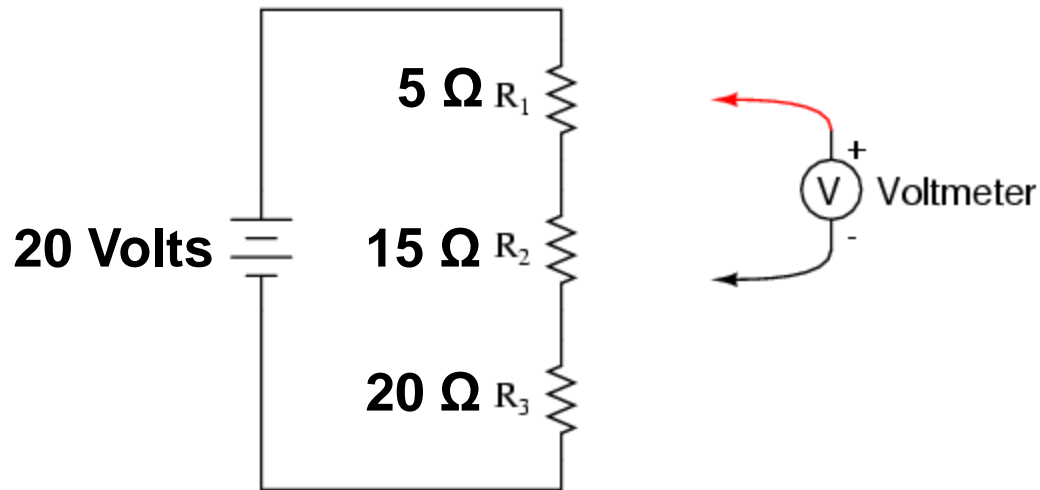

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$


$$I = E / R$$

$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$

$$I = 0.5 \text{ Amps}$$



# 3. Determine Voltage Drops

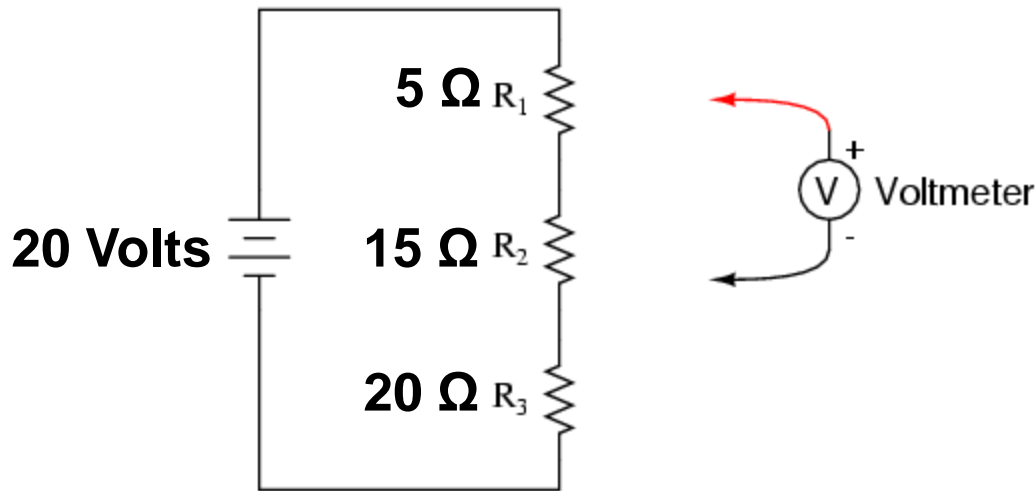

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$


$$I = E / R$$
$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$
$$I = 0.5 \text{ Amps}$$

$$E_{R1} = I \times R_1$$
$$E_{R1} =$$

$$E_{R2} = I \times R_2$$
$$E_{R2} =$$

$$E_{R3} = I \times R_3$$
$$E_{R3} =$$

# 3. Determine Voltage Drops

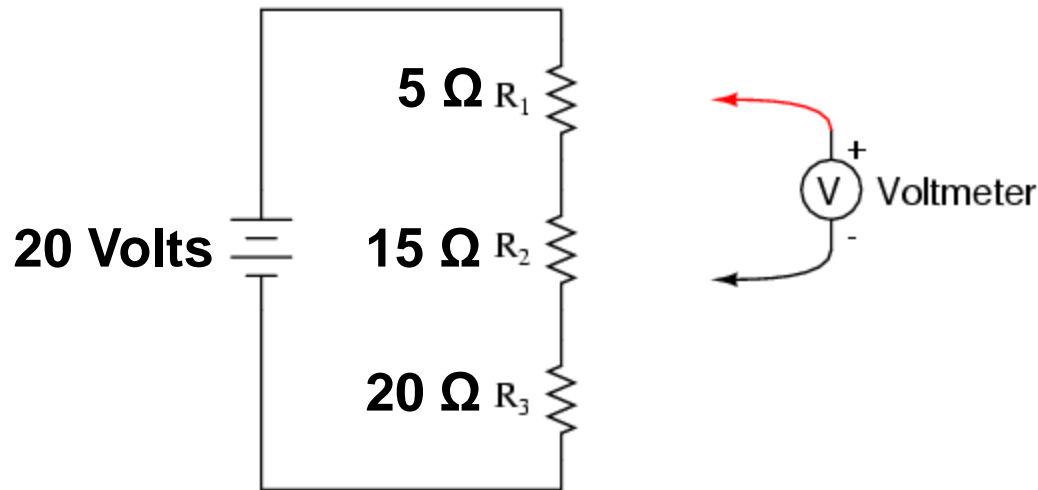

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$


$$I = E / R$$
$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$
$$I = 0.5 \text{ Amps}$$

$$E_{R1} = I \times R_1$$
$$E_{R1} = 0.5 \text{ Amps} \times 5 \Omega$$
$$E_{R1} = 2.5 \text{ Volts}$$

$$E_{R2} = I \times R_2$$
$$E_{R2} = 0.5 \text{ Amps} \times 15 \Omega$$
$$E_{R2} = 7.5 \text{ Volts}$$

$$E_{R3} = I \times R_3$$
$$E_{R3} = 0.5 \text{ Amps} \times 20 \Omega$$
$$E_{R3} = 10 \text{ Volts}$$

# 4. Check Your Results!

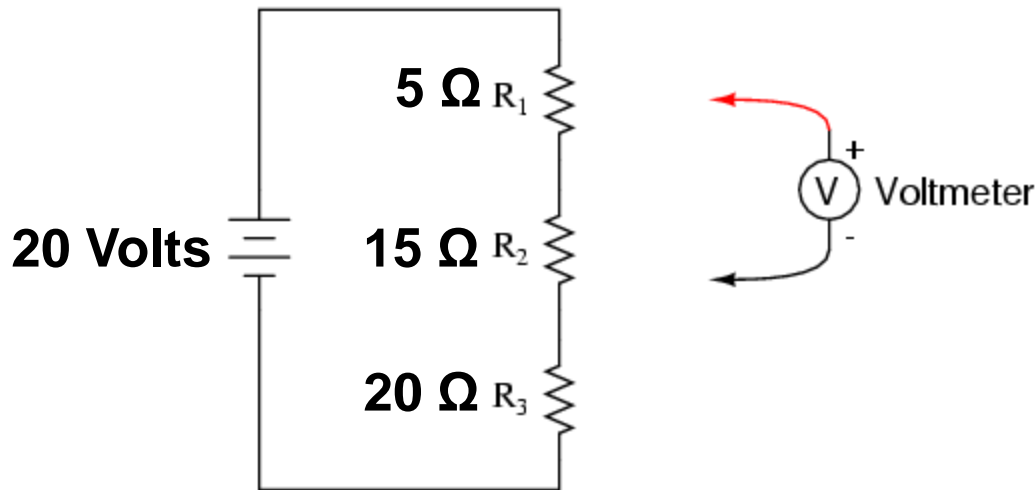

$$R_{\text{Total}} = R_1 + R_2 + R_3$$
$$R_{\text{Total}} = 5 \Omega + 15 \Omega + 20 \Omega$$
$$R_{\text{Total}} = 40 \Omega$$

$$I = E / R$$
$$I = 20 \text{ Volts} / 40 \text{ Ohms}$$
$$I = 0.5 \text{ Amps}$$

$$E_{R1} = I \times R_1$$
$$E_{R1} = 0.5 \text{ Amps} \times 5 \Omega$$
$$E_{R1} = 2.5 \text{ Volts}$$


$$E_{R2} = I \times R_2$$
$$E_{R2} = 0.5 \text{ Amps} \times 15 \Omega$$
$$E_{R2} = 7.5 \text{ Volts}$$

$$E_{R3} = I \times R_3$$
$$E_{R3} = 0.5 \text{ Amps} \times 20 \Omega$$
$$E_{R3} = 10 \text{ Volts}$$

$$E_{\text{source}} = E_{R1} + E_{R2} + E_{R3}$$
$$E_{\text{source}} = 2.5V + 7.5V + 10V = 20V$$
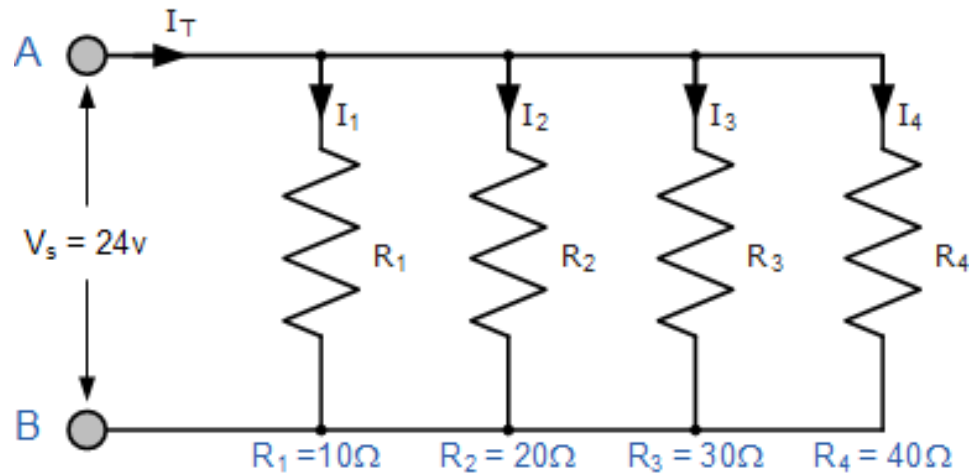
# Voltage in Parallel Circuits


- The voltage applied to each resistor in a Parallel Circuit is the same as the source voltage.



$$E_{\text{source}} = E_{R1} = E_{R2} = E_{R3} = E_{R4}$$

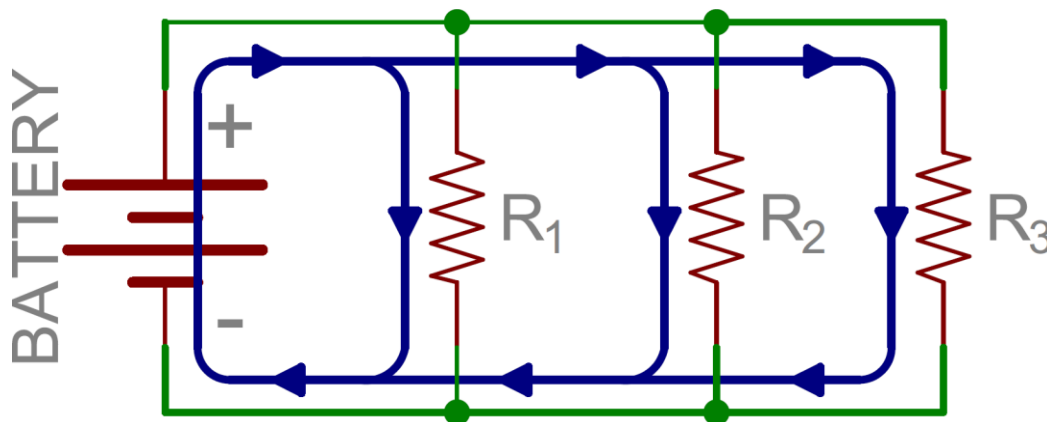
# Current in a Parallel Circuit

- The total current in a Parallel Circuit is divided among the resistors.
- The sum of the currents through each resistor equals the total current.




$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3}$$


# To Calculate Currents...

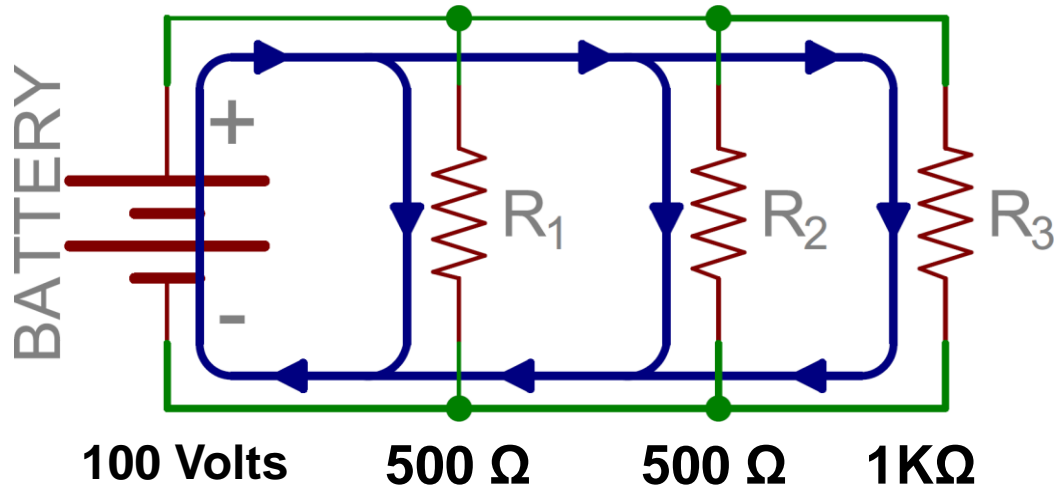

# Determine Equivalent Resistance

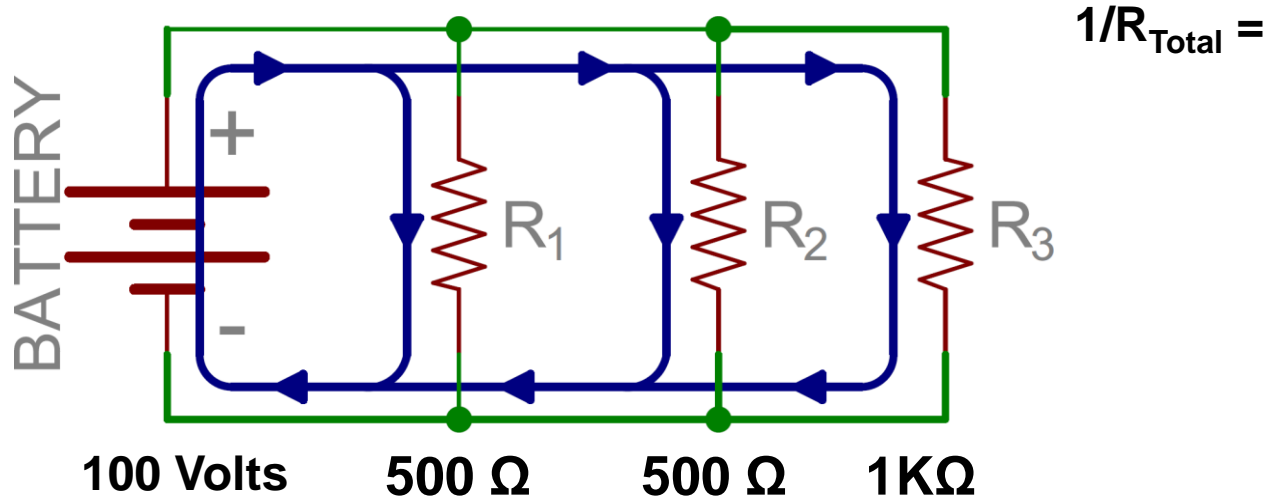


# Determine Equivalent Resistance

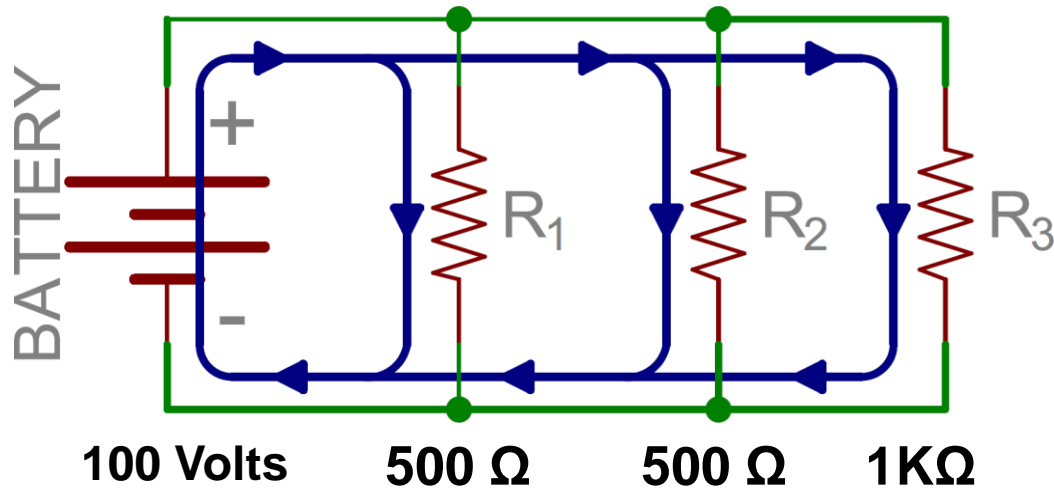

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
$$\frac{1}{R_{\text{Total}}} = \frac{1}{500} + \frac{1}{500} + \frac{1}{1\text{K}}$$




# Determine Equivalent Resistance

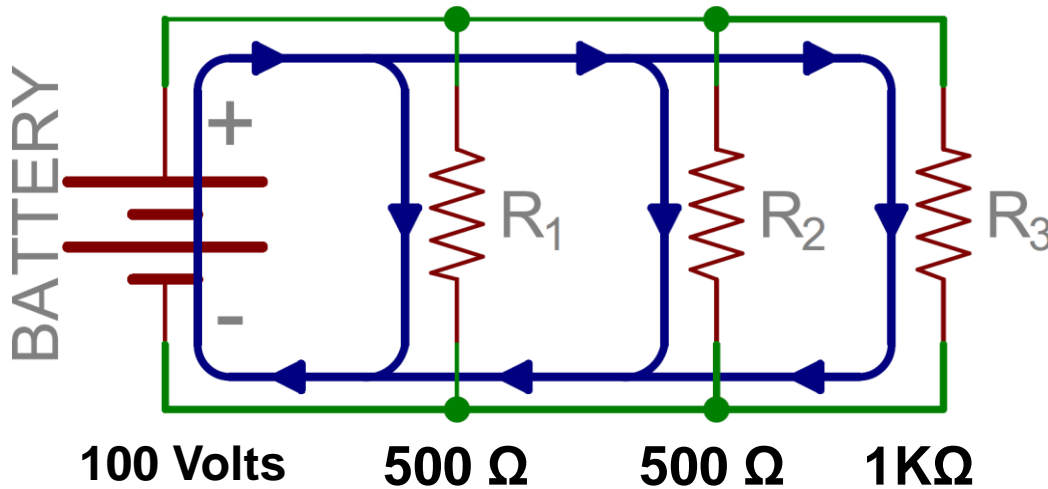

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1\text{K} \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

# Determine Equivalent Resistance

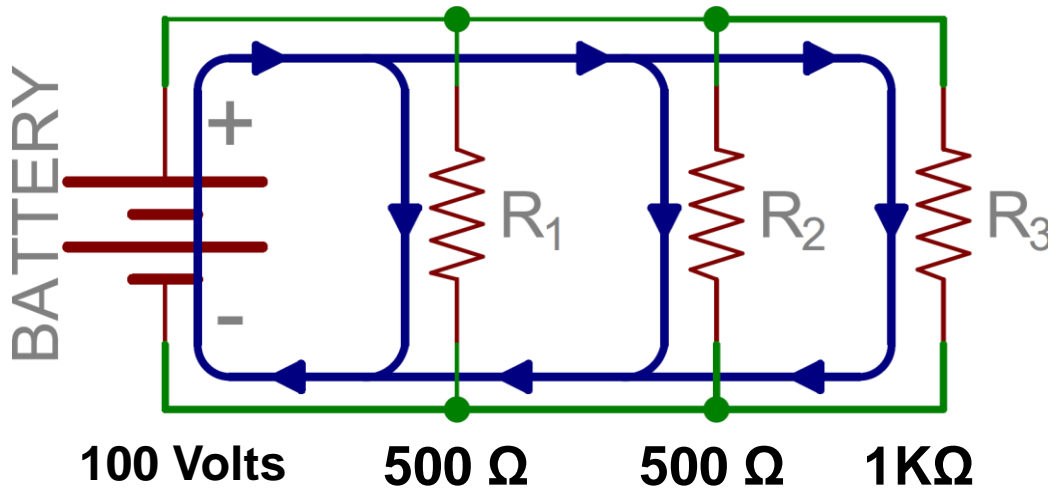

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3$$


$$1/R_{\text{Total}} = 1/500 + 1/500 + 1/1K$$

$$1/R_{\text{Total}} = 2/1000 + 2/1000 + 1/1000$$

$$1/R_{\text{Total}} = 5/1000$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

# Determine Overall Current

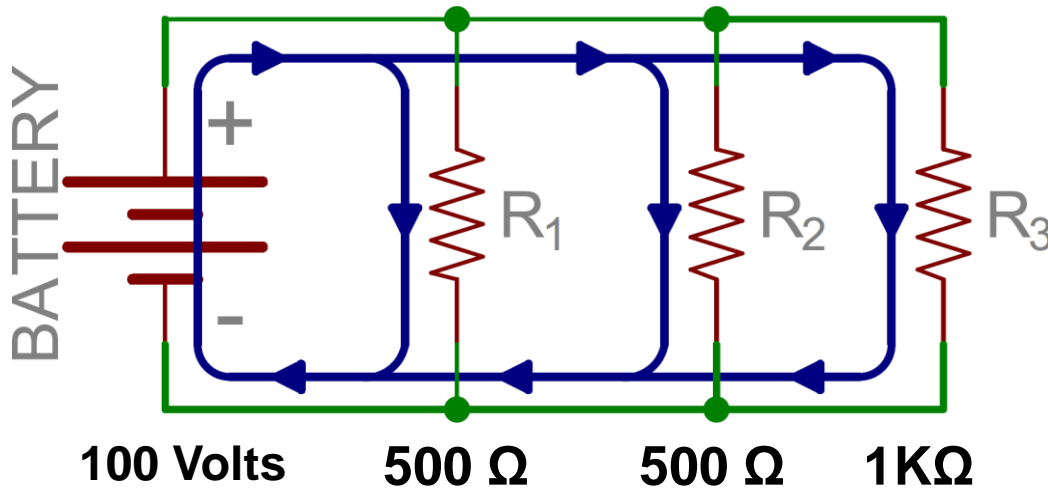


$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1\text{K} \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

I =

# Determine Overall Current

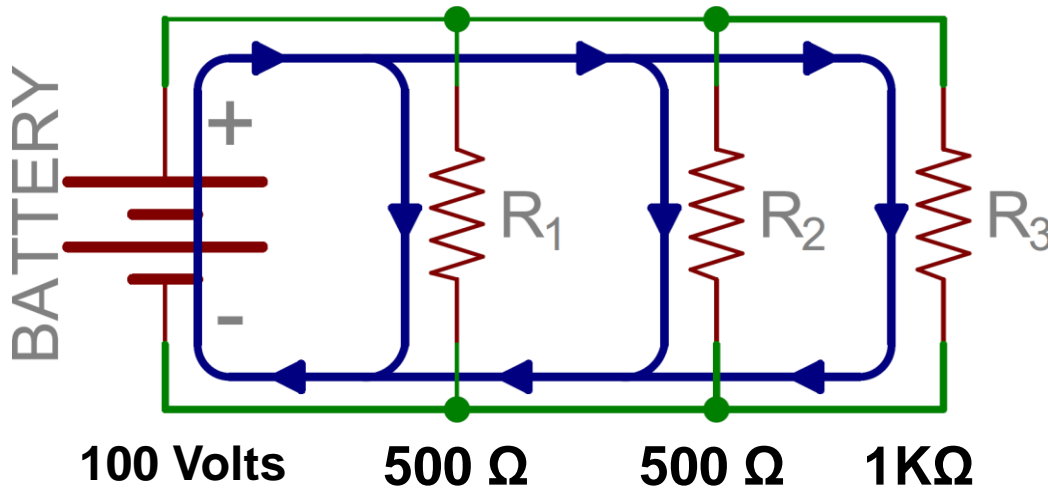

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_{\text{Total}} = 1/500 + 1/500 + 1/1K$$


$$1/R_{\text{Total}} = 2/1000 + 2/1000 + 1/1000$$

$$1/R_{\text{Total}} = 5/1000$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

# Determine Overall Current

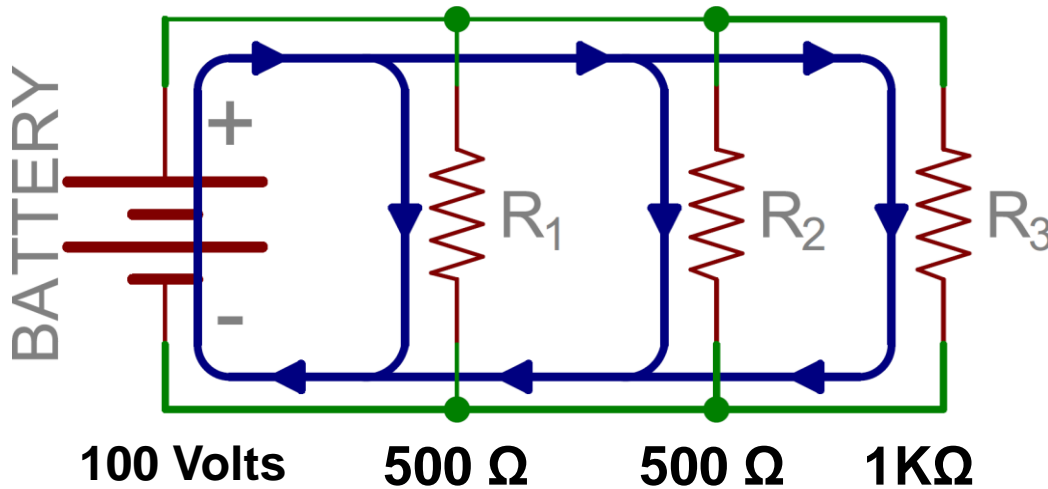

$$\begin{aligned} 1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\ 1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1\text{K} \\ 1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\ 1/R_{\text{Total}} &= 5/1000 \end{aligned}$$


$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

# Determine Individual Currents

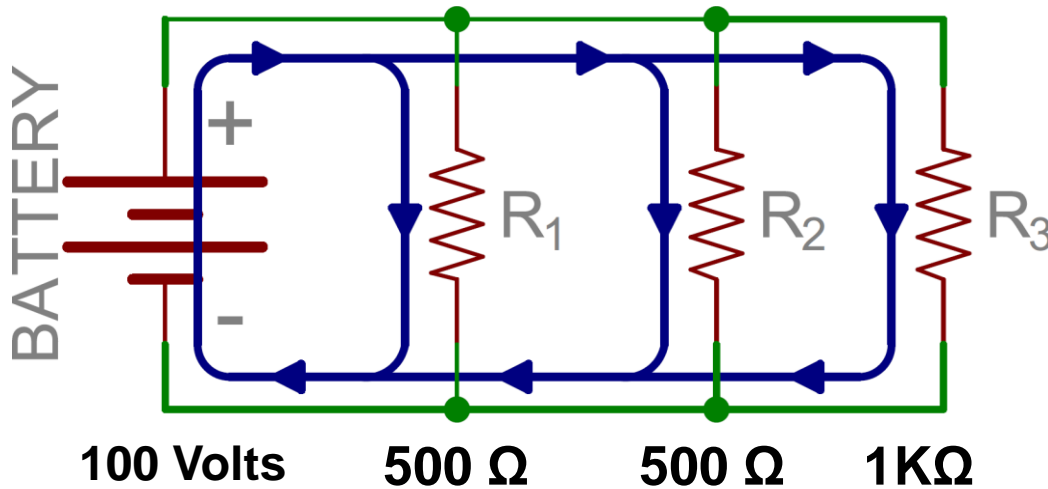

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1\text{K} \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200\ \Omega$$

$$I = E / R$$

$$I = 100\ \text{V} / 200\ \Omega$$


$$I = 0.5\ \text{Amps}$$

$$I_{R1} =$$

$$I_{R2} =$$

$$I_{R3} =$$

# Determine Individual Currents

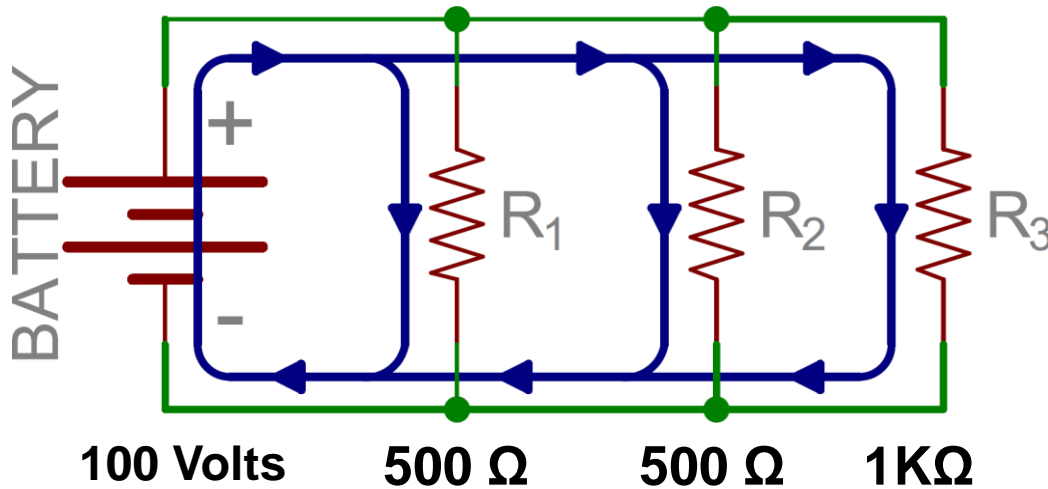

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$


$$\begin{aligned}I &= E / R \\I &= 100 \text{ V} / 200 \Omega \\I &= 0.5 \text{ Amps}\end{aligned}$$

$$I_{R1} = E / R_1$$

$$I_{R2} = E / R_2$$

$$I_{R3} = E / R_3$$

# Determine Individual Currents

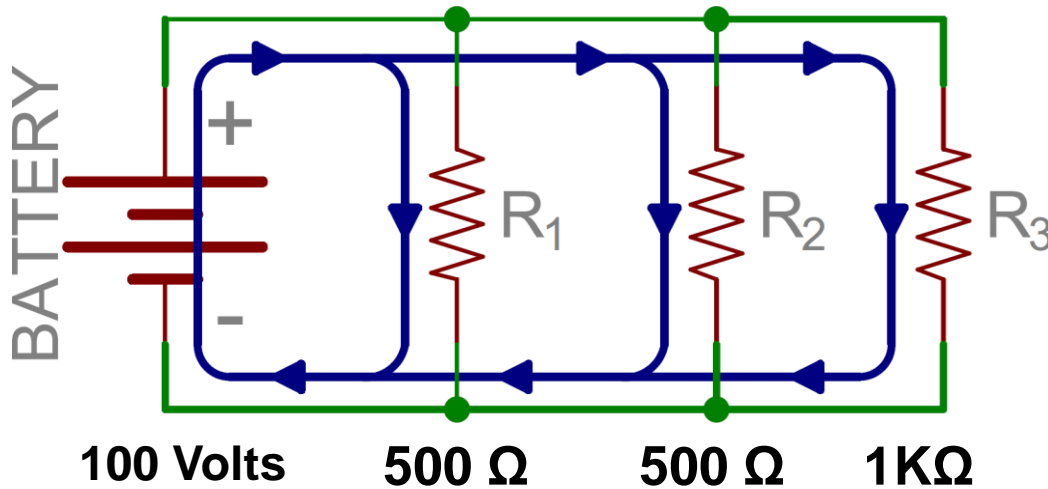

$$1/R_{\text{Total}} = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_{\text{Total}} = 1/500 + 1/500 + 1/1K$$

$$1/R_{\text{Total}} = 2/1000 + 2/1000 + 1/1000$$

$$1/R_{\text{Total}} = 5/1000$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} =$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$

$$I_{R2} =$$


$$I_{R3} = E / R_3$$

$$I_{R3} = 100 \text{ V} / 1000 \Omega$$

$$I_{R3} =$$



# Determine Individual Currents

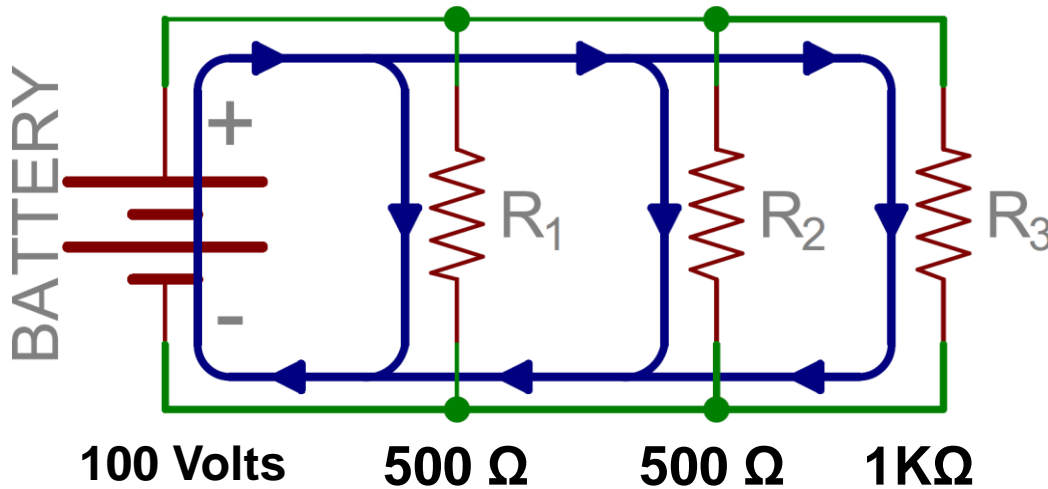

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} = 0.2 \text{ Amps}$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$


$$I_{R2} = 0.2 \text{ Amps}$$

$$I_{R3} = E / R_3$$

$$I_{R3} = 100 \text{ V} / 1000 \Omega$$

$$I_{R3} = 0.1 \text{ Amps}$$

# Check your Answer!

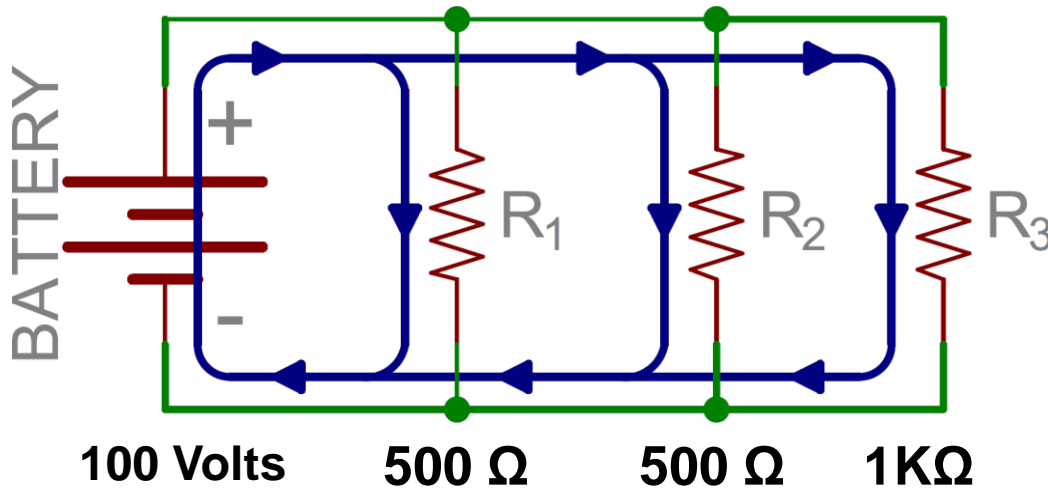

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} = 0.2 \text{ Amps}$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$

$$I_{R2} = 0.2 \text{ Amps}$$


$$I_{R3} = E / R_3$$

$$I_{R3} = 100 \text{ V} / 1000 \Omega$$

$$I_{R3} = 0.1 \text{ Amps}$$

$$I_{\text{Total}} =$$

# Check your Answer!

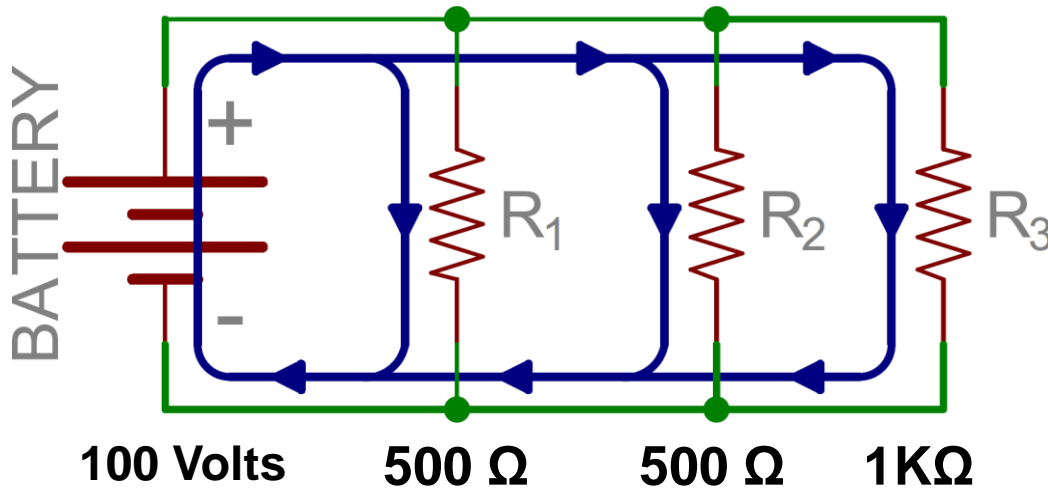

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} = 0.2 \text{ Amps}$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$

$$I_{R2} = 0.2 \text{ Amps}$$


$$I_{R3} = E / R_3$$

$$I_{R3} = 100 \text{ V} / 1000 \Omega$$

$$I_{R3} = 0.1 \text{ Amps}$$

$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3} =$$

# Check your Answer!

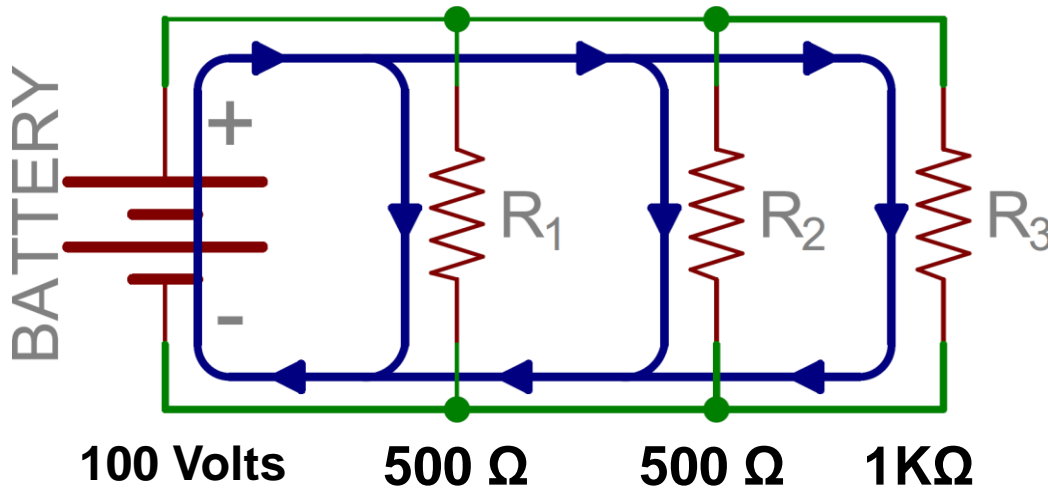

$$\begin{aligned}1/R_{\text{Total}} &= 1/R_1 + 1/R_2 + 1/R_3 \\1/R_{\text{Total}} &= 1/500 + 1/500 + 1/1K \\1/R_{\text{Total}} &= 2/1000 + 2/1000 + 1/1000 \\1/R_{\text{Total}} &= 5/1000\end{aligned}$$

$$R_{\text{Total}} = 1000/5 = 200 \Omega$$

$$I = E / R$$

$$I = 100 \text{ V} / 200 \Omega$$

$$I = 0.5 \text{ Amps}$$

$$I_{R1} = E / R_1$$

$$I_{R1} = 100 \text{ V} / 500 \Omega$$

$$I_{R1} = 0.2 \text{ Amps}$$

$$I_{R2} = E / R_2$$

$$I_{R2} = 100 \text{ V} / 500 \Omega$$

$$I_{R2} = 0.2 \text{ Amps}$$


$$I_{R3} = E / R_3$$

$$I_{R3} = 100 \text{ V} / 1000 \Omega$$


$$I_{R3} = 0.1 \text{ Amps}$$

$$I_{\text{Total}} = I_{R1} + I_{R2} + I_{R3} = 0.2 + 0.2 + 0.1 = 0.5 \text{ Amp}$$


# Series Parallel Combinations

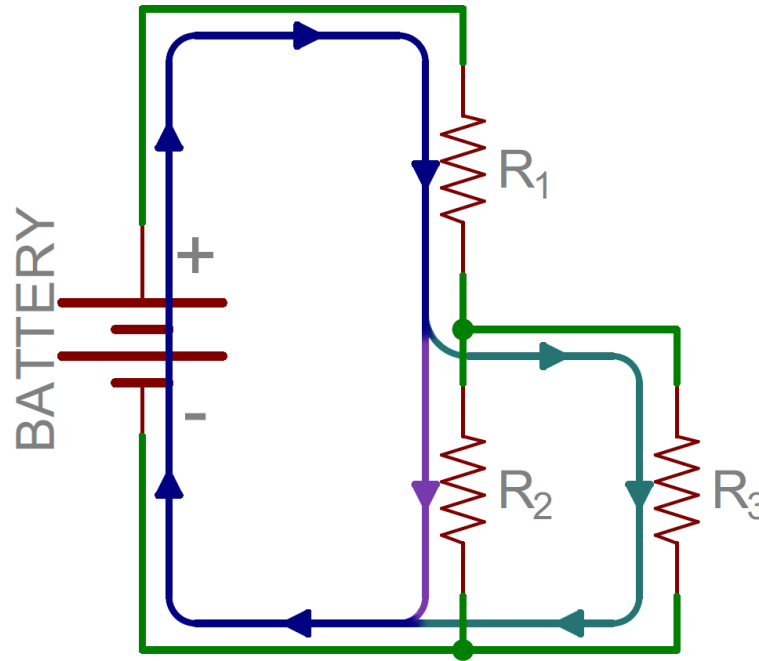


# Series Parallel Combinations

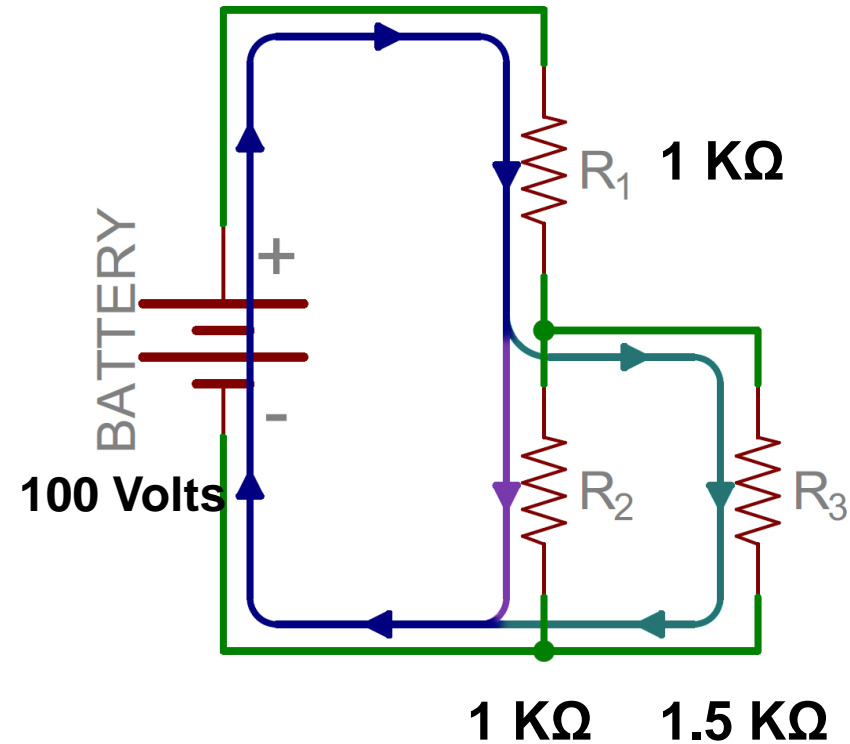

# Series Parallel Combinations

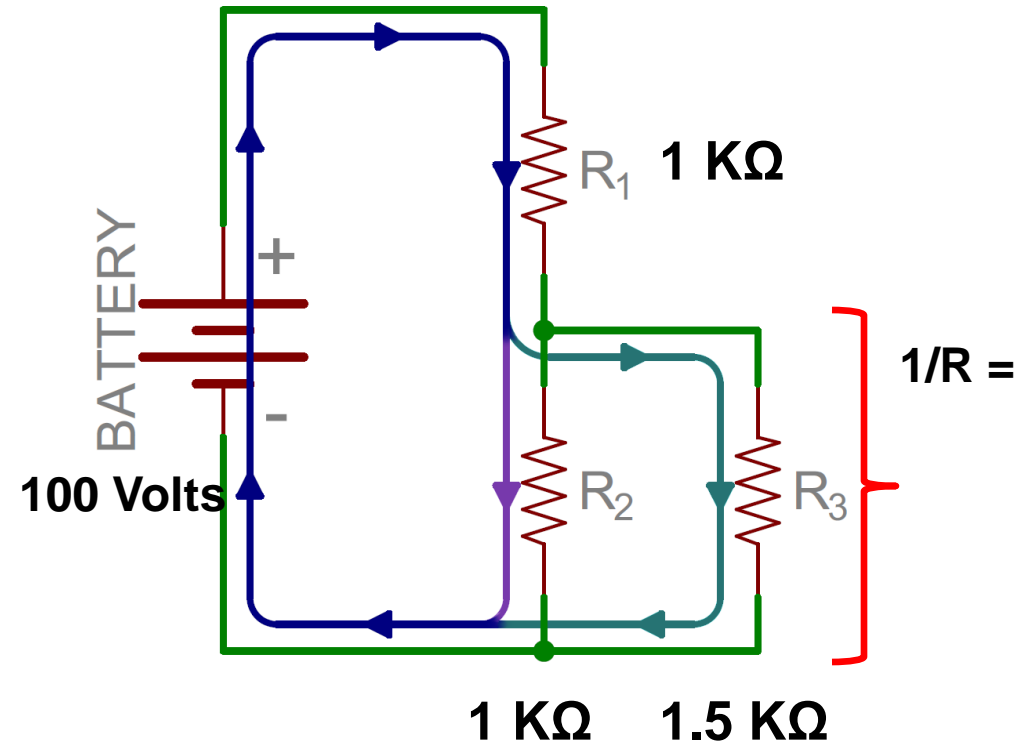


# Series Parallel Combinations

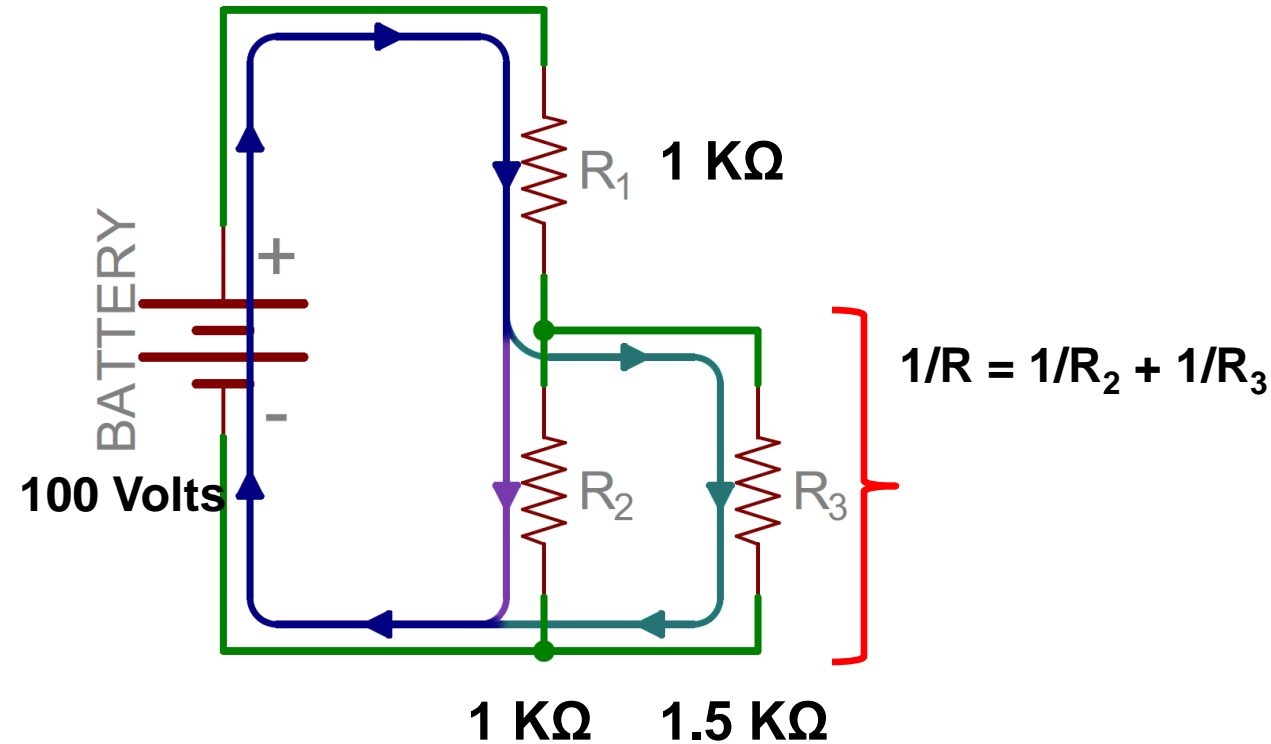





# Series Parallel Combinations

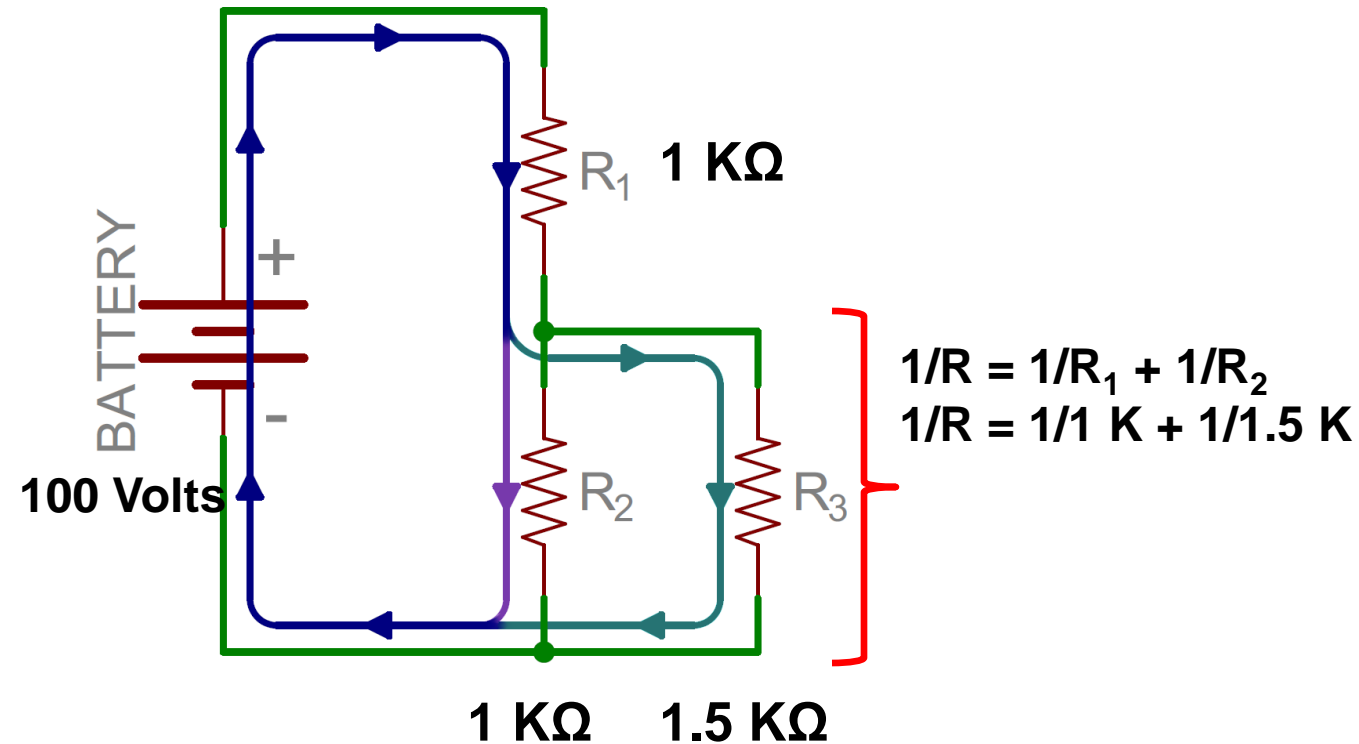


# Series Parallel Combinations

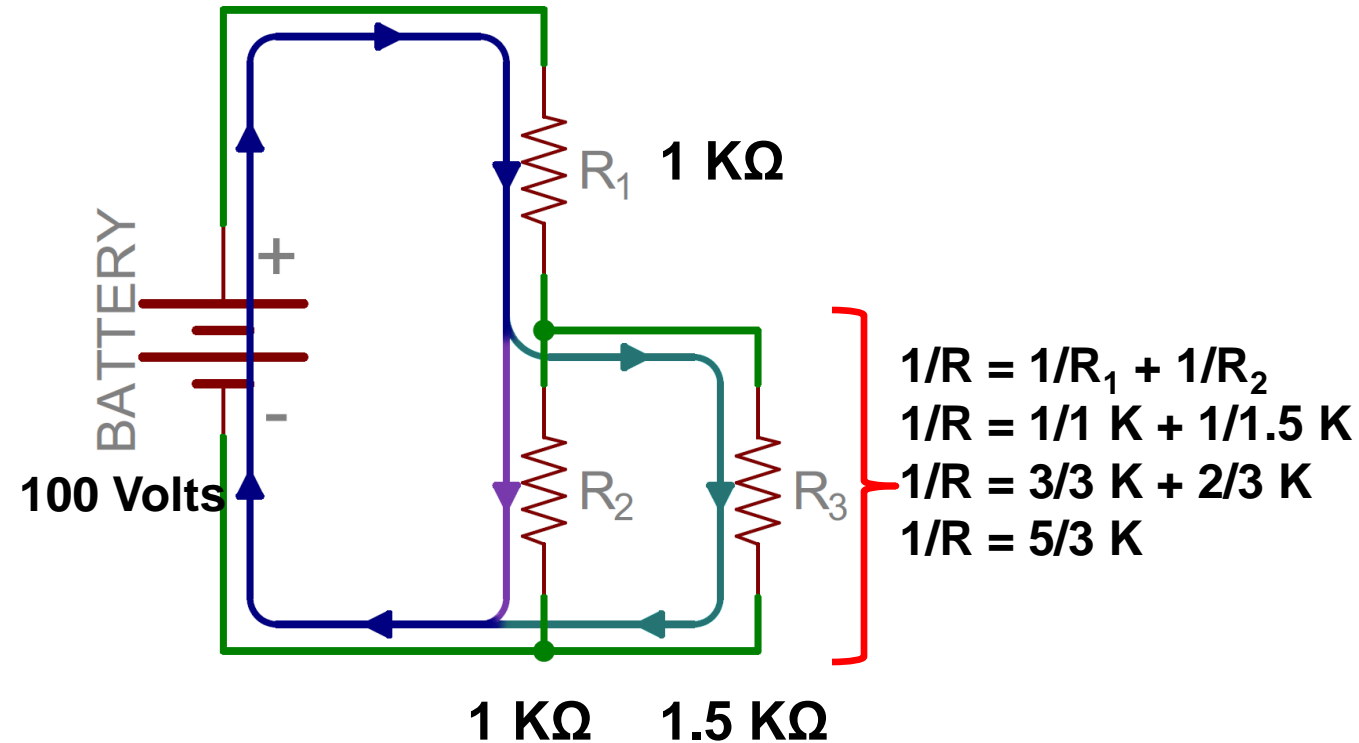


# Series Parallel Combinations

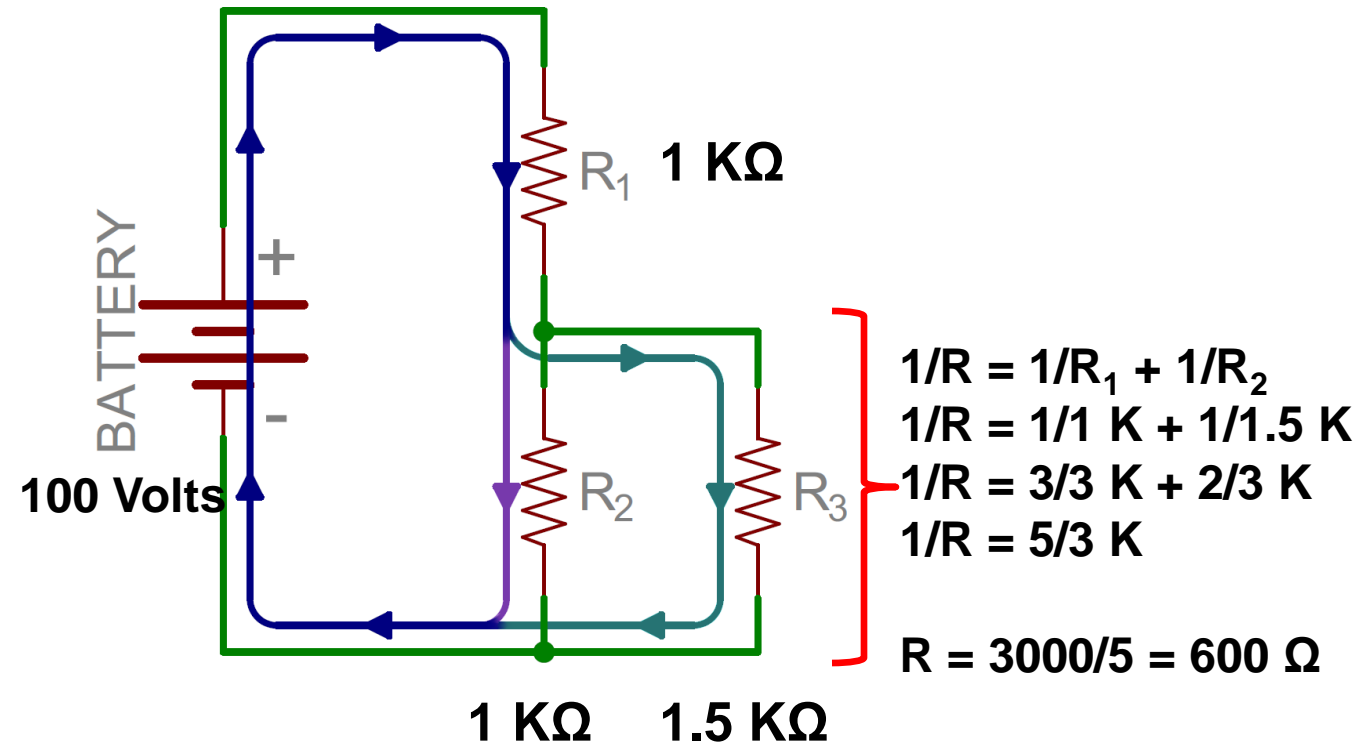


# Series Parallel Combinations

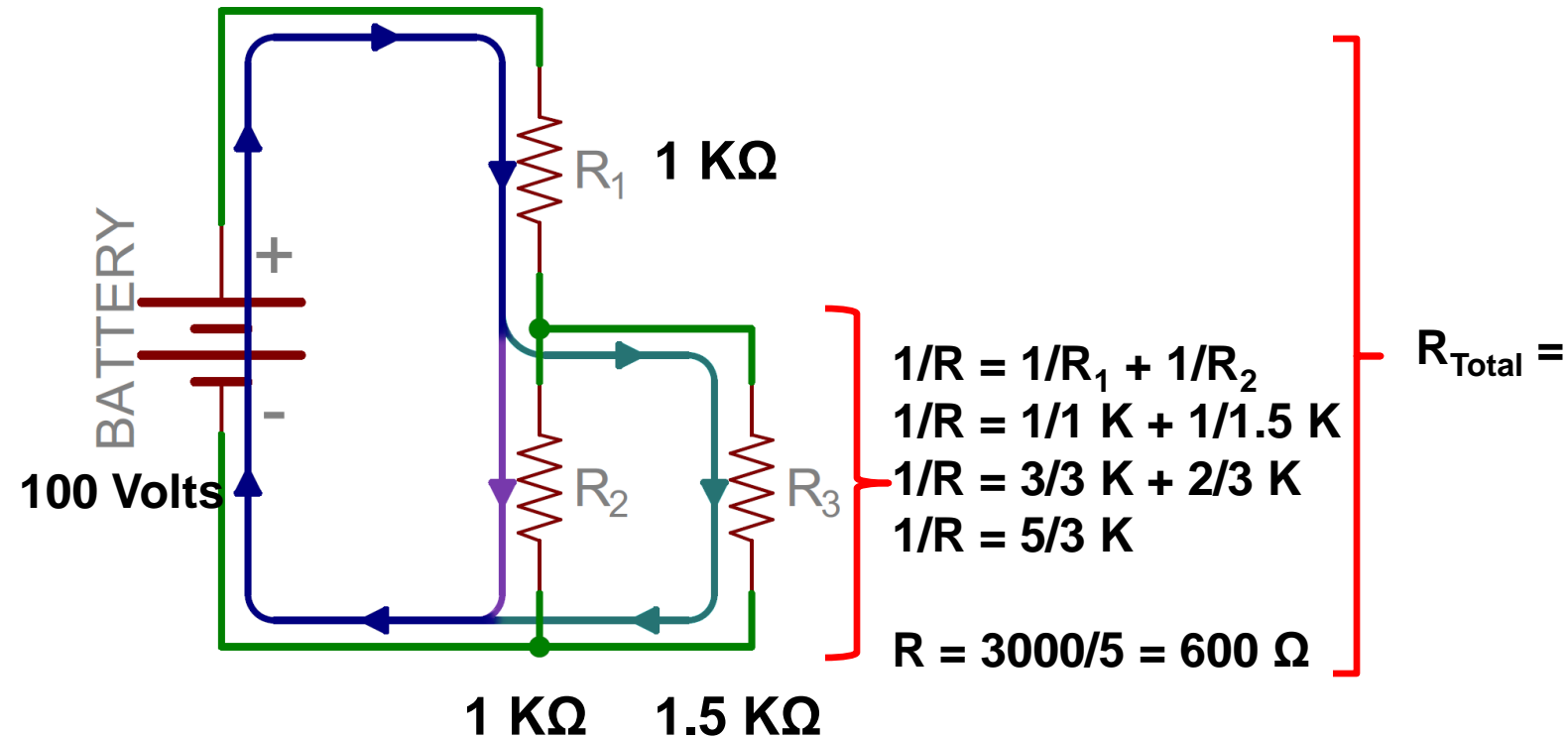


# Series Parallel Combinations

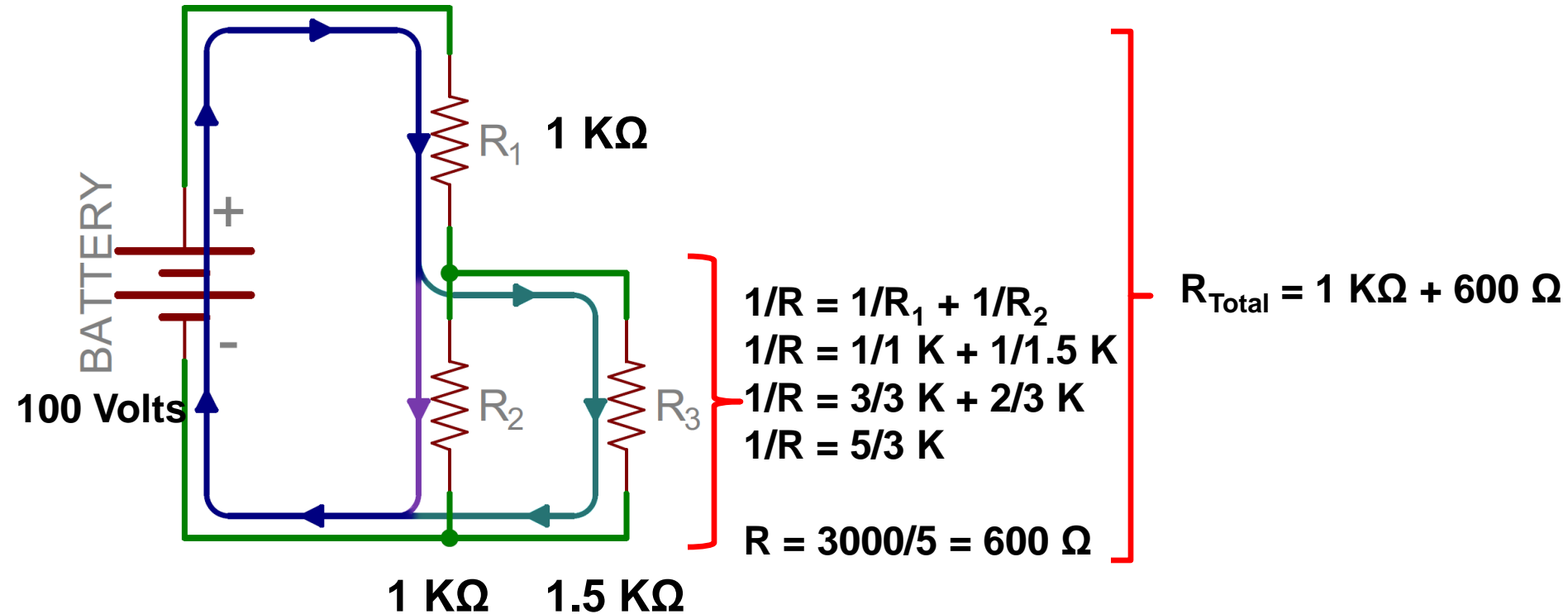

# Series Parallel Combinations

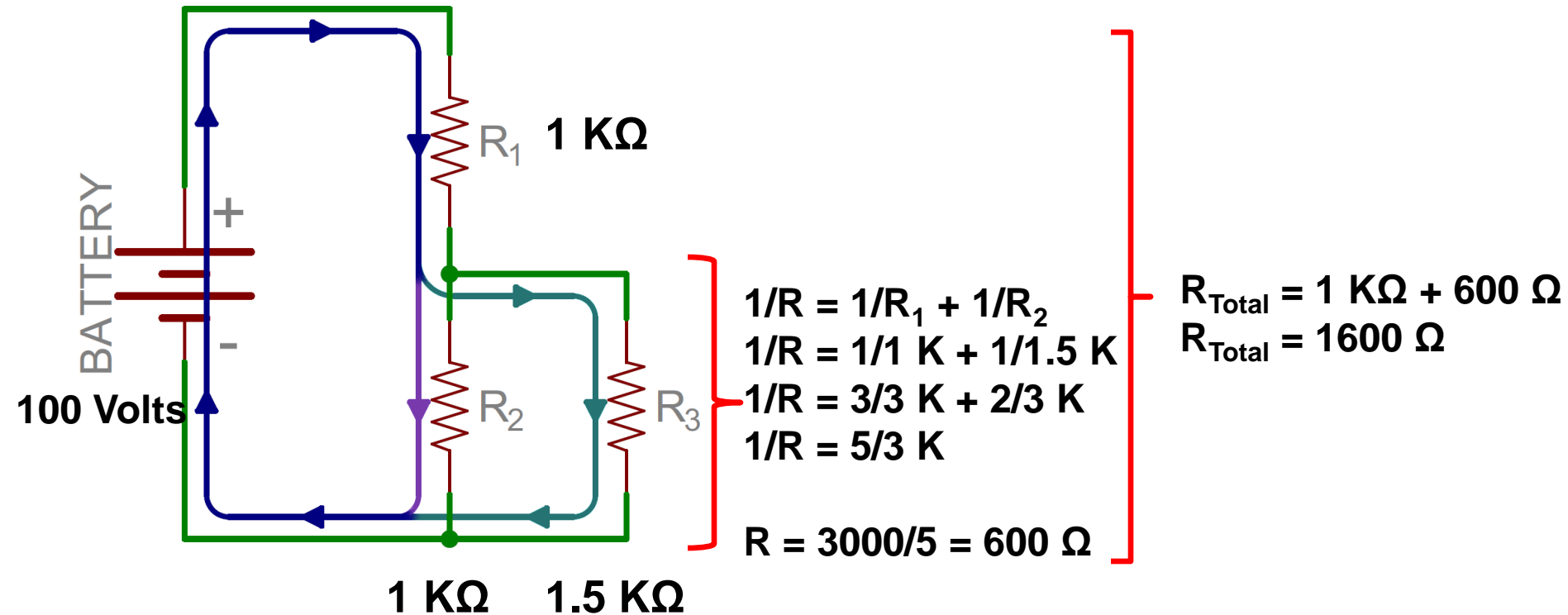

# Series Parallel Combinations

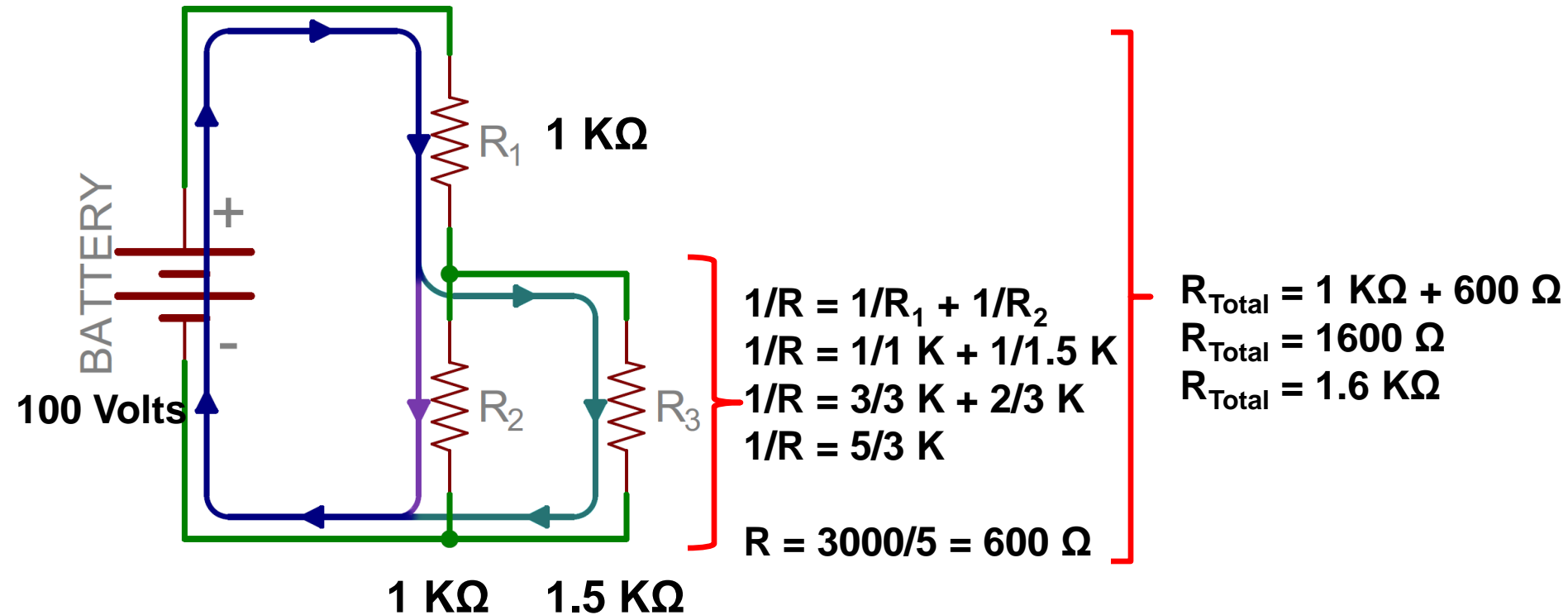

# Energy and Power

- Energy is the ability to do work.
- Two types: Kinetic and Potential
- A cell has Potential Energy – it stores chemical energy that can be released to do work.
- When electrons move against a resistance, work is done.
- The rate at which work is done is called Power




# Power

- Basic unit of Power is the Watt, abbreviated W.
- In electrical systems, we can calculate power if we know any two of
  - Voltage;
  - Current; or
  - Resistance.


$$P = E \times I = E^2 / R = I^2 \times R$$

# Calculating Power #1

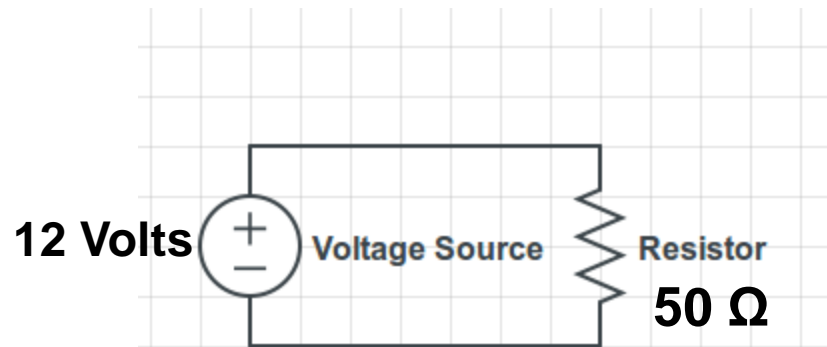


$$P = E \times I = E^2 / R = I^2 \times R$$

# Calculating Power #1

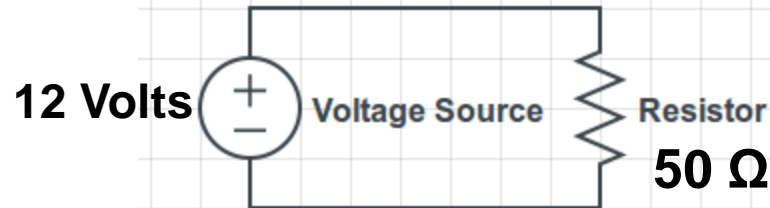

$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = E^2 / R$$

# Calculating Power #1

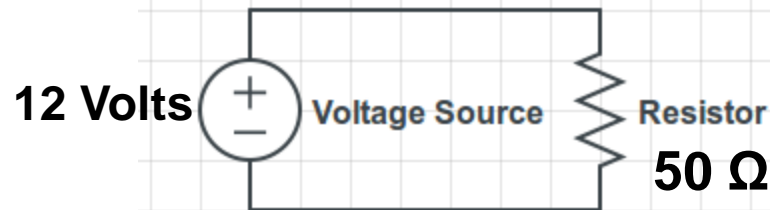

$$P = E \times I = E^2 / R = I^2 \times R$$


$$P = E^2 / R$$

$$P = 12^2 / 50$$

$$P = 144 / 50$$


$$P = 2.88 \text{ Watts}$$

# Calculating Power #2

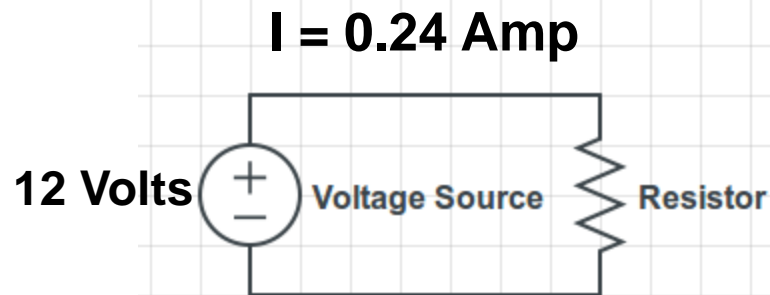


$$P = E \times I = E^2 / R = I^2 \times R$$

# Calculating Power #2

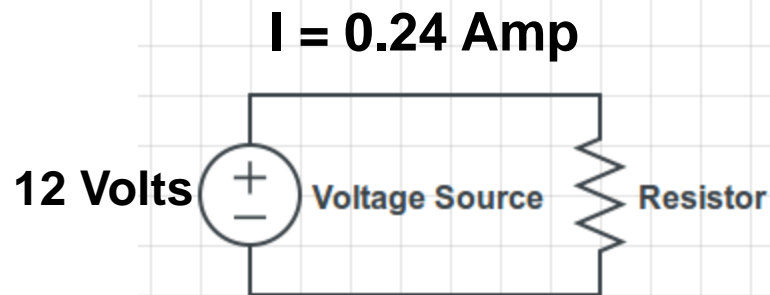

$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = E \times I$$

# Calculating Power #2

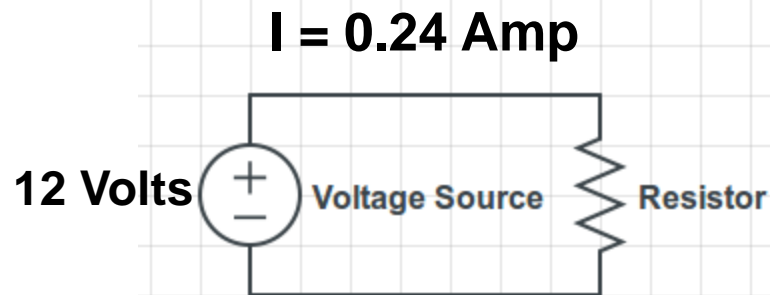


$$P = E \times I = E^2 / R = I^2 \times R$$

$$P = E \times I$$

$$P = 12 \times 0.24$$

$$P = 2.88 \text{ Watts}$$


# Calculating Power #3

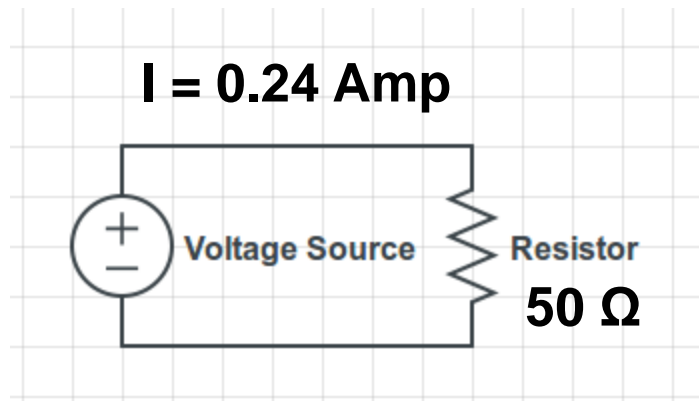

$$P = E \times I = E^2 / R = I^2 \times R$$




# Calculating Power #3

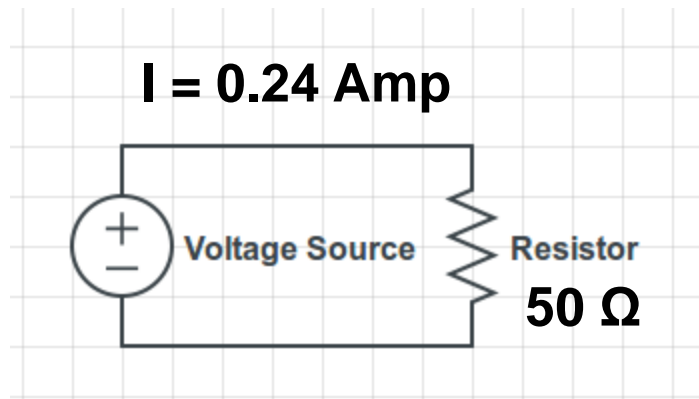

$$P = E \times I = E^2 / R = I^2 \times R$$
$$P = I^2 \times R$$

# Calculating Power #3

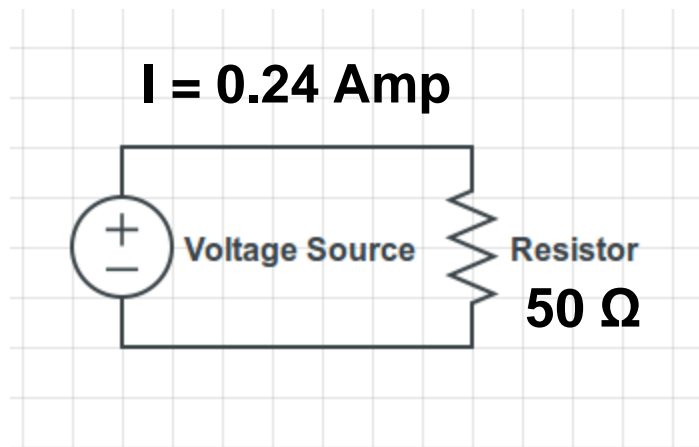

$$P = E \times I = E^2 / R = I^2 \times R$$

$$P = I^2 \times R$$

$$P = 0.24^2 \times 50$$

$$P = 0.0576 \times 50$$

$$P = 2.88 \text{ Watts}$$



# Questions?